

Illinois U Library NOVEMBER 1953

CQ RADIO AMATEURS' JOURNAL




COLLINS 32V-3

A self-contained table-top transmitter



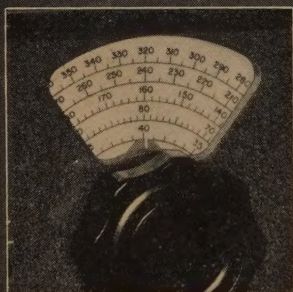Pick your frequency with the built-in 70E-8 VFO



You can count the kilocycles on the 32V-3 dial

- With this popular transmitter you QSY from the high end of 10 to the low end of 80 in a few seconds; just pick your band and set the built-in VFO to the desired spot. The 32V-3 will stay there — its frequency is controlled by the highly stable, built-in 70E-8 VFO.
- Have you ever wondered why the 32V-3 sounds so powerful on phone? It's because the audio circuits are Collins-designed and Collins-built for peak performance at speech frequencies.
- And, of course, spurious radiation has been reduced to an absolute minimum.
- The Collins 32V-3 runs 160 watts on cw and 140 watts on phone.

See your Collins distributor today for information on this popular transmitter.

For the best in amateur equipment, it's . . .

COLLINS RADIO COMPANY, Cedar Rapids, Iowa

11 W. 42nd St.
NEW YORK 36

2700 W. Olive Ave.
BURBANK

1930 Hi-Line Drive
DALLAS 2



CQ RADIO AMATEURS' JOURNAL

Vol. 9, No. 11
NOVEMBER, 1953

EDITORIAL STAFF

MANAGING EDITOR
OLIVER P. FERRELL

TECHNICAL EDITOR
E. M. BROWN, W2PAU

DEPARTMENT EDITORS

Herb Brier, W9EGQ	Novice
Wayne Green, W2NSD	Teletype
George Jacobs, W2PAJ	Propagation
Louisa B. Sando, W5RZJ	YL
R. C. Spenceley, KV4AA	DX

CONTRIBUTING EDITORS

Frank C. Jones,	W6AJF
G. F. Montgomery,	W3FQB
William I. Orr,	W6SAI
W. M. Scherer,	W2AEF

DRAFTSMAN

Thomas Smith, W2MCJ

BUSINESS STAFF

S. R. COWAN,	Publisher
S. L. CAHN,	Adv. Director
H. N. REIZES,	Adv. Mgr.
D. SALTMAN,	Prod. Mgr.
R. CAMPBELL,	Edit. Prod.
H. WEISNER,	Circ. Mgr.

BRANCH OFFICES

California: Ted E. Schell, 2700 West 3rd Street, Los Angeles 5, Calif. Dunkirk 2-4889.
Mid West: Harold F. Mann, 333 No. Michigan Avenue, Chicago 1, Illinois. Franklin 2-7100.
Foreign Subscription Representative: Radio Society of Great Britain, New Ruskin House, Little Russell St., London, WC 1, England.
Technical Book & Magazine Co., 297 Swanston St., Melbourne C1, Victoria, Australia.
Scandinavian Representative: Intrapress, 17 Nordre Paradisvej, Holte, Denmark.

CQ—(Title Reg. U.S. Post Office)—is published monthly by Cowan Publishing Corp., Executive and Editorial offices, 67 West 44th Street, New York 36, N.Y. Phone MURray Hill 2-0800. Reentered as Second Class Matter February 6, 1951 at the Post Office, New York, N.Y. under the Act of March 3, 1879. Subscription rates in U.S.A. Possessions, APO & FPO, 1 year \$3.00; 2 years \$5.00; 3 years \$7.00. Elsewhere add \$1.00 per year for postage. Single copies 35 cents. Printed in U.S.A. Entire contents copyright 1953 by Cowan Publishing Corp. CQ does not assume responsibility for unsolicited manuscripts.

POSTMASTER: SEND FORM 3579 to CQ, 67 WEST 44th ST., NEW YORK 36, N.Y.

OUR COVER

Ray Morris, W2QYS and W2AVA (seated) operating Bill Harrison's generator-powered Civil Defense field station. Complete in every respect, including Gonset, National and Collins equipment, this portable unit has been assigned to Area 1, New York State Command Net. A 2-meter ground plane antenna extends from the top of a Premax 36-foot telescoping mast. The PA speaker is connected to the Gonset "Communicator." A 96-inch whip antenna projects from the top of the station wagon. It is used on 10 meters and can be based loaded for the other bands. (Photographed by Joe Schimmel, W2QDM)

FEATURE ARTICLES

Antenna Rotation with a Servo-Mechanism
Henry G. Elwell, Jr., W2JKH.....13

Putting the BC-625 on 220 Mc.
Leroy W. May, Jr., W5AJG.....17

A Four-Band DX Antenna
Lcdr. Paul Lee, USN, W2EWP.....20

Simplified Pi-Network Solutions
J. J. Hoefer, W0III.....24

The Easter Island Expedition
Louis M. Desmaras, CE0AA, CE0AA/MM, CE3AG, CE3AX.....26

An Amplitude Modulation Review
G. Franklin Montgomery, W3FQB.....33

The Mail-Order Antenna
R. W. Johnson, W6MUR.....38

Commentaries:

MOBILE INSTALLATION BRIEFS
Norman Gertz, W1KYK.....28

THE QUESTION OF A HIGH-ANGLE RADIATOR
Major R. H. Mitchell, W6TZB.....29

Departments

DX and Overseas News (KV4AA).....30
The VHF-UHF News.....40
The YL's Frequency (W5RZJ).....43
Ionospheric Propagation Conditions (W2PAJ).....44
The Novice Shack (W9EGQ).....48


Miscellaneous

Scratchi 6
Zero Bias11

Check the specs...
Check the performance...

AND YOU'LL CHOOSE

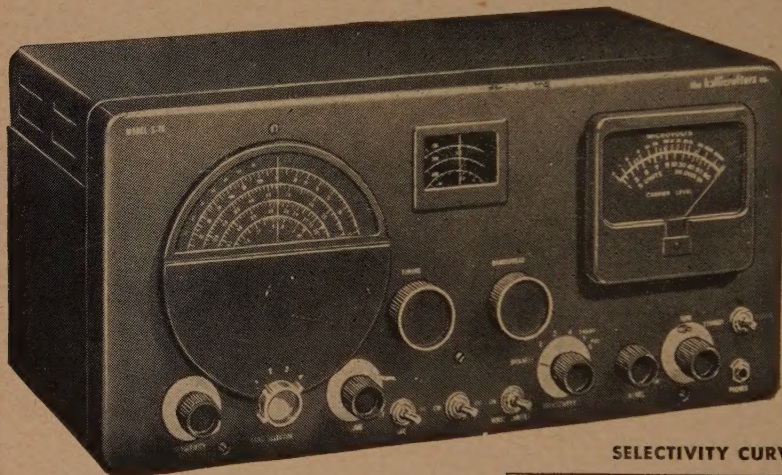Do you know any better way, any other way, to judge SW equipment than to check the specifications and the performance? Frankly that's the only valid way we can think of to make sure you get your money's worth. Check these specs. Take a look at the selectivity curve for the S-76. It is typical of the outstanding value Hallicrafters offers in every price class.



SELECTIVITY CURVES, S-76

Model S-76


Double conversion receiver. Broadcast Band 538-1580 kc plus three short-wave bands covering 1720 kc-34 Mc.

Calibrated electrical bandspread for easy tuning. Double superhet with 50 kc second i-f and giant 4-inch "S" meter. Five position selectivity, one r-f, two conversion, two i-f stages, temperature compensated. 3.2 or 500 ohm outputs.

Satin black steel cabinet. 18½" x 8⅞" x 9½" deep. Nine tubes, plus voltage regulator and rectifier.

For 105/125V. 50/60 cycle AC Use R-46 speaker

\$199⁹⁵

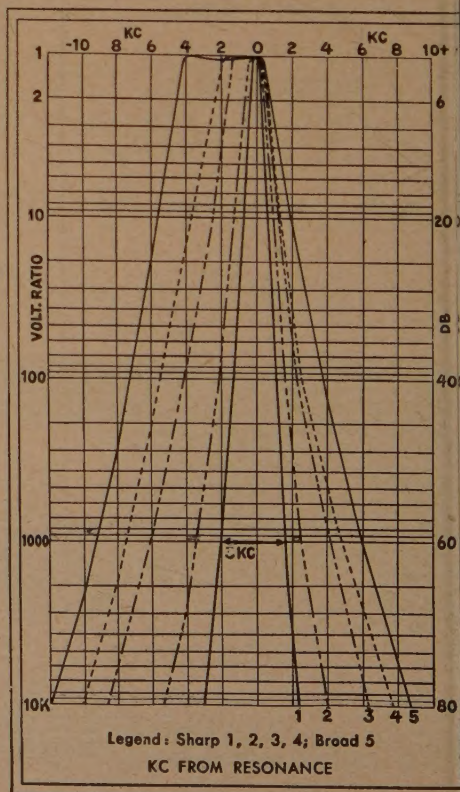

hallicrafters



Model HT-20. T.V.I. suppressed 100 watt AM-CW transmitter with all spurious outputs above 40 Mc at least 90 db. below full rated output.

All stages metered; single meter with eight position meter switch; output tuning indication. Frequency range of 1.7 Mc to 31 Mc continuous on front panel control. Seven tubes plus five rectifiers.

For 105/125 V. 50/60 cycle AC. . . . **\$449.50**

Model SX-71. Covers Broadcast Band 535-1650 kc plus four short-wave bands covering 1650 kc-34 Mc and 46-56 Mc.

Built-in Narrow Band FM one r-f, two conversion, and three i-f stages. Temperature compensated, voltage regulated. Three watt output (terminals for 500 and 3.2 ohms).

Satin black steel cabinet. 18½" x 8¾" x 12" deep. Eleven tubes plus regulator, rectifier. For 105/125 V. 50/60 cycle AC. . . **\$249.95**



Models S-40B, S-77A. Covers Broadcast Band 540-1680 kc plus three short-wave bands covering 1680 kc-44 Mc.

Electrical bandspread for easy tuning. One r-f, two i-f stages to draw in stations. Switches for automatic noise limiter, code reception and three-position tone control. CW pitch control and built-in speaker. Seven tubes plus rectifier. S-40B For 105/125 V. 50/60 cycle AC **\$129.95**
S-77A Same, for 105/125 V. AC/DC
32 lbs. **\$129.95**



Model R-46. Matching 10" PM speaker for use with Hallicrafters communications receivers SX-71, SX-76, SX-73 or SX-62. 80 to 5000 cycle range. Matching transformer with 500-ohm input. Speaker voice coil impedance, 3.2 ohms.

Satin black steel cabinet matches all Hallicrafters receivers. Cloth covered metal grille. 15" x 10¾" x 10¾" deep. Shipping weight 17 lbs. **\$24.95**



hallicrafters

World's Leading Exclusive Manufacturer of Communications and High Fidelity Equipment, Radio and Television


4401 West Fifth Avenue, Chicago 24, Illinois

Hallicrafters Ltd., 51 Camden Street, Toronto, Canada

Designed for



Application

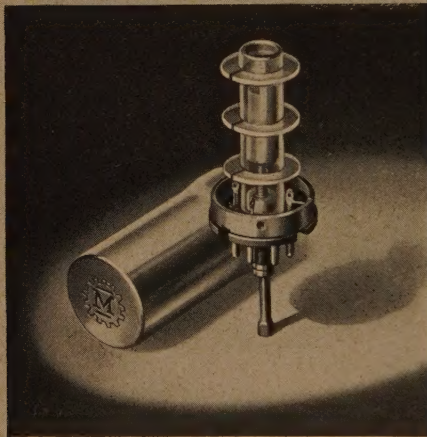

The No. 74001 Tunable Coil Form

Another new Millen "Designed for Application" product is the No. 74001 permeability tuned, shielded plug-in coil form. Standard octal base of low loss mica-filled Bakelite, polystyrene $\frac{1}{2}$ " diameter coil form, heavy aluminum shield, iron tuning slug of high frequency type, suitable for use up to 35 mc. Adjusting screw protrudes through center hole of standard octal socket. Special extension terminals facilitate connection to base pins.

**JAMES MILLEN
MFG. CO., INC.**

MAIN OFFICE AND FACTORY
**MALDEN
MASSACHUSETTS**



Feenix, Ariz

Dear Hon. Ed:

If you are knowing of any good bargains around town, letting me know, on acct. if anybuddies selling I'm buying. Boy oh boys, am I loaded down with the bux. Hon. Ed., Scratchi not filthy with money, he are wallowing in mud with the stuff. Wowie! what a feeling. I having so much money I considering subscribing to your Hon. Mag., instead of buying same fourth-hand at Joe's Triple-Dip Hunky-Dory Ice Cream and Used Magazine Parlor.

No, you needing not bother to looking through noosepaper to see what bank in Feenix are having been robbed recently. I are getting this money on acct. I not only reel smart gentlefellows, but quick thinker and geenyus to boot. But letting me begin as the commencing.

This past summer Hon. Brother Itchi are deciding it doing me good if I not staying around ranch, but getting out and seeing sum other parts of Hon. State. I agreeing, as only getting in trubbles at ranch. Howsumever, not doing much—as being without monies—until month ago, when I offered job at big dood ranch down near Toosahn. It seeming they having lots of boys 12 to 16 years old who wanting to learn how to being radio amchoors. The second I learning they willing to pay for deal likesame this I throwing a few clothes and lotsa radio parts in back of car and I'm off.

Now don't quick packing up your Hon. Suitcase because I not rolling in bux from what they paying. In fack, my salary are five measly bux a week, with room, food, and all the horses I can ride. Ha! You can putting all the horses I wanting to ride inside trans-sister and still having room left over for the geraniums. I not discouraged, on acct. food is good scenery are collosus and the class are small.

By second week are teecheing young kids how to making one-toob regenerative reseever. Idear going over grate after getting enough headphones so everybuddies can listening at once. Next, we are starting code practise, by listening in on amchoor bands. We getting along like peecky for cuppl days, until one nite we heering sum left-footed sender who not making sense. He sending stuff like XBGJKL WYTOPW QKLTZ and soforth.

We figuring this characters off his rockers until we heering him several nites after that, sending for ten minutes, then off for awhile, then on again. Finally I deciding to making copy of same. Ar


(Continued on page 8)

Bliley FOR 23 YEARS

...the dependable source
for AMATEUR CRYSTALS

TYPE CCO-2A CODE NO. E16

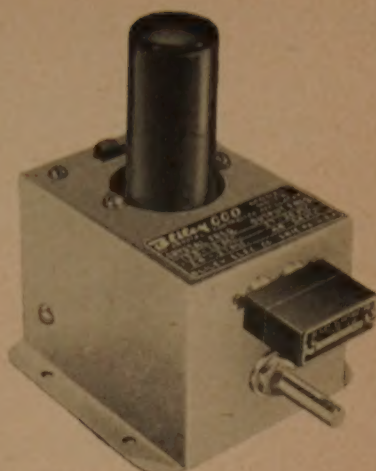Famous BLILEY "PACKAGED" OSCILLATOR
FOR 2-6-10-11 METERS



AMATEUR FREQUENCIES • CRYSTAL FILTERS • STANDARD FREQUENCIES

CODE	TYPE	APPLICATION	TOLERANCE	PRICE
E10	KV3	reference frequency 100 kc	±.005%	\$ 7.95
E11	MS433	reference frequency 1000 kc	±.005%	17.00
E13	MC9	13.6275 mc (multiplier to 27.255 mc) CITIZENS' RADIO SERVICE (CLASS "C")	±.04%	\$ 5.50
E14	CF3	455 kc—456 kc—465 kc Single Signal Filters	±5 kc	5.00
E15	CF6	455 kc—456 kc—465 kc Single Signal Filters	±5 kc	4.50

AMATEUR FREQUENCIES AND PACKAGED OSCILLATORS

E16	CCO-2A	packaged oscillator for 2-6-10-11 meters	11.95
E17	AX2	1803-1822 kc; 1878-1897 kc; 1903-1922 kc; 1978-1997 kc	±1 kc	3.75
E18	AX2	3500-3997 kc	±5 kc	2.95
E19	AX2	7000-7425 kc; 8000-8222 kc	±5 kc	2.95
E20	AX2	12.5-13.61 mc; 14-14.85 mc	±30 kc	3.95
E21	AX3	24-24.33 mc; 25-25.5 mc	±5 kc	3.95

SPOT FREQUENCIES FOR NET OPERATION

E22	MC9	3.0 mc-10 mc experimental frequencies	±.03%	\$ 4.80
-----	-----	---------------------------------------	-------	---------



KV3

CODE NO. E10



MS433

CODE NO. E11



MC9

CODE NO. E13 E22



CF3

CODE NO. E14



CF6

CODE NO. E15



AX2 AX3

CODE NO. 17 THRU 21

DIMENSIONS

CODE	TYPE	LENGTH	WIDTH	THICKNESS	PIN SIZE	PIN SPACE
E10	KV3	1 3/8"	1 1/8" (dia.)093"	.486"
E11	MS433	1 1/2"	1 3/8" (dia.)093"	OCTAL
E13	MC9	1 1/4"	1 3/8"	3/8"	.093"	.486"
E14	CF3	1 1/2"	1 3/8"	3/8"	.125"	.750"
E15	CF6	1 1/2"	1 3/8"	.695"
E16	CCO-2A	2 1/4"	3 1/4"	3"
E17	AX2	1 5/8"	1 3/8"	3/8"	.093"	.486"
E18	AX2	1 5/8"	1 3/8"	3/8"	.093"	.486"
E19	AX2	1 5/8"	1 3/8"	3/8"	.093"	.486"
E20	AX2	1 5/8"	1 3/8"	3/8"	.093"	.486"
E21	AX3	1 5/8"	1 3/8"	3/8"	.093"	.486"
E22	MC9	1 1/4"	1 3/8"	3/8"	.093"	.486"

BLILEY ELECTRIC CO., UNION STATION BUILDING, ERIE, PA.


(from page 6)



from "HASH"



to "SIRLOINS"

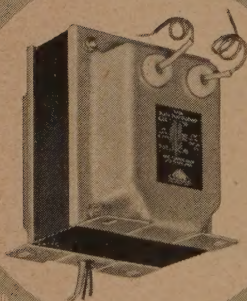

with

TRIAD TRANSFORMERS

If your QSO's are garbled due to modulator transformer QRM—then switch to Triad. Circuit tested for quality reproduction, Triad Modulation Transformers help insure uniform transmitter performance, without overmodulation, splatter or distortion. Short plate leads cut down losses, simplify installation and servicing. Multi-match design permits matching all popular types of modulators to RF load. Decal on case shows type and rating for easy re-ordering. Baked gray enamel finish adds professional smartness to your rig. From every standpoint—performance, long life, good looks and low cost, Triad Transformers are your best buy!

Write for Catalog TR-53E



filling many pages with messages, and next day showing them to friend of mine who Hon. Chief Op. at Border Patrol station nearby. This gentlemans not only l/c op. but he having much expereiance during last war desiphoning codes. After he over looking all the messages I bringing, he saying it un- probably meening anything, but he letting me know.


Not heering anything from silence for too days, then this selfsame Chief. Op. calling on landline and telling me to hotsfooting it to Border Patrol station immedjutly. I telling my class to designing for-toob reseever while I gone and off I go. When getting to station, Hon. Chief Op. grinning from ear to ear. He handing me envelope and telling me it all mine. Hackensaki! it are loaded with twenty dollar bills!!! I not even saying howcomes before he explaining how messages are reel honest-to-gracious spy messages. Are being sent by fellows who heading up ring of smugglers. Border Patrol getting dope from my messages and rounding up hole gang. Scratchi getting all the reward money.

Are hardly recovering from money when Hon. Chief Inspektor coming in room, shaking hand, and appointing me Honorary Border Patrolman—even giving me shiny new badge. I are-so exuberate I jumping in car and driving all way back to Itchi's ranch. Whooy! My class can go on designing for toob reseevers forever, but they not having champeers spy catcher Scratchi working at five measly bux a week.

Itchi and I counting money together, and I having twenty-five hundred smackers. My sacred Ant Fujii I never seeing so much monies in my life. After this Hon. Ed., please addressing me as Hon. Patrolman Scratchi.

Excoosing me, Brother Itchi coming in room. He say he been figuring out, and if I paying ate hundrec dollars he being able to paying income tax. INCOME TAX!! Hon. Ed., are you knowing a good lawyez what's cheep? I won't pay it. It's an outrage!! You think it easier to leeving home and heading for hills!! Letting me know quicklike, before income tax man gets here.

Respectively yours,
Hashafisti Scratchi

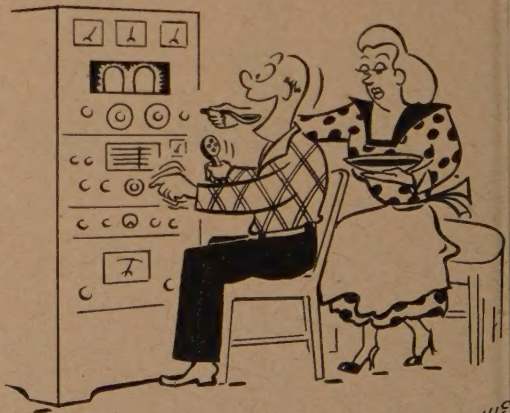

"... Nice signal, OM ... my number ... gulp
... 316280 ... seeuagin ... overnoff ... gulp.
CQ contest, CQ contest ..."

Zero Bias . . .

Docket No. 10712

On October 6th, the Federal Communications Commission released a "Notice of Proposed Rule Making" which would authorize Novice and Technician class licenses to be taken in the same manner as the present Conditional class license, i.e., by mail. (Particularly note: this is not a definite rule, but only a proposal which may possibly be enacted into the Rules and Regulations in 1954.)

The written and code portions of the examination would be conducted under the supervision of not more than two volunteer examiners either designated by the Commission or, under some circumstances, selected by the applicant. One examiner would conduct the code test and the other would handle the written theory portion of the test. The results of these examinations would then be attested to by the examiners and mailed to the nearest FCC Field Office. This is the identical procedure that the Commission has used for a number of years to provide a method of obtaining a license for the applicant who cannot reach a Field Office where examinations are periodically held.

The current proposal would also reduce the minimum distance that the Conditional class license need be from the examining point from 125 to 50 airline miles. Thus, not only would this docket permit the prospective Novice to take his examination, literally speaking, "by mail," but if he were also over 50 miles from the nearest Field Office, he could at a later date take a Conditional class examination that would give him the same operating privileges as the General class license holder. In addition, this docket would make it no longer necessary to submit to re-examination should the Conditional class licensee move to within 50 miles of the nearest field and examining office.

The Commission has indicated that these steps are being contemplated primarily in the interests of "stepping up" the processing of amateur licensing. While it is impossible to accurately estimate the work that might be saved by the Commission should this plan be

authorized, it is fairly safe to say that many important questions arise as to where the "time" is going to be saved, and how the processing is going to be "accelerated."

On the favorable side of the ledger, it is immediately obvious that the "conditions" under which an examination is being held will inevitably influence its results. Many prospective Novice or Conditional license holders will find it much more "comfortable" to have the examination given under the eyes of friends, or at least in surroundings that are familiar to the applicant. This would certainly tend to increase the total number of radio amateurs regardless of class. The past number of failures in the Conditional versus the General class examinations has clearly indicated that sometimes only one-tenth as many failures occur in the Conditional as compared to the General applications. There is little reason to suspect that this same approximation will not be carried into this new proposal and thus "accelerate" the number of applicants making the grade.

On the other side of the ledger, should the number of successful applicants suddenly increase, we are forced to ask where the time is saved by the Commission. The examinations still must be "graded" by the Field Office. While a minor amount of time will be saved by the Field Offices by not physically giving the examination, will not this saving only displace the work load into another division of the Commission (allocation of calls, etc.) which might result in the slowing down of the full licensing procedure from yet another quarter? It seems doubtful whether, on this one point alone, this docket is in the best interests of new Hams.

While the Commission has previously ruled against the "emotional" aspect in handing down decisions as they concern the Amateur Service, it is appropriate to mention that the new docket somehow is "degrading." The pride of accomplishment, as established by the so-called "Extra class license," is incompatible with the philosophy expressed under the new proposal.

Comments on this Docket may be filed with the FCC on or before December 31, 1953.

o.p.f.

PR

CRYSTALS

**AIRCRAFT-MARINE
BROADCAST-POLICE
FIXED SERVICES
AMATEUR-DIATHERMY
FREQUENCY STANDARD
MOBILE-INDUSTRIAL**



PETERSEN RADIO COMPANY, INC.
2800 W. BROADWAY • COUNCIL BLUFFS, IOWA

EXPORT SALES ONLY: Royal National Company, Inc., 75 West Street, New York 6, N. Y., U. S. A.

The Servo amplifier and rotator is mounted in the attic at the base of the 20-meter beam. Directly above the bearing is the coaxial feedline input connector.

This is the Solution to the Problem of Designing your Antenna Rotator—Let a Servo Point the Beam Automatically



Antenna Rotation with a Servo-Mechanism

HENRY G. ELWELL, JR., W2JKH

350 Hamilton Place, Hackensack, N.J.

The usual procedure in changing the direction of a remotely-controlled rotary beam is to snap on the motor switch, watch the direction indicator until the beam reaches the desired position, and then snap off the switch. Many amateurs attempt to set their VFO's, fill out their logs, monitor the band, or what have you, while the beam is turning. Quite often the result is that the next time they glance at the indicator they discover that the antenna has passed the desired position and is continuing on its way or has come to rest against the rotation stop. As W2JKH, however, I merely turn the antenna controller to the desired position and forget it, secure in the knowledge that, when the antenna reaches this position, rotation will cease. A simple servo-mechanism is the secret.

How a Servo-System Works

Figure 1 is the block diagram of a basic servo-system, whether it is used to steer an ocean liner

or to operate a furnace thermostat. The *Mixer-Feedback* circuit generates the signal that controls the system. When it is balanced, no error signal is fed into the amplifier, and no power is fed to the motor. Should the position of either the load or the controller be changed, a signal of phase and magnitude to correspond to the displacement is developed, causing the motor to move sufficiently in the opposite direction to re-establish circuit equilibrium.

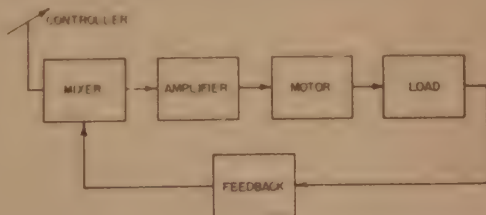


Fig. 1. Block diagram of the basic servo-system.

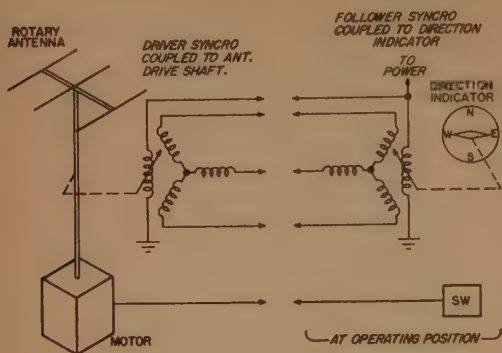


Fig. 2A. Conventional rotary beam antenna with synchro attachment for direction indication to the shack.

Various devices are used in the Mixer-Feed-back loop. One satisfactory arrangement is a pair of Synchro or Selsyn motors of the type frequently used as antenna direction indicators. Figure 2A shows how they are employed as direction indicators and Fig. 2B in a servo-system. In Fig. 2A both rotors are connected to an a-c power source. When they are in the same relative position, the voltages induced into the stators are equal in value and opposite in phase; therefore no torque is developed. As the beam moves, the "driver" Synchro rotor is turned, thereby generating a torque, and the "indicator" rotor turns to restore balance.

In Fig. 2B, only the "driver" rotor is connected to the power source. The "mixer" rotor is connected to the input of the amplifier. To understand the operation of the Synchros in this application, consider them as a two-part transformer, with variable coupling between the primary and secondary windings. The interconnected stators act as the coupling medium between them.

When the rotors are in the same phase, coupling is maximum, and when the phase difference is ninety degrees, coupling is minimum. The

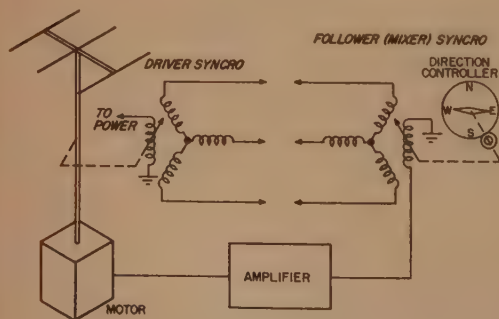


Fig. 2B. Servo-system showing the slight difference between this automatic system and the one pictured above in Fig. 2A. Addition of the amplifier diagramed in Fig. 3 makes all antenna positioning fully automatic from the operating position.

ninety-degree position is "normal," displacement from it couples part of the supply voltage into the amplifier through the "mixer" to act as the error signal mentioned above.

There are two general types of servo amplifiers, the *continuous-control* type and the *relay* type. Where it is necessary to control position to within a quarter of a degree or less, the former, which powers the motor directly, is indicated. Where an error of a few degrees can be tolerated, the relay type is satisfactory and much simpler.

As even a "sharp" rotary antenna seldom has a main lobe narrower than thirty degrees, a relay-type amplifier is the common choice, especially because any conventional rotator may be controlled with it.

A Practical Servo-system

Figure 3 and the photographs illustrate the beam-control system used at W2JKH. All parts, except the autosyns and the aircraft controller, which is used as the rotator, are standard, catalogue items. These parts are *surplus*, but are still available from several sources at reasonable prices.*

Actually, the rotator is not an essential part of the servo-system. Any standard rotator could be used, but this one is both economical and compact. Although a midget compared to a "prop-pitch" motor, it turns my three-element 14-Mc. beam with its nineteen-foot boom without difficulty.

Other Synchros may be substituted for those specified, but may require some modification of the amplifier input circuit.


The Amplifier

I have waited until the actual diagram was introduced to discuss the amplifier. Only the operation of the 2D21 thyratrons can be considered in the least mysterious. Their grids are connected in parallel and biased to plate-current cut off. The a-c error signal is fed to them through T1. A-c plate voltage is fed to the 2D21's in push-pull through the relay windings.

An error signal at the grids of sufficient amplitude and in phase with the plate voltage on one of the thyratrons will ionize the gas in it. This immediately reduces its plate resistance to a very-low value, and a large plate current flows, causing the relay to close and apply power to the rotator.

Once a thyatron "fires" its grid loses all control of the plate current as long as the plate voltage is positive and sufficient (10-15 volts) to maintain ionization in the tube, because the ionic bombardment of the grid neutralizes the effect of any external grid excitation. In this application, however, the a-c plate voltage auto-

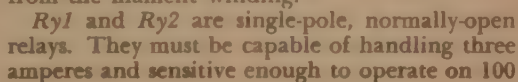* The reversible series motor, AYLC 1591 Aircraft Controller is readily available from surplus houses at this writing. The Synchros could be 26-volt, 400-cycle, Eclipse-Pioneer autosyns which are also commonly available. Editor.





The system described in the text easily rotates this three-element array on a nineteen-foot boom.

milliamperes (the maximum plate current rating of the 2D21's) or less. $R6$ and $R7$ limit the current to the desired value. 1,000 ohms permits about forty milliamperes to flow. The 50- μ fd condensers across the relay coils eliminate contact chatter and the .01- μ fd condensers across the motor leads eliminate brush noise.

The 24-volt, 400-cycle Autosyns work excellently on sixty cycles if the voltage is held to six or seven volts. I used a pair of one-to-one ratio gears to couple the driver Syncro to the beam drive shaft.

After the amplifier is wired, the next step is to adjust $C1$ to compensate for phase shifts introduced into the system. The easiest way is with the aid of an oscilloscope. Connect the vertical amplifier to the 2D21 grids and the horizontal amplifier to one of the plates. The resulting trace on the cathode-ray tube will be a diagonal straight line when $C1$ is correct. It will slant to the right or the left depending upon which plate is chosen, and which direction the *controller* Syncro is displaced to generate the error signal.

Incidentally, the scale and case for the *controller* may be a revamped *surplus* position indicator, or it may be constructed with a pointer on the Syncro rotor and a dial scale. Put enough friction on the pointer to hold it in position once it is set.

After $C1$ is adjusted, the amplifier gain must be set to match the output of the *Mixer* Syncro and the amount of coasting in the beam when power is removed from the motor. This is necessary for this reason: suppose the beam coasts five degrees. Also suppose that the amplifier gain is high enough; so that a position error of a degree or two is sufficient to fire the thyatron. As the antenna rotates, the error signal is reduced to zero when the antenna approaches the desired position and the relay opens, removing power from the motor. However, the antenna will coast beyond this point, producing an error signal of the opposite polarity. The other thya-

tron fires and closes the other relay, applying reverse current to the motor. The antenna comes to a shuddering stop and starts back in the opposite direction—if nothing breaks. The cycle may be repeated indefinitely as the system "hunts" for the null. Do not underestimate the strain it places on the motor, gears, and antenna even at a speed as low as one r.p.m.

To check the system for "hunting," put a piece of paper between one set of relay contacts, and turn the *controller* to close the other relay. Carefully watch, as the antenna zeros in to see if there is enough play or coasting to permit the second relay to close after the first opens. The paper between its contacts will prevent possible damage during the test.

Amplifier gain can always be reduced sufficiently to eliminate "hunting," but it is desirable to keep it reasonably high to permit more accurate antenna positioning. If all coasting and "play" were eliminated, accuracies of about one degree would be possible.

With a full twenty-eight volts on the driver motor, the AYLC 1591 rotated my antenna at two r.p.m., which resulted in quite a bit of coasting. Adding $R8$ reduced the speed to about one r.p.m. and coasting to about five degrees. By proper adjustment of $R1$, the relays open just as the antenna approaches the desired position and it coasts right on the nose.

There are at least three ways to make the antenna position shown on the *controller* agree with the actual position of the antenna. One is to allow the antenna to assume a position, loosen the clamp holding the *controller* case, turn the case until the beam to null again, repeat until the *controller* and antenna position agree. The second is to loosen the *controller* setscrews and turn the pointer or dial to position, without holding the rotor. Then retighten the setscrews. A third is to disengage the *driver* gear from the one on the antenna drive shaft, pull out the 2D21's, and manually close one of the relays until the antenna position corresponds with that on the *controller*. Re-engage the gears and place the tubes.

A Word of Caution

A servo-controlled rotator will always turn the antenna in the direction requiring the least angular motion to produce a null in the error system. For example, if the antenna is pointing north, and you desire it to point east, it will turn clockwise ninety degrees to reach the new position, whether the *controller* is turned ninety degrees in the clockwise direction or 270 degrees in the counter-clockwise direction. In an antenna installation with unlimited rotation, this entails no special problems. However, where feeders limit rotation, it could result in trouble.

A stop on the *controller* to limit its rotation to 360 degrees will eliminate almost all danger of twisting up the feeders. Not quite all, however. As explained above, if the *controller*

(Continued on page 58)

Putting the BC-625 on 220 Mc.

LEROY W. MAY, JR., W5AJG

9428 Hobart Street, Dallas 18, Texas

In Answer to Many Requests on How to Fire Up on 220 Mc.
We are Pleased to Present this Conversion Article on the
SCR-522 Transmitter Unit

The transmitter unit of the SCR-522 (BC-625) has added another conquest to its already long list of achievements. No doubt, it has been used in one form or another on all amateur bands from 160 meters on down to 2 meters. With the growing popularity of the $1\frac{1}{4}$ meter band, it is only natural that it would, sooner or later, move into that band.

Just as on all the other bands involved, there are probably many different ways to make this transmitter work satisfactorily on 220 Mc. The method to be outlined is one that has worked nicely and the output after conversion to 220 Mc. is approximately the same as when used in its natural state on 144 Mc. All meter readings should run just about what they do on 2 meters.

The Oscillator Stage

This stage originally is equipped with a type 6G6G tube (VT-198A) with the grid circuit operating in the 8-Mc. band and doubling in the plate circuit to 16 Mc. Before going further, and to refresh the memory, the original oscillator tube drives a type 12A6 which triples to 48 Mc. and in turn drives the first 832A tripler to 144 Mc. The last 832A in the unit is an amplifier, operating straight through on 144 Mc.

It is desirable to keep the last 832A operating as a straight-through amplifier on 220 Mc. if at all possible, so as to make the output on $1\frac{1}{4}$ meters the same as on 2 meters. This condition was met with no difficulty.

Therefore, the new line up will be $3 \times 3 \times 3$ plus the straight-through final, instead of the original $2 \times 3 \times 3$ and the straight-through final. The same series of 8-Mc. Crystals may be used. These will be in the frequency range 8144 kc. to 8333 kc. which will represent the limits of the 220-225 Mc. assignment.


Now back to the oscillator stage. Several tubes and circuits were tried in this stage and nothing at all was gained over the original tube, so the 6G6G was replaced and used. The changes that are necessary in circuitry of the oscillator-tripler stage are these:

1. Since the plate circuit will now triple to 24 Mc., it becomes necessary to remove 4 turns from the cold end of the plate inductor (118). The grid dip meter should now show that the circuit tunes through 24 Mc. No change is made in the plate tuning condenser (114).


Numbers used indicate the designation given by the Army to the various components of the BC-625 transmitter.

The 12A6 Stage

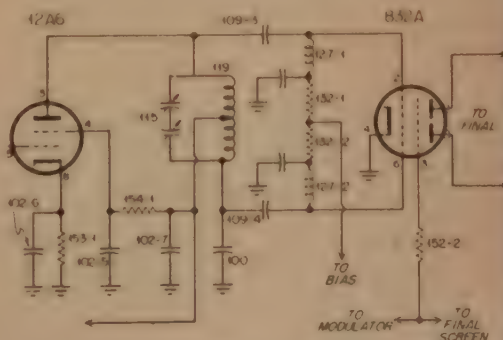This is the second tube in the r.f. string and is again used as the first tripler, taking the 24 Mc. oscillator output and multiplying to 74 Mc. It is possible that other later and "hotter" tubes



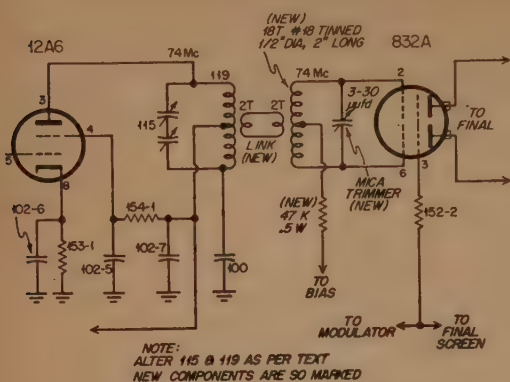Original circuit of the 1st and 2nd harmonic amplifiers in the BC-625 transmitter.



Modified tripler stages in the BC-625.

might work better in this stage but not too much was done along these lines. The old original 12A6 tube will triple and deliver ample drive to the next stage after a few modifications. Right now it is necessary to scale down the plate condenser and coil of this 12A6 tripler stage as follows:

2. Remove three turns from each end of the plate coil (119) and remove and discard the form on which the coil is originally wound. This will leave an air wound coil and the spacing should be adjusted so that the overall length of the coil is 1½ inches.

The plate condenser (116) should be altered so that 4 rotor and 4 stator plates are all that is left. This means removing 2 stator plates and 3 rotor plates.

A word about this plate removing operation. It is not necessary to remove the condensers at all. A pair of long needle-nose pliers and a little judicious wiggling and pulling will get the job done easily. After the first couple of plates have been pulled, the technique becomes simple. The grid-dipper should show resonance in this stage at 74 Mc.

The First 832 Stage

So far, we have been dealing with rather low frequencies (to a v-h-f man). Now the first

832A stage will become a tripler from 74 Mc. to 220 Mc. which is our final frequency. At this point an experiment is suggested. First off, leave the grid circuit of this first 832A stage as is, namely capacity coupled to the preceding 12A6 tripler. If the 832A is receiving ample excitation, there is no point in changing the input grid circuit. As most all owners of 522's have learned, these things look just alike, but do not always work exactly alike. Some are just naturally "hotter" for some reason. Here at W5AJG we felt that the grid of the first 832A stage was just a little low on excitation for best tripling efficiency, so we discarded the capacity coupling from the preceding stage and put in link coupling.


This will necessitate a new grid tank for the 832A input circuit resonating at 74 Mc. but plenty of room is available and it can be made up and installed in a few minutes. Upon installing this new circuit, it was found that the excitation had increased sufficiently for good tripling efficiency. The new coil is made as follows:

3. On a $\frac{1}{2}$ inch diameter form, wind 18 turns of No. 18 tinned solid bus wire. Remove the form and adjust spacing until the overall length is 2 inches.

The coil is tapped in the middle and a new 4000-ohm $\frac{1}{2}$ -watt grid resistor is fed in at this point. The coil is mounted directly to the grid lugs of the 832A socket and a 3-30 μ fd. mica compression trimmer is wired with stiff wire in parallel with the coil. It may be adjusted from the top of the set. A link of two turns at either end is made of insulated hookup wire and feeds from the 12A6 plate coil to the center of the new coil. When using this modification in the grid circuit of the first 832A, the components comprising the capacity coupling setup can be removed and discarded. These are:

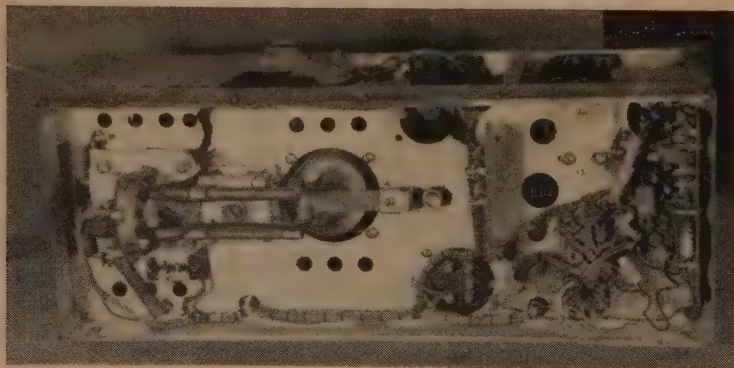4. Coupling condensers *109-3* and *109-4*
R-F chokes, *127-1* and *127-2*.
Grid resistors, *132-1* and *132-2*.
Bypasses, *102-8* and *102-9*.

The plate circuit of the first 832A tripler requires complete modification and the same will



This view shows the output of the first 832A stage and the input circuit of the final 832A amplifier. Both circuits operate on 220 Mc. and are link coupled with a piece of hookup wire shaped in the form of a closed hairpin.

hold for the grid and plate circuits of the final 832A amplifier. These circuits are now operating at 220 Mc. and the inductors will take the form of lines and hairpins.

In the plate circuit of the first 832A tripler stage the changes will be these:

5. Remove 4 rotor plates from the plate tank condenser (116). This will leave only 1 rotor plate in use. Remove and discard the following parts associated with the output of the tube: Plate tank coil (120). This is actually 2 wires in the form of a line. Coupling condensers, 109-1 and 109-2. R-F Chokes, 127-3 and 127-4. Bypasses, 102-12 and 102-13.


See the photograph showing the layout in the new form of the output of the first 832A and the input of the 832A straight through amplifier. Construct the new inductors you see as follows:

6. For the plate output inductor of the first 832A use shorted section of line composed of $\frac{1}{4}$ inch copper tubing spaced 1 inch center to center and $4\frac{1}{4}$ inches long.

Again referring to the photo, mount this line by two pieces of copper strap to the tank condenser (120) and out about $\frac{1}{2}$ inch from it. This actually places the tuning condenser of the 832A back about three inches from the hot end of the lines. Right at the hot end of the lines and for connection to the plate pins of the tubes, a couple of pieces of soft copper strip about $\frac{1}{4}$ inch wide are soldered to the tube connectors, which will be clipped to the plate pins of the 832A tube.

Final 832A Amplifier

Continuing on to the grid circuit of the 832A final, it is seen that a new grid input inductor is used. This consists of a hairpin shaped piece of copper strap going from grid lug to grid lug on the tube socket. It is made of a piece of material of about 0.015" thickness, $\frac{3}{8}$ -inch wide and 5 inches long. It is bent into shape and at the base is 2 inches wide, just the same spacing as the grid lugs on the 832A socket.

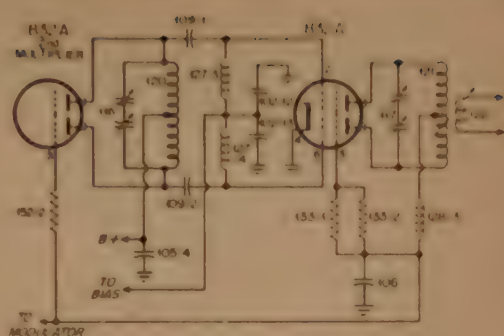

Original circuitry of the 832A final amplifier.


Also in parallel with the loop at this point is another 3-30 μ mf. mica compression trimmer condenser. The grid resistor for the final grid is that normally used as well as an additional 2000-ohm $\frac{1}{2}$ -watt resistor soldered at the electrical center of the hairpin.

Coupling between the hairpin and the previously described lines is obtained by forming a piece of insulated hookup wire around the two tank circuits. A little experimentation will produce the maximum grid current to the final.

As to the plate circuit of the final 832A amplifier, use is again made of another copper strap hairpin loop identical to the one just described for the grid circuit. This inductor is soldered on the final tank condenser (117). The original inductor (121) is discarded as well as the antenna coupling loop (122). A one-turn loop is used for the antenna pickup and this new loop is soldered to the antenna receptacle formerly holding the variable coupling link. The tank condenser (117) is again altered using the same technique for removing 4 rotor plates. This leaves only one rotor plate in use. All circuits associated with the last 832A stage should now grid dip to 220 Mc.

The plate condenser of the final stage has soldered to it two copper strips as previously described to engage the plate pins of the tube. Do not use the original flexible braided wires

(Continued on page 57)

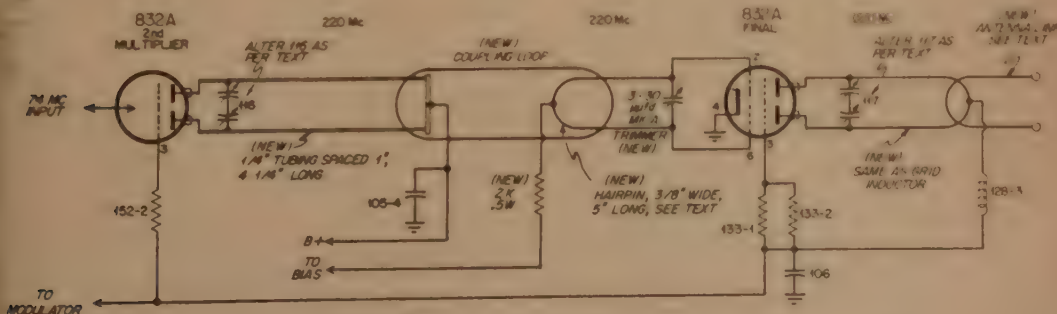

Modified 832A final amplifier showing the loops and coupling links to put it 220 Mc.

A Four-Band DX Antenna

LCDR. PAUL LEE, USN, W2EWP

c/o OPNAV, OP202XI, Navy Department, Washington, D.C.

Thought Provoking Design of a Vertical Radiator with Details of its Evolution and Construction

Do you have but little space for antennas? Do you want to be able to work four bands with one antenna? Do you have TVI troubles? Do you covet that *S9 Plus* report from half-way around the world? If you do, read on, for here is a reasonable and sensible answer to your wishes. If you aren't interested in any of these things, read on anyway, because here is an idea that you and the boys in your net can kick around a bit during "ragchews."

The antenna described here is a vertical radiator or perhaps we should say it is a combination of two vertical radiators. Looking back on our days in radio broadcast engineering, we remembered that a vertical radiator of the proper height is excellent for low-angle radiation. By reference to textbooks and past experience, we know that a height of 0.58 wavelength for our vertical radiator gives us the most low-angle radiation for our money. The calculated verti-


cal radiation pattern for a 0.58 wavelength vertical radiator is shown in *Fig 1a*. Inasmuch as the length of an antenna in wavelengths varies directly as the frequency, we can select a length which will be 0.58 wavelengths at the highest frequency we wish to use.

With the advent of the 21-Mc. band, and the more recent opening of it to phone operation, we were faced with the problem of selecting an antenna system which would work on four bands. We have neglected 28 Mc., because it is not going to be a very useful band to us for the next few years due to the trend of the sunspot cycle. We had been getting very good results with a drooping ground plane vertical radiator on 21 Mc., so the thought hit us, "Why not put it on top of our vertical radiator?", thus solving the problem as far as 21 Mc. was concerned.

Radiation Patterns

That left us 14, 7 and 3.9 Mc. still to be accounted for. So we then selected a *total antenna length* of 39 feet as being 0.58 wavelengths at 14 Mc. This length includes the 11-foot 21-Mc. drooping ground plane's whip. A length of 39 feet becomes 0.30 wavelengths at 7 Mc., and 0.16 wavelengths at 3.9 Mc. These are reasonable lengths for the lower frequencies. The calculated radiation patterns for 0.30 and 0.16 wavelength vertical radiators are shown in *Figs. 1b* and *1c*. As inspection of these curves will show, we are still able to get good low-angle radiation from our vertical at these frequencies.

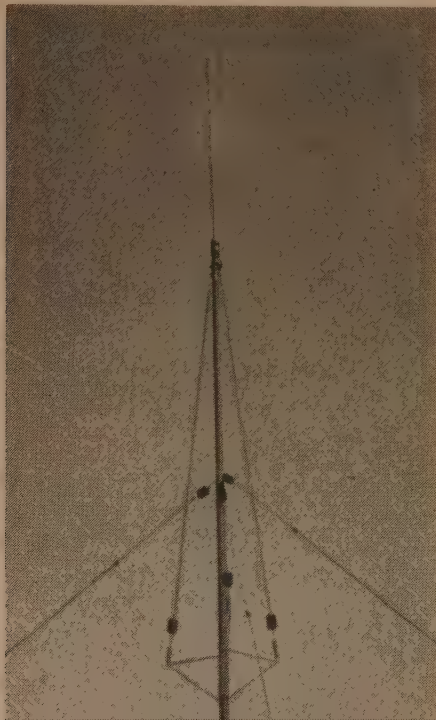Constructional details of the antenna are shown in *Fig. 2*. The mast is made from 2" aluminum tubing. It rests upon a large and rugged standoff insulator, and is guyed at a point 20 feet from the ground, in three directions. The guys are broken up by "egg" insulators, so that no portion of any guy is as long as 11 feet.



The vertical radiator when the author was at W4RXO. The total over-all height is only thirty-nine feet. Three drooping radials are used on 21 Mc., and a ground screen on all other bands.

The fitting which holds the 21 Mc. whip at the top of the 2" mast is a surplus type MP48 whip base insulator, complete with spring. It provides a means for fastening the coaxial feed line internally. The whip is made of surplus M551, M552, M551 and M552 whip sections, with the last section cut to give an overall whip length above the base insulator of 11 feet. A machined fitting holds the base of the MP48 whip base tightly inside the top of the 2" mast. The drooping ground plane radiator is fed by means of RG-8 U coaxial line which goes down through the mast, and which terminates in an



Fig. 2. Construction details of the 4-Band antenna. Only one radial has been shown in this drawing for the purpose of clarity.

SO-239 chassis type female connector set into the mast just above the base insulator. The outer conductor of this line is thus connected to the mast at top and bottom.

The three drooping ground plane radials are mechanically fastened to the MP48 whip base by means of three small "egg" insulators, and are electrically connected to the MP48 base at only one place, which is a bolt in the side of the "ground" portion of the MP48 base, above the spring. The length of each radial is exactly 11

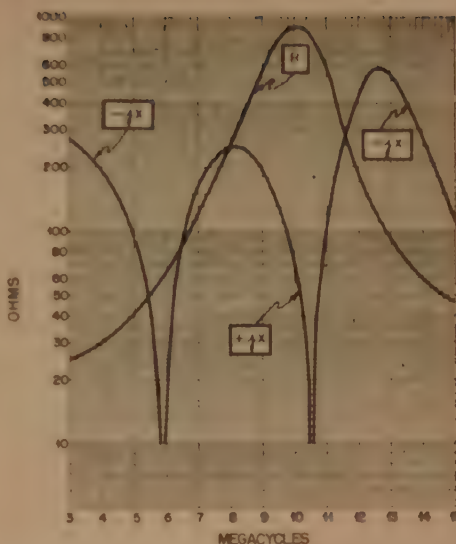


Fig. 3. Measured radiation resistance and reactance of the 4-Band antenna. The method of matching was developed after these measurements had been made.

feet, measured from this bolt. The bottom ends of the radials are secured to large "egg" insulators, which are fastened to brackets which hold the bottom ends of the radials a distance of 1 foot out from the mast.

At this point you are probably beginning to wonder how the 11-foot whip at the top of the mast is made to act as extension of the mast, and to radiate, at the three lower frequencies. Well, take a look at Fig. 2, and you will see that we have used a 7-foot 6-inch piece of RG-8/U coaxial line as a shorted quarter-wave stub cut for 21 Mc., the open end of which is connected between the whip and the drooping ground plane. The outer braid of the stub line is connected to the mast at several places along its length. The connection between inner conductor, outer braid, and mast itself, at the lower end of the stub, serves to effectively connect the whip to the mast at the three lower frequencies. This would not be true, of course, if the stub were insulated from the mast.

The Matching Network

Now, the question of feeding power to this antenna at four different frequencies arose.

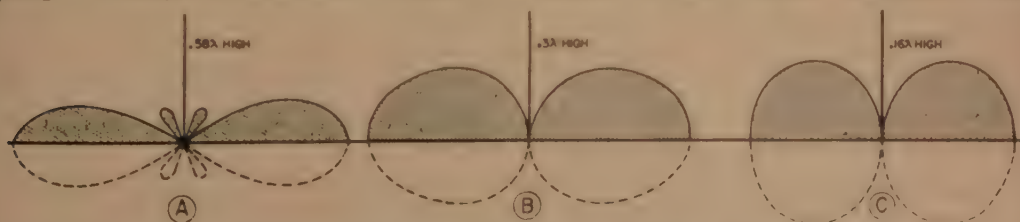


Fig. 1. Theoretical vertical radiation patterns. The antenna is considered to be 0.58 wavelength on 20 meters, 0.30 wavelength on 40 meters and 0.16 wavelength on 75 meters. Radiation on all of these bands is at the most favorable angles.



Base and tuning unit at W4RXO. The two-inch diameter aluminum tubing rests on a surplus insulator.

Obviously, we needed some sort of matching system between the base of the mast and our *RG-8/U* transmission line for our three lower frequencies, and we also had to feed 21-Mc. power to the drooping ground plane radiator at the top of the mast.

The first step was to measure the radiation resistance and reactance of the antenna at 3.9, 7, and 14 Mc., with a *General Radio Model 916A* r-f bridge. In order to get the complete picture, we took measurements at one megacycle intervals from 3 to 15 megacycles, and the results are plotted in Fig. 3.

The base impedance of our antenna at the three lower frequencies is shown in this table:

	R	X
3.9 Mc.	30	-j200
7.25 Mc.	135	+j190
14.25 Mc.	59	-j195

These three impedances can be matched to our 52-ohm line by a network such as the one shown in Fig. 4. At 3.9 Mc. the large inductance is used as a tapped loading coil. The exact size of the coil can be calculated, using an inductive reactance of 200 ohms at 3.9 Mc., which is required to balance out the 200-ohm capacitive reactance of the antenna. The position of the

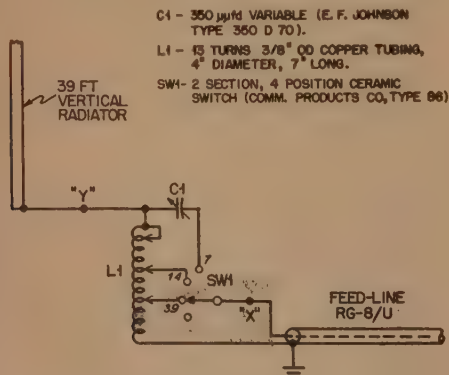


Fig. 4. Schematic of the matching network.

tap can be determined easily by experiment. At 14 Mc., the tap on the coil is at a higher position. At 7 Mc., we have a simple *L*-network with the series capacity in the feedline to balance out the inductive reactance of the antenna at this frequency. Adjustment of the 14-Mc. tap, and the setting of the variable condenser for 7 Mc., may be easily done by trial.

How did we feed the 21-Mc. power to the coaxial line up the mast? No, we didn't just plug it in when we wanted to go on 21 Mc. We wound the large coil out of coaxial line, and fed the 21-Mc. power through this line, and used coaxial line from the coil to the base of the mast as the lead-in for the three lower frequencies. Take a look at the sketch, Fig. 5, and at the photographs, and you will see how this was done.

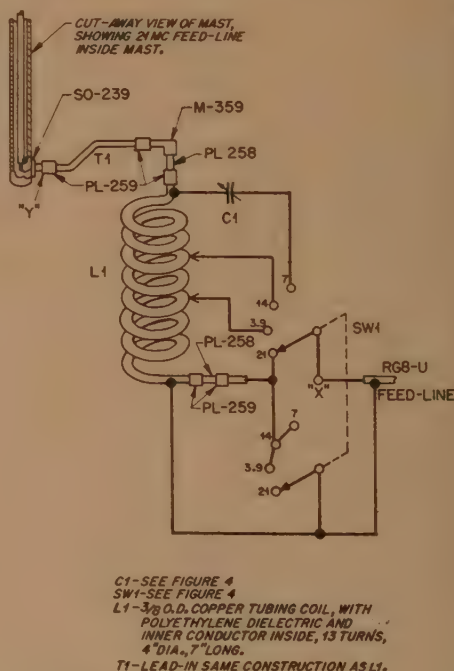


Fig. 5. Construction details of the matching network.

Where did we get our copper coaxial line? Why we made it! It was very easy. We took 15 feet of *RG-8/U*, stripped the vinyl covering and outer copper braid from it, thus leaving the polyethylene dielectric and the inner conductor. We then slipped this into a 15-foot length of 3/8" O.D. copper tubing, where it fits very nicely making our required length of copper coaxial line, and we wound it into an inductance of the proper size. A *PL-259* coaxial male plug was soldered on each end of the coil, and through the use of *PL-258* female junction fittings, connection can be made to the feed-line at each end of the coil, with *PL-259* plugs. A similar short piece of this home-made copper tubing coaxial line was used between coil and mast fitting as the lead-in. We passed it through an *E.*

Johnson Type 135-67 insulator before soldering the PL 259 plugs on the ends. It fits very nicely through the hole in the insulator; after the bolt is removed. After installation, the hole was caulked with rubber cement to make it water proof.

We used one coaxial line for the 21 Mc. and lower frequency feeds from the transmitter. The switching from 3.9 to 7 to 14 to 21 Mc. was done by means of a large rotary switch, as shown in Fig. 5. Relays may be installed to do this job, by remote control, if desired.

Note that the inner conductor of the coaxial coil *I.I.* is grounded at 3.9, 7, and 14 Mc., at the ground end of *I.I.*, through the contacts of *Sw1*.

Ground System

Our tuning unit, built into a waterproof aluminum box, is shown in the photographs. Once adjusted, it is closed up and left alone. The rotary switch shaft projects through the side of the box with a rubber grommet to keep water out. It is turned by using a screwdriver.

An antenna of this kind needs a good ground system. We buried eight radials, of #12 bare copper wire, each 60 feet long. They are all tied together at the base of the antenna, and one ground lead is brought up to the tuning unit cabinet. A six-foot square piece of copper ground screen would be a very good addition to this ground system, and some day we intend to put one in. The radials should be soldered to it, as shown in the sketch, Fig. 6. Of course, the ground system was installed *before* the resistance and reactance measurements were made!

In tuning up, it was useful to insert a 0-5 ampere line-current r-f ammeter at point "X," and a 0-9 ampere antenna current r-f ammeter at point "Y." The antenna current meter



Fig. 6. The efficiency of this type of antenna depends upon the ground system. This is the suggested arrangement for radials at the base of the antenna.



Fig. 7. This antenna current meter should be inserted at point "Y" in Fig 5 while the antenna is being tuned up.

needed an adapter to enable it to be plugged in between the coaxial lead-in and the connector at the base of the mast. This is shown in Fig. 7. For r-f current measurement purposes, the inner and outer conductors of the coaxial lead-in were connected together, as shown. When the system is properly tuned up on any one of the lower frequency bands, the power in the feed-line and antenna can be easily computed by Ohm's Law, for the line impedance is 52 ohms, and the radiation resistance of the antenna is known. These two power readings should be equal, and should also be equal to the final amplifier's power input multiplied by a reasonable efficiency figure, of say 70%. In our case our power output is approximately 670 watts.


Results

The results obtained with this antenna system on all four bands have been most gratifying. The drooping ground plane gives us very good low-angle radiation on 21 Mc. You may wonder why we "drooped" the radials so much, when the usual practice is to run them out at about 45 degrees from vertical. Well, we wanted to lower our angle of radiation, for one thing. And then, too, we wanted to keep them down alongside the mast so that they would not have a tendency to act as top-loading at the lower frequency bands and thus throw off our antenna height pattern calculations. By installing them as shown, there is a slight mismatch between the RG-8/U line and the ground plane antenna, but our standing-wave ratio on the line at 21 Mc. is only in the order of 1.35:1.0, and we did not consider this to be objectionable. We could perhaps eliminate standing waves entirely by making adjustments to the shorted quarter-wave stub, but it's not worth climbing a 2" pipe mast to do it! However, one of our dreams is to some day use a short, triangular tower of the "TV antenna" type as our vertical radiator, and then we'll be able to climb it and make such adjustments.

On 14 Mc. we can notice the difference between this antenna and the usual half-wave doublet or quarter-wave vertical, both of which we had used previously. Overseas signals are much stronger, and there is less "short-skip," or "stateside" QRM, because of the shape of the vertical radiation pattern, shown in Fig. 1. On 7 Mc. it performs beautifully, giving us S9 plus reports on almost every contact. On 3.9

(Continued on page 58)

Simplified

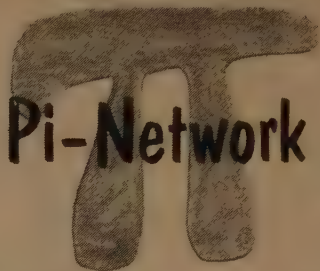

Pi-Network

Solutions

J. J. HOEFER, WØIJ

7510 Lowell, Overland Park, Kansas

This is an Easy Approach to Designing Your Own Pi-Networks for Inter-stage or Final Tank Circuits

The pi-network is an integral part of a considerable number of commercial radio transmitters. It is also becoming increasingly popular in home-built rigs. The advantages offered by the pi-network include the ability to match a large variety of antenna impedances to a very wide range of tube loading characteristics. Higher order harmonics may also be attenuated, inter-stage coupling can be effected with less TVI and coaxial cables may be easily fed with assurance that a maximum power transfer is possible.

Numerous articles ^{1, 2, 3, 4} have presented design information on the pi-network. This article

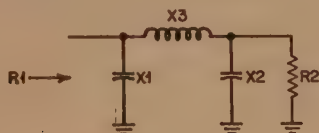


Fig. 1. Pi-network configuration with $R1$ representing the input load and $R2$ the output load.

shows a new simplified approach which permits the quick solution of problems involving antenna impedances of from 30 to 1000 ohms and tube loads of from 1500 to 9500 ohms.

Elementary Theory of Problem

To find how this simplified approach may be used refer to Fig. 1. In this schematic we see the commonly pictured circuit of the pi-network, where $R2$ is the load resistance (generally presented by the antenna, etc.) and $R1$ is the resistance looking into the pi-network. Note that $X2$ and $R2$ are in parallel and according

to Schottland ¹ they may be replaced with their series equivalents Xe and Ra . However we may also cancel the series capacitive reactance of Xe through the insertion of some additional inductive reactance, $X4$. Essentially speaking our tank circuit becomes $X3$, $X1$ and Ra (see Fig. 2).

The following relationships become apparent where the Q of the circuit is more than 10:

- (1). $Q = X3/Ra = R1/X1$
- (2). $X3 = X1$
- (3). $Ra = R1/Q^2$
- (4). $X4 = Xe$

The most difficult part of pi-network calculation now becomes the conversion of $X2$ to its series equivalent Xe .

This conversion is readily accessible if presented in graphical form (see Fig. 3). Here we see plotted $Ra/X2$ against $Ra/R2$. For problems where $R1$ and $R2$ are both known, Ra may be calculated from the equation (3) and $X2$ determined from the graph. It is now only necessary to calculate the ratio $Ra/R2$ and enter the graph along the horizontal axis at this value, read $Ra/X2$ from which $X2$ may be found.

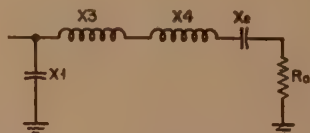


Fig. 2. As shown in Fig. 1 the reactance $X2$ and the load $R2$ are in parallel and may be replaced by their series equivalents Xe and Ra . Additional inductance $X4$ cancels the capacitive reactance of Xe .

Thus, a complete family of curves is unnecessary (involving $R2$, Ra and $X2$) and in addition, since $Ra/X2$ equals $Xe/R2$, the value of Xe may also be calculated.

1. Schottland, "Pi-Networks as Coupled Tank Circuits," *ELECTRONICS*, April, 1944.
2. Pappenfus and Klippel, "Pi-Network Tank Circuits," *CQ*, September, 1950, p. 26.
3. Whalley, "The Design of Pi-Network Tank Circuits," *R.S.G.B. Bulletin*, April, 1952, p. 439.
4. Technical Topics, *QST*, April, 1952, p.

Working Example

Assume that we want to design a pi-network that will match a quarter wave whip antenna with a radiation resistance of 35 ohms to a tube running 600 volts at 100 ma input. To a good approximation the tube will want to see the following load

$R1 = 500 \Omega$
 $R1 = 500 \times 600 / 100$
 $R1 = 3000 \Omega$

So the problem becomes one of matching 35 ohms ($R2$) to 3000 ohms ($R1$). As a result, if we assume a Q of 10 or more, using equation (3)

$Ra = R1 / Q^2$
 $Ra = 3000 / 100$
 $Ra = 30 \text{ ohms}$

and the ratio

$Ra / R2 = 30 / 35$
 $Ra / R2 = 0.86$

and from Fig. 3

$Ra \times X2 = Xe \times R2$
 $Ra \times X2 = 0.35$

from which

$Xe = 12.2 \text{ ohms}$ and $X2 = 86 \text{ ohms}$.

Equation (1) may be rewritten

$X1 = R1 / Q$
 $X1 = 3000 / 10$
 $X1 = 300$

therefore

$X3 = 300 \text{ ohms}$
 $X4 = 12.2 \text{ ohms}$

and the total

$X1 = X3 + X4 = 300 + 12.2 = 312.2 \text{ ohms}$.

The circuit now appears as shown in Fig. 4. From this point the values of the necessary capacitances and inductances may be obtained

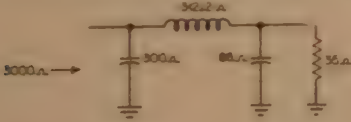


Fig. 4. Load and reactances obtained through solution of sample problem involving a quarter-wave whip antenna and a 3000-ohm plate load.

from the usual charts available in determining reactances for the particular frequency in use.

The value of 300 ohms reactance at $X1$ may be difficult to obtain. At 10 meters this is a total capacitance of approximately 18 μfd . and would consist of the tube output capacitance, wiring capacitance and the minimum value of the tuning capacitor. If difficulty is experienced the solution lies in a lower E/I ratio, or in an increase in the Q of the circuit.

The problem of matching a tube to a following grid circuit is somewhat different, as the grid circuit impedance is usually higher than the tube will want to see. Note that we can reverse the input and output values shown in Fig. 4 and make the circuit look the other way around. Thus for matching into a higher impedance from a lower one we turn the network end-for-end.

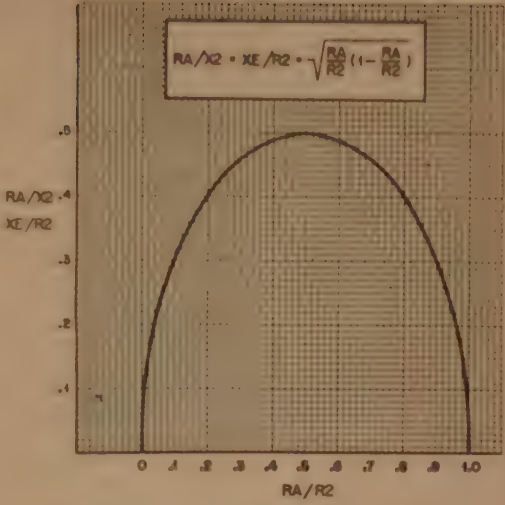


Fig. 3. This graph enables the easy conversion of $X2$ to its series equivalent Xe .

For practical purposes the grid circuit impedance is given by the approximation

$R = 600,000 (P/I^2)$

where P is the grid driving power and I is the d-c grid current in milliamperes (obtained from a tube manual).

For a single 807

$R = 600,000 (0.4/4^2) = 15,000$

If the driver tube is running at about 250 volts and 60 ma. the plate load should be

$R1 = 500 (250/60) = 2080 \text{ ohms}$

Looking from the grid back toward the plate, the circuit becomes as shown in Fig. 5. To reduce harmonics the Q must be kept fairly high but circulating currents should be kept reasonably low. A Q of 20 is recommended as a compromise.

Therefore

$Ra = 15,000 / 400 = 37.5 \text{ ohms}$
 $Ra / R2 = 37.5 / 2080 = 0.018$
 $X1 = 15,000 / 20 = 750 \text{ ohms}$

The ratio $Ra/R2$ cannot be read accurately



Fig. 5. Parameters for solution of the second sample problem. Note that the pi-network has not been turned end-for-end.

on Fig. 3, but when $Ra/R2$ is very much less than unity

$X2 = Xe = (RaR2)^{1/2}$

Thus,

$X2 = Xe = (37.5 \times 2080)^{1/2} = 289 \text{ ohms}$

The circuit is now shown in Fig. 6 with approximate reversal.

(Continued on page 66)

Easter Island Expedition

LUIS M. DESMARAS, CE3AG, CEØAA

as told to Dick Spenceley, KV4AA

Casilla 761, Santiago, Chile

At noon, August 7, 1953, I landed on Easter Island with my Ham equipment. This climaxed a three year fight to operate an amateur station from this rare spot. Four hours later and for the first time in history amateur signals were emanating from Easter Island under the call of CEØAA.

First contacts were made on phone with my friends CE3AB, CE3AG, CE3OA and CE2CC, all of whom had been diligently tuning around 14,100 kc., day and night, awaiting my appearance on the ether.


Before telling of operations, however, this story would not be complete without mentioning some of the difficulties encountered before this expedition became an actual fact.

Since 1950 I had been determined to put Easter Island on the air. Each time the yearly trip was announced I approached officials who could authorize my passage but this always resulted in a polite "brush off" as passenger accommodations on this ship are practically nil and all available space taken up with indispensable cargo such as foodstuffs, mail and other necessary items. Return trips carry produce of the Island back to Chile. One of the principal items is wool.

Towards the end of 1952 I had been lucky enough to acquire some friends who were in a position to influence my request for passage and, in that way, I was able to announce my trip which I was advised would take place some time in December, January or February. This trip



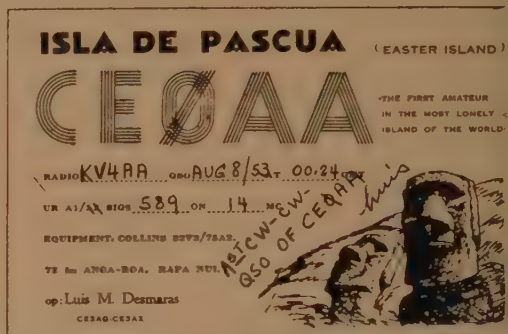Operating position at CEØAA showing the OM hard at work.



A very welcome addition to any shack!!

failed due to a decision of the government to change the administrative system of the island which, for most part, had been governed by an agricultural company for the past twenty years. This contract was terminated in December 1952 and the Government started to assemble various technicians to visit the island and render a report for future planning.

The Chilean Under-Secretary of the Navy and Engineer of Radio Communication, Commander Angle C. Lira, took charge of all operations and with a sympathetic understanding regarding the desires of amateur radio operators, put his o.k. to my application. Unfortunately the limited accommodations available precluded Armando, CE3CZ, who had planned to accompany me.

In March, 1953 notice was given to all concerned that the Naval Transport "ANGAMOS" would be leaving Valparaiso on April 10. Later another notice was received advising that the trip would be postponed until the end of May. As you know, we did not leave in May, or June, but finally got underway on the 24th of July. This date is near the middle of Winter in the Southern Hemisphere and this fact did not add to our comfort. After a two day stop at Juan Fernandez Island, better known as Robinson Crusoe's Island, where passengers and supplies were dropped, we proceeded on our way. Several days before reaching Easter the 4,500-to-high seas which we grimly endured.

It was my intention to put CEØAA/MM on the air during this voyage, but fearing something

would go wrong with the equipment, which would nullify all my past efforts. I spent my time zealously guarding the transmitter which was lodged in a special baggage compartment.

Concerning Easter Island

Now a brief word about Easter Island itself. This island, with an area of 65 square miles, is well known for its mysterious stone monuments or "moais" built thousands of years ago by a now extinct race. There are about 800 inhabitants of which twenty are white and the rest are of Polynesian origin. The natives are extremely kind, affectionate and hospitable. They are strongly built and of good intelligence. They speak the Rapa-Nui language but the majority are familiar with Spanish.

Upon sighting Easter we were forced to circle the island for 36 hours waiting for the wind to subside and the seas to calm sufficiently to permit before a landing to be made. This reduced me to a nervous wreck as it was impossible to get any sleep a condition which was certainly not conducive to the Ham radio operation that followed. The landing was eventually made and in a few hours I had set up the transmitter, receiver and electric plant at the house of my friend, Urbano, as previously arranged. A multiband antenna, 66 feet long, was put up with one end thirty feet high and the other fifteen. After checking everything for proper operation I tuned on 14,100 kc. and, with great emotion, heard the signals of CE3AB, CE3AG and others who were standing by.

First Contact

At 2308 GMT (1608 local time), August 7th, I called CE3AB and immediately established contact for the first QSO from Easter Island. Contact with my own station, CE3AG, operated by CE3DG, followed and I was able to speak with my family and assure them that all was well. QSO's with CE2CC, CE3MJ, PY3DZ, CP5EK and LU7TA followed in quick succession. I had been on the air barely forty minutes when, to my surprise, I heard CW signals calling me. Among them I was able to identify W6GDJ whom I came back to, on phone, for the first W contact at 2349 GMT. A QSO with W6RW followed and then I hooked PA0UN for the



Luis by the side of Hotumatua monument. According to legend, Hotumatua was the founder of the race actually living on the island.

first European contact. Next, W2AGW came through for the first phone-to-CW W2 contact. Later I learned that these CW calls were a result of a QST by CE3DG on 14,005 kc. informing the gang of my whereabouts. At 0024 GMT I tuned the 32V-2 to 14,001 kc. and, with great satisfaction, contacted KV4AA for the first CW to CW QSO. This was rapidly followed by contacts with W6SAI and K2EDL (ex-W6IBD). In that way I had started the CW ball rolling and there was very little rest for me from then on.

Ten minutes on this frequency had precipitated an avalanche of W calls with all signals between 579 and 599.

After eight hours of operation 165 contacts had been made and every W district had been worked. First contacts in each district were as follows: W1RY, W2AGW, W3EVW, W4CEN, W5NW, W6GDJ, W7PGX, W8WZ, W9NDA and W0NWX. At that point the need for sleep overcame me and I QSB'd into a much needed rest.

The next days of operation resulted in 271 contacts on CW and phone with North America, South America, Europe and Oceania. Conditions favored ZL and VK contacts on 3.5 and 7 Mc. and many were made.

The Record of QSO's

Nothing short of remarkable were the propagation conditions existing between CE0AA and W-land. There were only very short periods during the entire day when W's could not be heard. During these periods nothing else could be heard either. Thus, W, VE and Central America Hams reaped the biggest harvest of Easter Island contacts.


Of the 1538 QSO's made; 996 were W's, 108 were LU's, 97 were CE's, 68 were G's, 36 were



Start of the expedition: Luis follows the transmitter up the gangway.

(Continued on page 55)

Commentaries

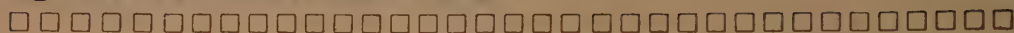

A Department of Constructive Suggestion

Do you have some ideas that you have never been able to follow through to completion? In working on one project did you accidentally uncover another interesting fact that might be up someone else's alley? Would you like to get some more ideas on how to approach a problem and at the same time see if anyone else has taken a crack at it?

If so, the answer is "Commentaries" a place to discuss your experiments, ideas or gimmicks. "Commentaries" is designed to fit the need for a place to publish material that does not exactly merit feature billing, or which is not specific, or short enough to be of use in the "Shack and Workshop" department.


All items used are paid for and contributions should be directed to "Commentaries," c/o CQ Magazine, 67 West 44th Street, New York 36, N.Y.

Mobile Installation Briefs

Loading Coil Protection

While stationed at the Camp Pendleton, California, Marine Base, the salt-laden atmosphere quickly ruined the metal cans over my mobile antenna loading coils. Therefore, I replaced them with polystyrene covers as illustrated in the first picture. To do so, I obtained a length of polystyrene tubing approximately the same diameter as the old can, and a piece of 1/4-inch flat stock.

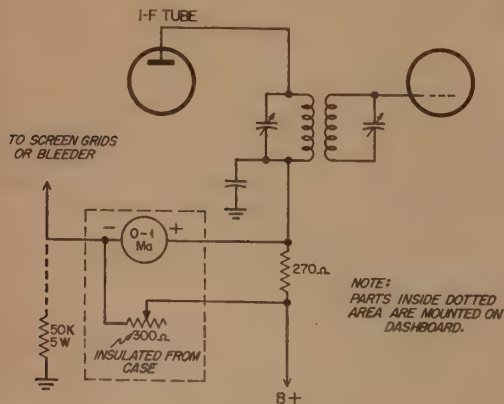After cutting the tubing to a length to cover the coil, I cut a piece from the flat stock on a bandsaw to fit over the end of the tubing. Next,



WIKYK S-meter circuit.

I drilled a hole in its center to pass the antenna stud before cementing the two pieces together. I used *Duco* household cement, but regular polystyrene cement should work at least equally well.

Naturally, it was necessary to readjust the loading coils after changing the covers.

Mobile Receiver S-Meter

I certainly missed not having an S meter on my mobile receiver. The second picture and the diagram (Fig. 1) illustrated how I remedied this. I used an S-meter salvaged from an old *National* receiver, but any meter with a one milliampere movement will serve equally well.

I mounted the meter and the "zero-adjust" resistor in a discarded metal box, which happened to have a hole in one end just the right diameter to accommodate the meter. I then mounted the assembly under the automobile dash board. A three-wire cable connects the meter into the automobile receiver.



Polystyrene loading coil cover designed by WIKYK to replace a corroded metal cover. Incidentally, there is considerable evidence that removing the cover improves radiation efficiency.



The dash mounted S-meter.

A bridge circuit is used to produce a forward movement of the meter pointer with an increase in signal strength. It is connected in the high-voltage lead of any tube in the receiver controlled by the a-v-c circuit. The B+ lead of one of the i-f tubes is a logical place to connect it.

The terminal marked "screen grids or bleed er" may be used to supply the screen voltage (through dropping resistors) for the r-f and i-f tubes in the receiver, or it may be grounded through about a 50,000-ohm, 5-watt resistor.

Transmitter Rack

The third picture shows the small rack I installed in the trunk of my 1952 Ford, to accommodate the mobile transmitter, modulator, and power supply and still leave room in the trunk for other purposes. It is constructed of angle iron salvaged from an old Army bunk. The side pieces are drilled and tapped for 10-32 screws to accept standard relay rack panels. The holes are spaced alternately $\frac{1}{2}$ -inch and $1\frac{1}{4}$ -inches apart, center-to-center, vertically, and $18\frac{1}{4}$ inches apart horizontally.

The rack top fits into a groove across the top of the trunk hump, and screwing the shock



This home constructed rack mounted in the trunk compartment easily accommodates the mobile modulator and transmitter.


mounts on the side pieces and the diagonal braces to the floor of the trunk produced a rigid installation unaffected by vibration.

Norman Gertz, W1KYK

The Question of a High-Angle Radiator

A few years ago I was struggling away in Virginia trying to compete in the CD Party and Sweepstakes with W4KFC and some of the other boys in the Potomac Valley Radio Club. As far as I could determine, my results on contacts beyond about 500 miles were as good as those of any of the other locals. Inside that 500-mile radius I just didn't seem to be laying down any type of signal.

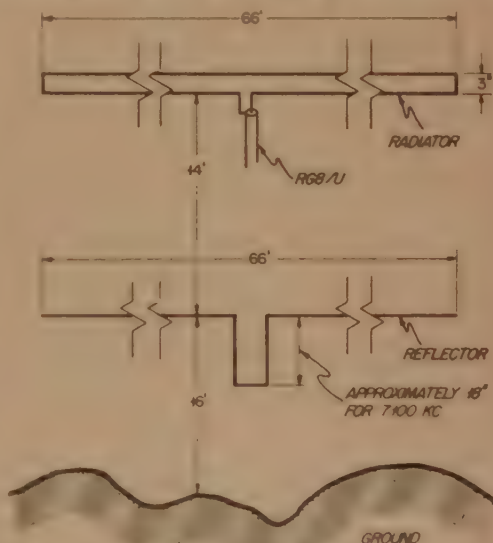Examination of the one-hop F2-layer transmission nomograms indicated that angles of radiation between 35 and 85 degrees were called for. My verticals were radiating most of their stuff well below 30 degrees. Drawing that 500-mile radius on a map quickly convinced me



Mounting a reflector under the antenna.

that plenty of contest customers were being passed up (unintentionally) and a good high angle radiator was needed.

Getting away from the trend towards verticals, my first antenna was a horizontal end-fed wire, 134 feet long and averaging about 30 feet above ground level. It was somewhat better, but not what I had in mind as being satisfactory. The trouble appeared to lay in the poor ground under the antenna which rose and fell from 20 to 60 feet below the antenna as it wandered through the pines.

Waynick and Hacke¹ have shown from a

Continued on page 69

1. J. E. Hacke and A. H. Waynick, "Restricted Range Sky Wave Transmission," Proc. I.R.E., vol. 36, #6, June 1948, p. 787.

DX



AND OVERSEAS NEWS

Gathered by **DICK SPENCELEY, KV4AA**

Box 403, St. Thomas, Virgin Islands, U. S. A.

We welcome the following newcomers to the **HONOR ROLL**

W2QHH	39-219
W6KYG	37-200
W6YK	37-144

At Time of Writing

COCOS ISLAND, TI9: W6UXX is presently on another trip which should put him in the vicinity of this QTH around November 1st. Evan feels that his chances of getting on the air this time are good. There will be other chances to get Cocos off your chest as TI2TG advises the possibility of two treasure expeditions coming to pass sometime between November and February. TI Hams who may go along include TI2AB, TI2RC and TI2ES. On top of this we quote an item from the West Gulf Bulletin of Aug. 22nd: "The West Gulf DX Club has tentative plans for a DX-pedition to TI9, Cocos Island, at the end of the present rainy season, probably some time during the month of December. Present plans are for at least two members to go down to Costa Rica and be joined with at least two TI2's. Contributions are requested to help assist in the jaunt and will be published in the Bulletin from all members as well as those not in the Club. All calls contributing will be given special consideration for contacts while there which will be from ten days to two weeks. So boys, get on the band wagon and let's go. Contributions should be sent to W5FXN and marked "For the TI9 expedition."

ANDORRA, PX1: W6SAI advises via letter from PX1YR that Yves has now been officially licensed after passing his code examination and has expressed a liking for CW. He will run 80 watts to a folded dipole.

• • •

RUDOLPH ISLAND, UA: OKIMB reports a UA station will be active from a weather station from this QTH, near Nova Zemlya, and has been seeking permission to contact W stations. The country status of this spot has not been determined.

• • •

ZANZIBAR, MAURITIUS, NYASALAND, G2RO/VQ1RO/VQ8AY/ZD6RO: Bob Roberts reports on his recent activities at these spots as follows: "In VQ1RO I had a fine time as I was able, for one night, to use an antenna supported by two 200 foot masts. A couple of hundred W stations and many other countries were contacted. W's were worked at the rate of one every 20 seconds! Operation at ZD6RO was a disappointment due to poor QTH and only 27 contacts were made, one being a starting KG6. A few W's were QSO'd using the call of VQ8AY. Among them were W5MET and W1HX. Operations at VQ2RO were fair but no W contacts were made due to very poor conditions in that direction. Due to transportation weight limitations I had to

(Continued on page 32)



As the only Ham station on IWO JIMA, KAØIJ, is kept plenty busy with state-side traffic. The rig is housed in the trailer seen above and consists of a BC-610 transmitter and Super-Pro receiver. Ops. Capt. Tex Crayton and Bill Cierebeij are shown in the left photo with Tex in the operating position. Antenna is a V-Beam.



Right—Well known on the bands is WSMET, Dick Kemp, of Rogers, Ark. Dick alternates between WSMET and WSMET MM. The home rig runs 300 watts to an 813. First licensed in 1932 as W9LZO, Dick has also held the calls of W8QJN and W3IWK.

Center—KV488, the source of those potent phone and CW signals from St. Croix, Virgin Islands, is operated by Bill Thomas, ex-W4CG. Bill's first crack at the ARRL phone contest netted him a score of 176,080 which was "tops" for stations outside of W and VE. Yep, Bill runs a kw, and has the usual assortment of rotary beams.



Right, below—No chair can hold Warren Newcombe, W6WYC, when those rare W7's come pounding in!!

Signals from EA0AB, Spanish Guinea, get a big boost from the rotary beam pictured below. The OM, Angel Garcia Margello Barbera Esq., is seen here getting a birds-eye view of the photographer. Photo Courtesy of W4RBQ.



(from page 30)

borrow a receiver at each QTH visited. While these have always been available some have been in very poor condition and I have been considering the construction of a lightweight TRF battery receiver (90v/1.5v) to cover 14 Mc. only." G2RO will visit many rare spots in the next year and a half and he pleads that all contacts be of the "contest type" variety limited to a simple RST report. The occasional W station who insists on holding him for no good reason ruins the chances of many others. Request for "Please listen for my phone" will be ignored. Bob will arrive in New York in Mid-November and will next be heard from the West Indies. You will be kept informed of all his future moves.

• • •

AR, MP4: MP4BAU showed up on 026 2215 GMT QSO'ing W5AVF. We take it that Adi now has his new CW rig going and we look forward to plenty of activity from him. For Qatar phone contacts watch for MP4ABW 110/190 kc.

• • •

CAMBIA, ZD3/TIMBUKTU, TU2: from PA0UN and G3AAM we hear that Jim, ST2UU, is considering a trip to these spots in late September or early October. This appears to be a change of plan which formerly included Yemen in the itinerary. These QTH's are not definite, but, knowing Jim, we expect him to show up somewhere! The TU2 prefix was mentioned but Timbuktu apparently comes under the FF8, French Sahara, call. Some activity from Gambia would be very welcome.

• • •

JAN MAYEN, LB5/6/8: LB8YB has now moved from Myggbukta Island, off Greenland, and is now very active from Jan Mayen. He may be found on 7020 kc. QSO's were noted with W6CGQ, W6RW, VE2WW and W6KYG around 0145 GMT. It will take a year for QSL's to come through.

• • •

NICOBAR ISLANDS, VU5: VU5AB has been active from this spot on phone. Watch 14190 kc. around 1500 GMT. See QTH's.

• • •

RIO DE ORO, EA9: EA4BH confirms his intentions to be on from this country for a two weeks' stay which should have started about October 20. The trip of EA2CN/EA2CA to this spot may also have been heard from by now.

• • •

RUANDA URUNDI, OQ0: Furthering our efforts to have this QTH separate we have just received the following letter, long awaited, from the Belgian Society, U.B.A.:

"I am at present able to confirm officially that the Ruanda-Urundi Territory, Prefix OQ0, may be considered as a separate radio country. It has been long and tedious working to convince certain authorities that

this measure has no political significance, but now everything seems clear at last. I apologize for the long delay, but you will understand that we had to have the consent of all authorities concerned before giving this confirmation. We hope that this will result in numerous contacts for the lucky few amateurs installed there, and many points for numerous fellow amateurs all over the world. 73

(Sig) Jos Mussca
President, U.B.A.

Presently active in Ruanda-Urundi are OQ0CZ, O5O CW, and OQ0DZ on phone. It is also reported that W6TOT will soon be active in this area as OQ0FZ. We have forwarded the above data to ARRL in hopes that a formal announcement accepting Ruanda-Urundi will soon be forthcoming.

• • •

AMIRANTE ISLANDS, VQ9UU: G2MI advises that this group falls, administratively, under the Seychelles group and thus VQ9UU's operation there on August 11 will probably cover the same as a Seychelles QSO. This will be looked into further.

• • •

DX NOTES IN GENERAL

KS6AB has been active on 065 around 0200 GMT. ISLV holds forth on 060. See QTH's. . . VK9WZ has been on from the Admiralty Islands. He counts it same as New Guinea. Watch 7030 and QSL via W.I. . . . Another SV0/Crete visit was rumored for Sept. but no signs up to Sept. 16th. . . The DI9AA we have been hearing with a very chirpy and drifting QRI is the German ship "XARIFA" of the Hans Hass underwater photography expedition. All communication depends on DI9AA on the 3.5, 7 and 14-Mc. Ham bands. (Via W. Gulf Bulletin) . . . Dick McKercher, HZIMY etc. is not back in the states where he hopes to be heard short from W0MLY. See QTH's. . . CR8AB, the son of CT1CB, is in Portuguese India, but his gear is still Portugal. Has anyone any solid dope on CR8A? . . . W5NMA reports KC6AA, Yap Island, active on phone xtl 14228 plus VFO while W5ALA overheard W6TM working VR6AC, Pitcairn Is. 002, Aug. 11. . . W0EID nabbed FUSAA, 064, 0855 GMT while FW8AB, Wal. Is., has been heard several times by VR2CG and QSO'ed by ZL3JA on 105. . . G3AAM reports contacts with KA0IJ, A3, 14270 at 0930 GMT and with VR4AE, 04 at 1200 GMT. . . DL4JN nabbed Saja, AC3SQ, 080 1430 GMT. . . ZC5VS is active again after a layoff as may be heard on 079 between 1300/1500 GMT. . . CR5AC holds forth on xtl 008 (drifts to 011) most days around 1930 GMT while HR1AA may be heard, concentrating on European QSO's, 006, 2230 GMT and later Jack should be settled in new QTH in Tegucigalpa now with new beam antenna. He says QSL via HR1A. . . F3AT, ex-FF8AP, is plenty active in F-land now. Iva says he may go to FL3 in a couple of years. . . KX6U plans to move to Truk, using KC6UZ, for an extended stay. . . Henry JZ0KF, continues activity from Dutch New Guinea, 083, 0335 GMT. ARRL is holding a bunch of QSL's for him. . . Plenty of activity emanates from Argentine Antarctica through the efforts of LU4Z, LU3ZO, LU5ZO, LU3ZS and LU4ZD. This is embossed! VP8AJ on 008. . . TA3AA (via W9RRG) wishes known that he is again active on all bands during weekends and holidays. . . A number of EA9DC QSL's have been coming through thanks to the efforts of EA4B. . . The Russian situation remains foggy. UR2M showed up on Aug. 26, 095, QSO'ing everything in sight. UG6KAA was heard calling CQ DX and UA0KK was heard calling VS6CG. We have a couple of people who intend to QSO UA3KAA, Central Radio Club, Moscow, and try to get the real lowdown. KV4AA QSO'ed UA3AF who gave QTH as Moscow and all seemed to be the up-and-up. . . FK8AE has been QSO'd on 7020 0900 GMT. He also appears on 030.

Exploits

G6ZO upped to an imposing 247 with CE0AA, VQ7U and VQ9UU while W2BXA added the same three.

(Continued on page 52)

Amplitude Modulation Review

A Down-to-Earth Discussion of Modulation Efficiency with Plate Modulation in One Corner and the Various Types of Constant or Controlled-Carrier Screen Grid Modulation in the Other

G. FRANKLIN MONTGOMERY, W3FQB


Contributing Editor, CQ

Planning a new phone transmitter, either for mobile installation or for the home station, nearly always involves deciding whether to use plate modulation or one of the several available types of screen-grid modulation.^{1-8, 17} Both have advantages, and the choice between them depends upon equipment already on hand and upon the goal of the planner. The technical object in building a transmitter is to construct a device that will convert d-c power obtained from batteries or a power supply to radio-frequency power, and there are occasions when we are interested in the efficiency of this conversion. For example, if the plate supply is limited, as in a mobile setup, which modulation method gives the greatest efficiency? If a particular final amplifier tube is to be used, which method gives the greatest power output? In view of the large number of published articles on modulation schemes, it is understandable that there is some confusion in response to questions like these, and it is the purpose of this article to compare the merits of plate and screen modulation in order to furnish some clear answers. The discussion will be limited to ordinary AM omitting single-sideband technique, and will begin with constant-carrier transmission, reserving controlled-carrier refinements until later.

Constant Carrier

Plate modulation is one of the oldest methods used by amateurs to effect radiotelephony. The

final amplifier, operating class-C, is supplied with plate power from two sources in series, the d-c plate supply and an audio power amplifier (Fig. 1). For 100-per cent modulation, the audio amplifier, called the modulator, must be able to supply sine-wave output power equal to one-half the d-c power drawn by the final amplifier from the plate supply. When the class-C final is properly operated, it presents a constant, resistive load to the modulator, and the total plate voltage and plate current supplied to the final are directly proportional to each other at all points of the audio cycle. Because of this proportionality, the instantaneous power input to the final is proportional to the square of either the instantaneous plate voltage or current. The efficiency of the final amplifier, i.e., the ratio of radio-frequency

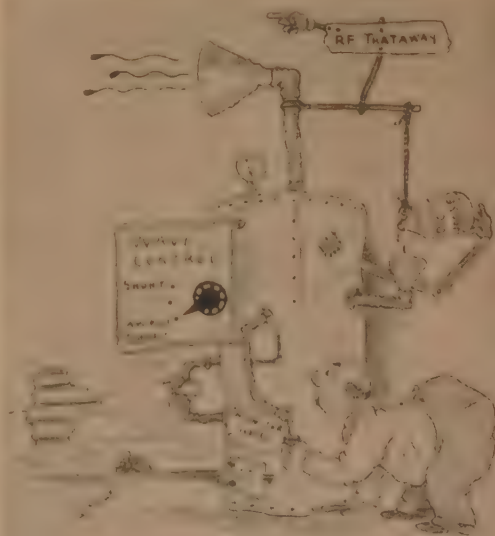

1. Byron Goodman, "Clamp-Tube Modulation," QST, March 1950, p. 48.
2. George R. Lippert, "A 'Constant-Modulation' 'Phone System,'" QST, April 1950, p. 44.
3. G. K. Hickin, "Improved Clamp-Tube Modulation," CQ, July 1951, p. 24.
4. Richard M. Smith, "Screen-Grid Modulation of the Modern-Style 813 Transmitter," QST, October 1951, p. 38.
5. John L. Reinartz, "Screen and Grid Modulation," CQ, December 1951, p. 43.
6. Byron Goodman, "The Rothman Modulation System," QST, January 1952, p. 56.
7. Max I. Rothman, "Rothman System of Modulation," CQ, April 1952, p. 21.
8. C. O. Bishop, "A System of Gating Modulation," CQ, October 1952, p. 19.

"The...object...is to construct a device that will convert d-c power...to radio frequency..."

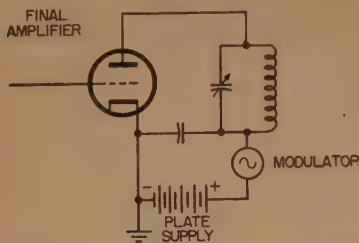


Fig. 1. Basic schematic for plate modulation.

power output to instantaneous plate power input, is constant, regardless of what the instantaneous input power may be. We can regard the class-C final as simply a convenient device for converting the power that it consumes to radio-frequency power, and it is immaterial whether the supplied power is audio or d.c.; both are converted with the same efficiency.

Contrast this situation with screen modulation (Fig. 2). Once again, the final amplifier is operated class-C but receives plate power; at a fixed voltage, only from the d-c plate supply. The output of the audio amplifier, or modulator, is applied in series with the supply to the screen grid, and since the final plate current depends upon the voltage of the screen, the plate current will vary with the audio voltage. The power consumed by the screen grid is much less than that consumed by the plate, so that the audio power output of the modulator need be only a small fraction of the power that would be necessary to plate-modulate the same final. For ideal operation, the plate current is directly proportional to the instantaneous screen voltage, and, since the plate supply voltage is fixed, the instantaneous plate power input to the final is also proportional to the screen voltage. For linear modulation,^{3,9} however, the radio-frequency power output must be proportional to the square of the plate current, as in the plate-modulated case. In consequence of this requirement, the instantaneous efficiency of the final amplifier also must be proportional to plate current.^{10, 11, 17} In screen modulation, therefore, we can again regard the class-C final as a device for converting d.c. to radio-frequency power but with the distinction that it does so with an efficiency proportional to the power that it consumes. (Note further that, except for minor differences in the amount of audio power required of the modulator, the same operating principles apply to control-grid or suppressor modulation.)

Considering the general principle that one does not get something for nothing, plate modulation and screen modulation are not as different as they may appear to be. In plate modu-

lation, it is first necessary to generate considerable audio power at only moderate efficiency and then to convert it to radio-frequency (that is, sideband) power by supplying it to the class-C final. In screen modulation, the average efficiency of the class-C final is low because of the requirement that instantaneous efficiency be proportional to plate current, but since it is unnecessary to generate large audio power to begin with, nothing much has been lost in the process. We can regard screen modulation as a method of using a relatively large radio-frequency amplifier to perform the functions of an ordinary plate-modulated final and modulator combined. There are still differences in the two methods, however, and it is our purpose to examine the differences more carefully.

With constant-carrier operation, the effectiveness of the transmitter increases with the



"In view of the large number of published articles on modulation . . . there is some confusion . . ."

strength of the transmitted carrier, and it seems fair to compare systems on the basis of the carrier power that a given power supply can produce. Accordingly, we choose to calculate the *overall carrier efficiency*, that is, the ratio of carrier output power to the total d-c plate power supplied to the final and the modulator when the carrier is modulated 100-per cent by an audio sine wave. If we let P_o represent the carrier output power and P_p the d-c plate power, then the overall carrier efficiency is

$$E = \frac{P_o}{P_p}$$

Let us see what this efficiency turns out to be for several different choices of modulator.

Plate Modulation

Plate modulation involves two efficiencies, the efficiency of the class-C final and the modulator

9. George Grammer, "Some Facts of Modulation," *QST*, March 1951, p. 49
10. George Grammer, "Some Aspects of Screen Modulation," *QST*, November 1951, p. 41
11. Frank C. Jones, "Some Experiments with Screen Grid Modulation," *CQ*, January 1952, p. 13

efficiency. Remembering that the modulator must supply an audio output power equal to one-half the d-c power supplied to the final, we can calculate the total d-c plate power as

$$P_s = \frac{P_o}{E_{ef}} + \frac{P_o}{2E_m E_{ef}}$$

where E_{ef} is the class C final efficiency, and E_m the modulator efficiency. The first term in the sum is the d-c power supplied to the final, and the second term is the d-c power supplied to the modulator. The equation can be rewritten in the form of the overall carrier efficiency

$$E = \frac{P_o}{P_s} = \frac{2E_m E_{ef}}{1 + 2E_m}$$

Now let us assume some typical efficiencies for the different classes of amplifiers. The final, of course, will be operated class-C; the modulator may be either class-A or class-B. If we assume a working efficiency of seventy per cent of the maximum theoretical efficiencies for the three classes of amplifiers,³² and allow a small additional amount of plate power for the modulator driver in the class-B case, then the efficiencies are

$$E_m \text{ (class A)} = .35$$

$$E_m \text{ (class B)} = .50$$

$$E_{ef} \text{ (class C)} = .70$$

When a class-A modulator is used, the overall carrier efficiency is, then,

$$E \text{ (class A)} = \frac{2(.70)(.35)}{1 + 2(.35)} = .29$$

and for the class-B modulator,

$$E \text{ (class B)} = \frac{2(.70)(.50)}{1 + 2(.50)} = .35$$

These overall efficiencies mean, simply, that for every 29 watts of carrier output, 100 watts of d-c plate power must be supplied when a class-A modulator is used; if a class-B modulator were used instead, 100 watts of d-c power would be efficient to provide 35 watts of carrier.

Screen Modulation

Screen modulation involves only one efficiency, that of the final amplifier itself, but we have seen that this efficiency changes with modulation. The peak efficiency of the final under modulation will be the same as the constant efficiency of the same final if it were plate modulated; the efficiency of the final with no modulation is one half of this figure. If we allow an additional five per cent of the supply power for the screen modulator tube itself, then

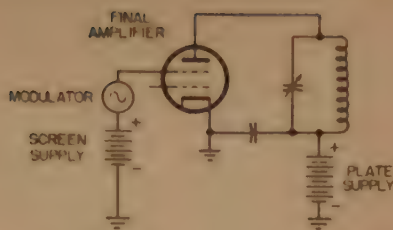


Fig. 2. Basic schematic for screen-grid modulation.

$$P_s = (1.05)2 \left(\frac{P_o}{E_{ef}} \right)$$

and

$$E = \frac{P_o}{P_s} = \frac{E_{ef}}{2.7}$$

If we assume, as before, that $E_{ef} = .70$, then

$$E \text{ (screen)} = 0.33$$

which means that 100 watts of plate supply will produce 33 watts of carrier.

Examination of the three overall carrier efficiencies shows that there is really very little reason to choose between plate and screen modulation from the efficiency standpoint, and the choice must therefore be made on other grounds. How about final plate dissipation? The discussion at the beginning makes it plain that if we are to use screen modulation, and therefore require the final amplifier to act as r-f generator and modulator combined, the tube itself must be somewhat larger than is needed otherwise. How much larger must it be?

Plate Dissipation

The plate dissipation of a plate-modulated final is maximum with full modulation. The average input to the final with full modulation is one and one-half times its d-c power input, and the power dissipated at the plate, P_d , is simply that fraction of the input power that does not appear as useful r-f output, or, in terms of the carrier output power,

$$P_d = (1.5) \frac{(1 - E_{ef}) P_o}{E_{ef}}$$

If E_{ef} is .70 as before, then

$$P_d \text{ (plate mod.)} = (1.5)(.30) \frac{P_o}{0.70} = 0.64 P_o$$

which means that the plate dissipation is 64 per cent of the carrier power.

One of the odd consequences of the variable-efficiency characteristics of screen modulation is



"Plate modulation is one of the oldest methods..."

the fact that maximum plate dissipation occurs with no modulation; the plate cools off when modulation begins (we are still assuming constant-carrier operation). The power dissipated at the plate is, again, that portion of the plate input power that is not converted to useful output, or

$$P_d = \frac{(1-E_{rf}/2)P_o}{E_{rf}/2} = \frac{(2-E_{rf})P_o}{E_{rf}}$$

where the factor 2 appears because the carrier efficiency, as before, is only one-half the peak class-C efficiency. If $E_{rf} = .70$, then

$$P_d \text{ (screen mod.)} = 1.30 \left(\frac{P_o}{0.70} \right) = 1.86P_o$$

or, the plate dissipation is 186% of the carrier power. As a matter of curiosity, let us calculate the plate dissipation for 100 % sinusoidal modulation. For these conditions, it turns out that the average efficiency is exactly 75% of the peak efficiency E_{rf} , the extra 25% being due to the production of r-f sideband power. The plate dissipation, then, is

$$\begin{aligned} P_d \text{ (screen, full mod.)} &= \frac{(1-3E_{rf}/4)1.5P_o}{3E_{rf}/4} \\ &= \frac{(4/3-E_{rf})(1.5)P_o}{E_{rf}} \end{aligned}$$

For $E_{rf} = .70$,

$$P_d = 1.36 P_o$$

or 136 % of the carrier.

Constant-Carrier Comparisons

We are now in position to construct tables giving typical operating data. Table 1 assumes that we have available for the final stage and modulator a source of d.c. at 450 volts at 100 milliamperes, or 45 watts, and shows the

TABLE 1. SUPPLY POWER $P_s = 45$ WATTS		
MODULATOR	FINAL PLATE DISSIPATION P_d (WATTS)	CARRIER POWER OUTPUT P_o (WATTS)
CLASS A	8.4	13
CLASS B	10	16
SCREEN	28	15

required final plate dissipation and the carrier power output that can be expected using either plate or screen modulation with constant-carrier transmission. Table 2 assumes instead that we have available for the final a tube rated at 15 watts plate dissipation (such as the 2E26) and

TABLE 2. PLATE DISSIPATION $P_d = 15$ WATTS		
MODULATOR	TOTAL d-c POWER INPUT P_s (WATTS)	CARRIER POWER OUTPUT P_o (WATTS)
CLASS A	73	21
CLASS B	60	21
SCREEN	22	7.3

shows the expected carrier output and the total d-c power input required, including power supplied to the modulator, when the final stage operated at its maximum rated dissipation.

Controlled Carrier

A method that has recently regained popularity, particularly in connection with screen modulation, is controlled-carrier operation.¹³ The concept of controlled carrier is a simple one. The modulating speech wave of voice transmission is not a constant-amplitude wave and consequently the modulation of a constant carrier averages considerably less than 100 per cent. In practice, if the speech wave is undistorted and if the modulation reaches 100 per cent only on voice peaks, the average modulation will be only 20 to 25 per cent. With such a low modulation percentage, transmission of a full, constant carrier represents wasted power because the full carrier is really necessary only during those short intervals when the speech wave attains its maximum amplitude. Carrier control is a method whereby the amplitude of the carrier is maintained just sufficient to accommodate full modulation; when the amplitude of the speech wave is small, the carrier level is low, and so on. The circuits used to effect this control of the carrier are various—2, 6, 7, 8, 13, 14, 15, 16, but in principle they all operate by substituting a special modulating vo-

13. George Grammer, "Screen Modulation with Limited Carrier Control," *QST*, April 1951, p. 64
14. Donald H. Mix, "Carrier Control with Self-Biasing Clamp-Tube Modulator," *QST*, November 1952, p. 16
15. Frank C. Jones, "Further Experiments with Screen Modulation," *CQ*, December 1952, p. 17
16. Jose A. Vivares, "Controlled Carrier with a Cathode Follower," *QST*, September 1952, p. 15
17. W. L. Orr, *RADIO AMATEURS' MOBILE HANDBOOK*, Cowan Publishing Corp., New York, 1952, pp. 79-83.

age for the ordinary audio output of the modulator. This special voltage consists of the regular audio output in series with a slowly varying d-c voltage whose amplitude is equal to (or slightly greater than) the peak amplitude of the audio. The d-c voltage cannot be allowed to change as rapidly as the variation in the audio wave itself, or severe modulation distortion will result. Instead the d-c voltage, while it may build up rapidly at the beginning of a burst of speech, must necessarily decay rather slowly. Its action is quite similar to that of the b-c voltage in a receiver; it responds to the variations in the peak amplitude of the audio waveform averaged over some small interval of time, in much the same way that the a-v-c voltage responds to variations in the peak amplitude of a received rf signal.

The saving in average carrier power that is obtained in controlled-carrier operation can be used to generate a transmitted signal having greater peak power during modulation than would be possible with the same final as normally operated. If there is no distortion, intentional or otherwise, in the speech wave that is used for modulation, the ratio of peak power to average power is about 12 to 15 db. The plate dissipation of the class-C final depends, of course, on the average power input, so that controlled-carrier operation, with undistorted speech, will permit operation of the final at higher peak inputs as long as the maximum voltage and current ratings of the tube are not exceeded. If we take the peak-to-peak power ratio as 12 db., then we would expect that carrier control, with plate modulation, should allow us to transmit an effective signal power sixteen times that of a constant-carrier transmitter. But there is a limitation here, because the generator of large peak power requires high supply voltage on the final. A power increase of sixteen times requires that both peak plate voltage and peak plate current be increased by a factor of four relative to the constant-carrier conditions and there are few tubes, obviously, that will withstand such an increase within

their ratings. Usually we cannot expect to increase the plate supply voltage of the final to much above its maximum rating for plate-modulation service. The conclusion, for plate modulation, is that controlled-carrier operation offers little practical advantage except, of course, that the average d-c power consumption of the final may be reduced considerably for the same peak-modulation carrier output.

The situation is somewhat different for screen modulation. Since the final plate voltage in this arrangement is fixed, we can generally operate the final with a plate voltage about twice its maximum c-w rating. This increase in itself would yield a peak power no greater than that obtainable from the same tube in plate-modulated service, but with constant-carrier operation and screen modulation it is usually impossible to run the final this hard without exceeding its rated plate dissipation (see Table 2). If we again assume a difference of 12 db. between peak and average levels of the modulation waveform and assume that the low-level modulation can be represented approximately by a sine wave, then the plate dissipation for controlled-carrier screen modulation is, approximately,

$$P_d = \left[\frac{(1-3E_{rf}/16)}{3E_{rf}/16} \right] \left[\frac{(1.5)P_o}{16} \right] = \left[\frac{(16/3-E_{rf})}{E_{rf}} \right] \left[\frac{(1.5)P_o}{16} \right]$$

where P_o is the carrier output for peak modulation. The average carrier output is one sixteenth of P_o . If E_{rf} is .70, then

$$P_d = 0.62 P_o$$

This dissipation figure of 62% of the peak-modulation carrier power compares favorably with the 64% value that we have found for constant-carrier plate modulation and shows that carrier control in screen modulation permits use

(Continued on page 67)

"... There is ... little reason to choose between plate and screen modulation from the efficiency standpoint ..."



The

Mail Order Antenna

A 40-Meter Vertical for the Space Starved Amateur

R. W. JOHNSON, W6MUR

1202 Avoca Avenue, Pasadena 2, California

Getting a 7-Mc ground-plane antenna on a small city lot can be quite a problem. After all, a 32 to 36 foot antenna does not stand up by itself, unless it is made of some special (and usually expensive) material. The little matter of erecting a guyed "whip," without breaking it in half in the process is also something to consider. Then, there is the base insulator, as well as the location of the radials, to worry

about. The radials are around thirty-five feet long too, you know.

The "Sears-Roebuck Special" eliminates or avoids most of these problems. Its evolution began upon noticing in a *Sears* catalog that aluminum irrigation tubing, with 0.050-inch walls, was listed in twenty-foot lengths and in diameters of two, three, and four inches, at a cost of \$4.85, \$6.75, and \$8.95, respectively.¹ I ordered a length of each of the larger sizes.

The tubing proved to be very rigid, therefore, I joined the two lengths together in the manner shown in Fig. 2. First, I cut four pieces of plywood, 48 x 3/4 x 1/2 inches, to use as spacers between the two pieces of tubing. After dressing them down to fit, I wrapped them with thin flashing material (*Sears* "Valley Roll," 0.19 x 14 inches—\$2.38 for a ten-foot roll), so that they would become conductors.

Next, I telescoped the two lengths of tubing together for four feet, with the aluminum-sheathed wooden strips evenly spaced between them. The assembly is held together by six 3/4-inch threaded rods (Cut from *Sears* "Redi-Bolt Rod"—sixty-five cents for a three-foot length) completely through tubing and spacers, three in one direction and three more at right angles to them. Nuts and washers on the rods and some strong-arm work with a pair of wrenches finished this part of the job.

The complete 36-foot length weighs twenty-eight pounds, and when held horizontally from one end, the sag is just discernible.

Installation

I dug a hole four feet deep in which to set the antenna with a standard post-hole auger. It

Looking up from the base of W6MUR's vertical. The small diameter tube on the left is the matching section. It is ten feet long, one inch in diameter and four inches from the radiator.

1. Not all *Sears* catalogs list this tubing, which is described on page 842 of the spring-summer, 1953 edition (No. 206) of the catalog distributed in the Los Angeles area. If not listed locally, it can be ordered from: *Sears*, 925 South Homan St., Chicago 7, Ill. It is also available from other sources.

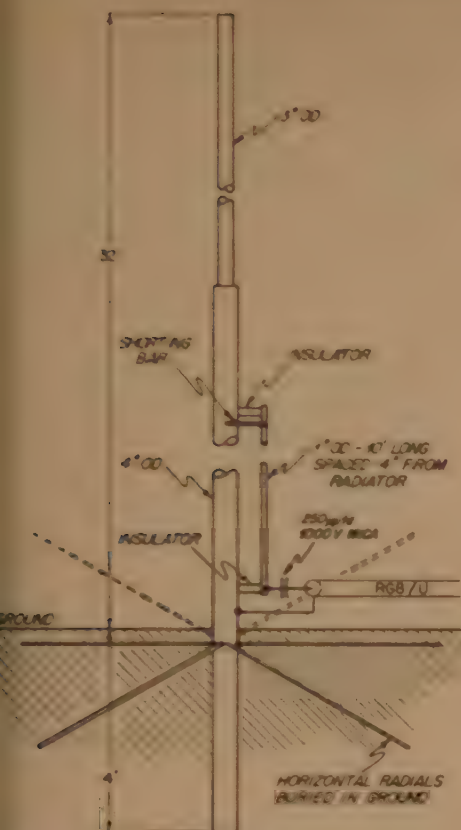


Fig. 1. Working sketch of the 7-Mc. vertical antenna described in this article. The details are thoroughly explained in the text.

happened that the only suitable place in the yard for the antenna was beside a neighbor's garage. After the hole was dug, I leaned the antenna against the garage and worked it down to the hole.

Holding the antenna vertical with one hand, I pushed dirt into the hole around it and tamped it down firmly with a "two by four." This operation took five minutes! And I am now del powered. I now had a self-supporting vertical antenna, thirty-two feet high.²

Next, I fastened a ten-foot length of one-inch meter aluminum tubing left over from an old antenna, parallel to the bottom section of the antenna and four inches from it, as indicated in Fig. 1. Insulators are National GS-3 or equivalent. (These I could not find in the *Sears* catalog.) Double-thick bands of the flashing aluminum fasten the insulators to both pieces of tubing and are also used for the shorting bar at the top of the matching section. The bottom of the one-inch tubing extends to about an inch and a half from the ground.

locations where the temperature drops below freezing, rain and moisture trapped inside the tubing might freeze and split it; therefore the four feet that are below the ground should be plugged and a few small holes drilled in the tubing near the ground level to prevent water from accumulating—Editor.

To reduce ground losses, I next installed a set of four, buried, No. 9, aluminum fence-wire radials. (*Sears*—\$6.10 for 500 feet.) I used a lawn edger to cut slots in the ground a few inches deep in which to bury them. One radial angles across the lawn and is connected to a water pipe. The others run off in different directions, as permitted by buildings and other obstructions.³ The incisions in the lawn healed in two days to where they were no longer noticeable. Copious watering helped heal the scars.

The feed line is RG-8/U, 52-ohm, coaxial cable, which may be buried. Its shield connects to the base of the antenna at the same point at which the radials are connected, and the inner conductor is connected to the one-inch diameter tubing through a 250 μ fd, 1,000-volt, mica condenser (good for up to a kilowatt input). The SWR is less than 2:1. It could be made to approach unity by careful adjustment, but the difference in results would be negligible.

The condenser is important in obtaining a low SWR on the feed line. Only at the ends and at points a whole multiple of a $\frac{1}{4}$ -wave from them does a resonant antenna represent a pure resistance. At other points along its length, there is also a reactive component present. With this feed system, the reactive component is reflected to the feed point as inductive reactance, which is tuned out by the capacitive reactance of the condenser.


Adjustment

Although duplicating the antenna shown will result in an efficient antenna, the following information is included for the benefit of those who are experimentally inclined or who wish to vary the dimensions in the matching section.

Adjustment procedure is this: substitute a variable condenser of about 300 μ fd. capacity for the fixed condenser. Connect an s-w-r meter

(Continued on page 68)

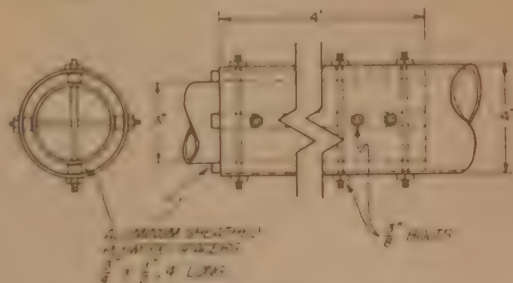3. The radials are not absolutely necessary. The antenna will work without them at reduced efficiency, because of higher ground losses. Their exact length is not critical, but should be at least $\frac{1}{4}$ -wave long (thirty-five feet at 7 Mc.). If possible, A minimum of four gives best results. Ground losses will continue to decrease slowly as additional ones are added. Broadcast stations use 120, equally spaced around the base of the antenna — Editor.



MAT—20' LENGTHS ALUMINUM TUBING—1 LENGTH 3"OD x .05 WALL
1 LENGTH 4"OD x .05 WALL

Fig. 2. Method of joining lengths of three-inch and four-inch aluminum tubing.

The VHF-UHF News

FURMAN C. COBB

c/o CQ Magazine, 67 West 44th St., New York 36, N.Y.

Anyone Have a Nice High Mountain?

In the early part of September the National Bureau of Standards (particularly the CRPL) released "Summary Technical Report 1805" describing *obstacle-gain* v-h-f transmission. The essence of the report is that a nice high sharp obstacle located near the mid-point of a proposed v-h-f path will actually *increase* received signal strength! It seems that the old idea of climbing up on top of a ridge or mountain is totally unnecessary, plenty inconvenient and far too expensive. The same effects are sometimes possible by just backing away from the mountain and letting "knife-edge" effect take over.

Knife-edge effect, or obstacle-gain as the CRPL prefers to call it, is not a new theory (the Bell Telephone Laboratories predicted it as early as 1933). Prior to CRPL experimental verification few v-h-f workers had given it any serious thought as a means to extend point-to-point coverage. V-h-f transmission in mountainous areas was known to be lossy and plagued with severe erratic fading. Psychologically, the idea of a mountain between the transmitter and receiver was never considered too healthy. Now it appears that the bigger the intervening mountain the better the chance of getting over it with a lot stronger signal than


if the mountain weren't there in the first place.

The accompanying illustration shows the profile of the path in Alaska (160 miles long) which utilizes the obstacle-gain knife-edge of Mt. Fairweather to reduce the signal loss. With 50-watt transmitters and 50-foot high antennas the loss over this path at 38 Mc. would be of the order of 207 db.* However, the basis of obstacle-gain theory, which combines diffraction and ground reflection effects, the predictable loss should be only 127 db. The experimental results showed the loss to be 134 db., within 7 db. of the value predicted.

* I will discuss transmission losses in a later column. For those to whom the term is new it might be well to point out that this figure was obtained by assuming the earth to be perfectly smooth and spherical. Hence any loss figure less than the predicted value may be construed as a "gain" over the theoretical transmission loss.


PROFILE OF PATH FROM YAKUTAT TO GUSTAVOUS, ALASKA

$h_t = h_r = 50$ feet; $f = 38$ Mc

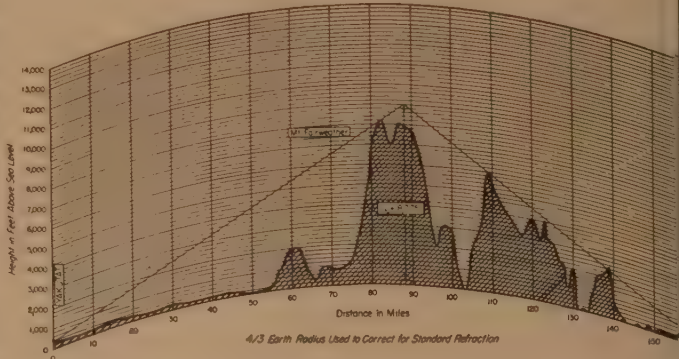

TYPICAL SAMPLE RECORDING ON THE ABOVE PATH

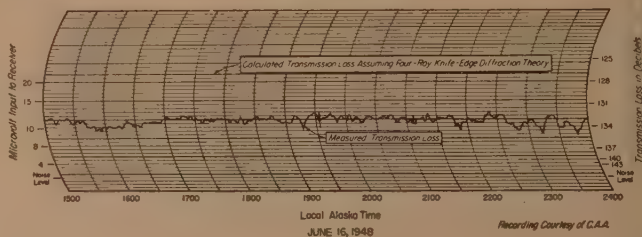50 Watt Transmitter Power
 $h_t = h_r = 50$ Feet



Experimental evidence of the obstacle-gain phenomenon obtained by the Civil Aeronautics Administration. The top figure is a profile of the transmission path from Yakutat to Gustavus, Alaska (160 miles) with the knife-edge of Mt. Fairweather utilized to reduce the signal loss. The power was 50 watts and the antennas were only 50 feet above ground level. With the 8775-foot mountain between the two terminals the signal increased 73 db. above the theoretical level. The bottom graph shows a sample recording.

nounced reduction in signal fading. It was brought out in the Summary Report that the high angles (relatively speaking) required to graze the top of the mountain causes the radio waves to miss the turbulent lower portion of the atmosphere which creates most of the fading. During a thirty test period the signal strength over the mountain varied by less than plus or minus 2 db around the mean value of 134 db.

Just what this means to the fellows working 6 and 2 meters is fairly evident to predict. One of the basic requirements for the obstacle gain theory to be of any value is that the height of the knife edge be much greater than the elevation of the common horizon. In other words, at 2 meters and over a 150 mile path, a mountain rising only 1000 feet above the surrounding terrain would not have the desired effect. Theory predicts that the 30 db loss might be

expected above and beyond the normal transmission loss.

It would appear that obstacle gain will be most important to the gang in the Rocky Mountain area, possibly not for DX, but for consistent work out to ranges of 180-200 miles. If nothing else, this experimental evidence does show that the California gang once again have the drop on the east coast boys—imagine getting signal gain because someone put a mountain in your front yard!

The "Skeleton" Slot Antenna for 144 Mc.

G2HCG attacked an interesting subject in the January 1953 issue of the R.S.G.B. Bulletin when he described his experiments with slot antennas. Such antennas are supposed to be particularly useful on only the u-h-f bands. At those frequencies it is mechanically feasible to cut a rectangular hole in a large metallic surface and by feeding it in an appropriate manner make it radiate reasonably well. Its greatest use today is in flush mounting in the skin of aircraft.

OM Sykes, G2HCG, seems, however, to have reversed the design and constructed his antenna out of tubing formed into the shape of a rectangle. His final dimensions as shown in the accompanying drawing were 13 inches by 37 inches fed with 600-ohm line. The long side of the "skeleton" slot (it is reported) must be vertical to radiate a horizontally polarized wave. However, your reviewer thinks that considerable energy is also going out in the vertical plane at the same time and would like to call for more experimental evidence before making final acceptance of the design.

The series of drawings on this page demonstrate the design sequence of the "skeleton" type so-called slot antenna. In A we see the usual straight dipole, in B we have the $\frac{1}{2}$ -wave extended antenna and in C the wave ends are bent downwards. The latter antenna still radiates a portion of its output in the same manner as the straight antenna. Now if we stack another antenna directly below it, but "upside down" we may join the ends since they are at the same potential. Carrying it a little further we can short out the feed points and take another feed point, say at the center of the "skeleton." The top and bottom sections still radiate appreciable horizontally polarized energy, and since they are stacked $\frac{1}{2}$ -wave apart they will "beam" broadside to the array.

With a single reflector spaced a quarter-wave behind the "skeleton," this antenna is supposed to have a 4 db. forward gain as compared with the straight dipole. Stacking seems to be possible and the final sketch shows the method of feeding with 300-ohm line and matching sections into a pair of "skeleton" slot antennas.

While this is an interesting design and may possibly be of use in certain instances (lends itself to extreme mechanical rigidity) the theory is certainly not too clear, and, as described by G2HCG, is somewhat confusing—especially when the requirement of at least $\frac{1}{2}$ -inch tubing is considered. All-in-all, we'd like to see some experimenting since this antenna might get around the necessity of polarization shift in areas where both horizontal and vertical polarization still has adherents. It is not a magic array and on close examination looks very much like our old friend, the "Bruce" array.


Meteor Propagation Tests by W4HHK

During the past few years a fairly heavy emphasis has been placed upon the contribution of meteoric ionization to the E-layer. Many scientists have shown that when a meteor is swept into the earth's atmosphere the velocity is so great (on the order of 30 to 80 miles per second) that ionization takes place in a cylindrical volume constituting the meteor path or trail. This ionization is momentary and seems to concentrate at a height of from 50 to 75 miles above the earth's surface. This is the area of the so-called E-region.

It has been shown that a certain number of meteors will each day produce a residual background ionization and that some of the bigger and faster meteors will momentarily produce sufficient ionization to refract radio waves up to 150 Mc. The general term used to distinguish these short-periods is "bursts." The active duration of the bursts has not been clearly established and there is some evidence that a short period of two-way communication might be possible using this mechanism.

Starting around the first of July, W4HHK and W5RCI have been engaged in a series of schedules with W2AZL, W2NLY, W2UK and other interested parties to ascertain the potentialities of meteoric ionization burst transmission. Most of this work has taken place on 144.020 Mc.

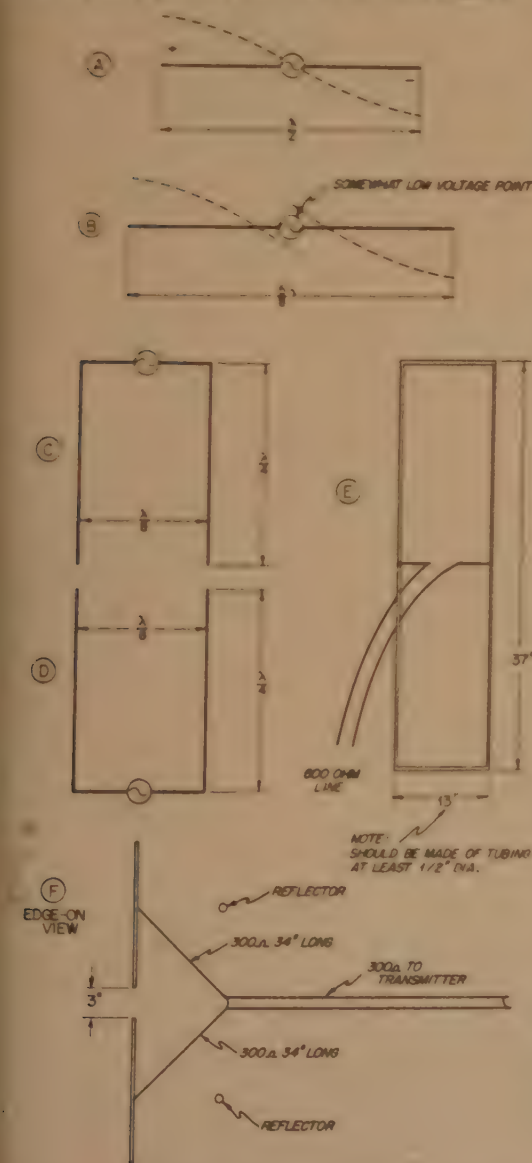At this writing the northern end of the path has copied both W4HHK and W5RCI (identified complete calls). The southern end has obtained copy on W2AZL, W4A.



Derivation of the "skeleton slot" antenna for 144 Mc.

and W2UK. Bursts have also been heard that according to the schedules and frequencies should be credited to W2NLY, W3GKP and others. Equipment is being improved, and at latest reports W2UK was erecting a 30-wavelength per leg rhombic while W4HHK was gathering the components for a kilowatt rig.

The schedules have been nightly, 2215 to 2235 EST, with the northern end calling on the odd five-minute periods and W5RCI and W4HHK transmitting on the even five-minute intervals. Morning schedules are also being attempted from 0600 until 0630 EST on the same calling and listening basis.

While undoubtedly these tests are not something that will completely change the character of v.h.f. propagation as it applies to Hams, they should be valuable towards furthering our knowledge of meteoric type ionization. If contact can be established for a short period of time it may also provide a means for a WAS on 144 Mc. We shall report further on these tests in a later issue.

Some Thoughts on New Products

The Amperex Electronic Corporation has just announced their "junior" version of the popular AX9903 or 5894. It is a twin tetrode called the 6252. The plate

upper edge of the band to watch for DX openings. Spotting a frequency in the 152-174 Mc. range, they have monitored a channel used by the police, forestry or fire stations some 80 to 150 miles away. A notable increase in signal strength is a good indication of a possible opening. A good bet for this job is the latest communications receiver put out by Radio Apparatus Corp., 55 N. New Jersey St., Indianapolis, Ind. It is called the



Amperex 6252



Radio Apparatus DR-200

Model DR200 and has provisions for both spot frequency operation, or for tuning manually the range of 30-50 Mc. and 152-174 Mc. Naturally, it is strictly NEFM. The cost is supposed to be very low.

Notes

Our V.H.F./U.H.F. column was cut back this month due to some extra space requirements that came in at the last moment. Next month we will be back with a full 3-plus page column . . . Many thanks to G5CD who recently sent in some material on his helical antenna for the 420-Mc. band. Photograph and details next month . . . Various club papers throughout the country are now allocating space each month to V.H.F. columns. Out in New Mexico, W5RFF has been doing a nice job reporting for the Albuquerque VHF Club in the CQ/NM Bulletin. His latest column reported that W5NSJ was set up on 220 Mc. and looking for contacts. Also K5NRX was sending code practice on 2 meters on Monday, Thursday and Saturday at 1930 local time.

dissipation is only 20 watts (ICAS) as compared to the 40-watt dissipation of the AX9903. The manufacturer reports a power output of 12 watts at 600 megacycles. Physically it is 3 inches in overall height, and slightly less than 1 1/4 inches in diameter. The 6252 sounds like it would be particularly useful in mobile transmitters and as a buffer/multiplier into the 420-Mc. band.

An increasing number of 2-meter operators have been turning to the commercial channels just outside the

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946 (Title 39, United States Code, Section 233) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF CQ, published monthly at New York, N. Y. for October 1, 1953.

1. The names and addresses of the publisher, editor, managing editor, and business managers are: Publisher, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.; Managing Editor, Oliver P. Ferrell, 67 West 44th St., New York 36, N. Y.; Business Manager, Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.) COWAN PUBLISHING CORP., 67 West 44th Street, New York 36, N. Y.; Sanford R. Cowan, 6 Embassy Court, Great Neck, N. Y.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgagees, or other securities are: None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and beliefs as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

Sworn to and subscribed before me, this 28th day of

(Signed) S. R. COWAN, Publisher
September, 1953.

HARRY N. REIZES, Notary Public



Monitored by LOUISA B. SANDO, W5RZJ

24th St., Los Alamos, New Mexico

Often this column turns out to be more of a family affair than just of and for the YLs. After all, amateur radio is becoming increasingly a hobby for the whole family, so it is only natural. Many a YL's story is so closely tied with that of other members of the family that her's can't be told without including theirs. Such is the case of the Battin family of Elgin, Ill., whose story we are very happy to share with you.

It's an all-Ham family—Edith, W9OTO; her OM Everett, W9OWD; daughter June, W9OTM, and son John, W9MEM. It all started with John. He had such an all-consuming interest in things radio that he started repairing receivers at the age of 9½ years! He was 13 when he got his Ham ticket. He is now 16, and in addition to his Hamming he has a good radio service business which he carries on in a 2-room trailer in the back yard. One room is the service room and the other the Ham shack. Of course, he has built his own rigs and is now running 500 watts, phone and CW, operating mostly 40 and 80, and 20 CW, where he likes to go after DX.

All this Hamming had a very strong influence on the rest of the family, and about two years ago Edith, Ev and June all took their exams on the same day—and came up with calls so similar. June is 19 years old. She graduated from the Elgin high school in '52 and now works for a shoe store. For her station W9OTM runs about 40 watts using a Lyeco 600 transmitter with additional modulator, and she has a BC348 receiver. She operates mostly CW on 40 and 80 (holds a 20 WPM CPC), but she does get on 75 and 40 phone once in a while. June also does

some of her own repairing. Other hobbies include reading, dress making, crocheting, bicycle riding with her brother, and she plays violin in the Elgin Civic Orchestra each winter.

Edith, W9OTO (also known as "Honey"), and her OM, W9OWD, share the same station. They have been on CW mostly until John recently built them a new rig which they also use on 75 and 40 phone. They also get on 160 some in the winter. Their receiver is an S-40.

Practically a club by themselves, they are all charter members of a new radio club begun in Elgin last January. June is secretary-treasurer. Ev helped out with code classes and the club has "graduated" five Novices and two General Class licensees since its beginning. All the Battins are "Rag-Chewers" and John has WAS. Edith, at this writing, needed only Nevada to complete her WAS.

Not only do the Battins share their radio hobby, but also their interest in helping less fortunate people. Ev, W9OWD, is a minister and musician. He is totally blind and has been for 28 years. He plays several instruments, including piano, piano accordion and guitar, and it is through his music that he makes his livelihood. Most of his preaching is done in the missions on Chicago's "Skid Row." The whole family helps when he has a service. They take complete charge, supplying special music, pianist and song leader. They sing group numbers, duets or solos. Ev and Edith both play piano and when she sings solos she accompanies herself with her Spanish

(Continued on page 63)

YLs enjoying the New Hampshire State Convention at Concord on Sept. 13th: Left to right, front row: W1FTJ, VZD, UBM, BCU, OAK, UZR, WTQ, WOY. Second row: W1YYM, RYJ, QJX, W8ATB, W1SVN, TRE. Third row: W1YFV, VFK, ZEJ, W4AVA, W1VYH. Fourth row: W2KYF, W1WIT, YU, VOS, OME, UFM. Fifth row: W1UET, ULF. Last row: W1RLQ, UKR, QON, FOF, YPQ.



ALL TIMES IN C. S. T.

15 Meters 20 Meters 40 Meters 80 Meters

CENTRAL, USA TO:

South East Asia
 Hawaii
 Australasia

ALL TIMES IN P. S. T.

15 Meters 20 Meters 40 Meters 80 Meters

WESTERN, USA TO:

Europe & North Africa
 Central & South Africa
 South America
 Guam & Mariana Islands
 Marshall Islands
 Australasia
 Japan & Far East
 Philippine Islands & East Indies
 Malaya & South East Asia
 Hong Kong, Macao & Formosa

ALL TIMES IN E. S. T.

15 Meters 20 Meters 40 Meters 80 Meters

EASTERN, USA TO:

Western Europe
 Central Europe & Balkans
 Southern Europe & North Africa
 Near & Middle East
 Central & South Africa

South America
 South East Asia
 Australasia
 Guam & Pacific
 Japan & Far East
 West Coast, USA

ALL TIMES IN C. S. T.

15 Meters 20 Meters 40 Meters 80 Meters

CENTRAL, USA TO:

Western & Central Europe
 Southern Europe & North Africa
 Central & South Africa
 Central America & Northern South America
 South America
 Japan & Far East

Symbols For Expected Percentage Of Days Of Month Path Open:

(0) None (1) 10% (2) 25% (3) 50% (4) 70% (5) 85% or more
 * Indicates time of possible ten-meter opening.

Ionospheric Propagation Conditions

Forecasts by

GEORGE JACOBS, W2PAJ

144 40 72nd Ave.

Long Beach, Calif. 90801

General Propagation Conditions

10 METERS—DX poor to fair with some daytime openings expected on certain North-South paths.

15 METERS—Fair to good world-wide DX during daytime hours.

20 METERS—Band closing earlier because of decreased hours of daylight. Daytime DX conditions fair to good with Northern Hemisphere signals somewhat stronger as a result of the seasonal decrease in solar absorption and atmospheric noise levels.

40 METERS—Fair to good dark hour world-wide DX possible. Band opening earlier for DX because of early hours of darkness, also closing earlier in the evening on East-West paths because of MUF failure.

80 METERS—Night-time DX fair and improving with considerably less atmospherics. When MUF failure causes 40 meters to drop out, check 80 for openings.

160 METERS—DX possibilities improving with decreased absorption and lower atmospheric noise levels in Northern Hemisphere. DX possible during approximately the same hours as 80-meter openings but on fewer occasions and with weaker signals.

In general, in the Northern Hemisphere during November, solar absorption and atmospheric noise levels continue to decrease, daytime usable frequencies increase and night-time frequencies decrease considerably from summer values.

This overall picture of band conditions is intended to indicate qualitative changes in each band from month to month. For specific times of band openings for any particular circuit, refer, as usual, to the *Propagation Charts*. Commencing last month these *Charts* appeared in a slightly different, but perhaps handier format.

A note to you fellows who conduct local nighttime nets on the 80-meter band. Towards the end of November, and until the late spring, you will experience considerable difficulty keeping satisfactory contact with stations located within a radius of approximately 100 miles. The reason for this is that on a good many nights the MUF for these short paths will drop below 3.8 Mc. after approximately

3:30 p.m. Local Standard Time, and below 3.5 Mc. about an hour later. I suggest that you give serious consideration to the 160-meter band or the VHF bands for local network operations.

This month's *Propagation Charts* are based upon a predicted smoothed sunspot number of 16. The *Charts* have been calculated from world-wide ionospheric contours appearing in the CRPL-D series, "Basic Radio Propagation Predictions," issued monthly by the Bureau of Standards. This publication is available on a purchase basis from the Superintendent of Documents, U.S. Government Printing Office, Washington 25, D.C., for 10 cents a single copy or \$1.00 for an annual subscription of 12 copies.

Methods for using these charts for calculation of propagation conditions on a specific circuit are given in Circular 465 of the National Bureau of Standards, entitled "Instructions for the Use of Basic Radio Propagation Predictions," available for 30 cents from the Government Printing Office.

Information concerning the theory of radio-wave propagation, measurement, techniques, structure of the ionosphere, ionospheric variations, prediction methods, absorption, field intensity, radio noise, lowest required radiated power and lowest useful high frequency is given in Circular 462 of the National Bureau of Standards, "Ionospheric Radio Propagation." This circular is available from the Government Printing Office for \$1.00.

One Way Skip

W2JOA, among others, has recently asked for an explanation of "one way skip"—the phenomenon that is occasionally observed when stations from a particular area can be heard, but not worked, especially when the power being used is about the same level at both ends of the circuit.

Considering equal radiated powers at both ends of the circuit (where radiated power is equal to the power into the antenna multiplied by the power gain of the antenna as compared to a reference half-wave dipole, a half wavelength above ground), the laws of reciprocity are generally considered to hold true for radio propagation. That is to say, a radio signal going for example from New York to Rio should be affected by the ionosphere in exactly the same degree as the signal traveling the reciprocal path from Rio to New York. Actually, as far as signal strength goes, this is usually true. In our example, the signal received in New York from Rio should equal the strength of the signal received in Rio from New York. However, the intelligibility of a signal, that is whether it will be heard or not, depends not upon the signal strength alone, but upon the signal to noise ratio at the receiver. The atmospheric noise levels throughout the world vary considerably with geographical

Severe Ionospheric disturbances are expected

Nov. 11-12 and 15-17, with the complete period

of 11-25 subnormal. Good short wave propagation

conditions are expected Nov. 1-10 and 27-30.

area, being highest in the equatorial regions and lowest in the polar regions. It is the difference in atmospheric noise levels that may exist at each end of a circuit that usually accounts for what may at times appear to be a violation of the laws of reciprocity. Going back to our example of the New York—Rio circuit: during November at 1600 EST, the atmospheric noise level on 20-meters in Central America and the Northern Countries of South America, including Rio, is approximately 13 db. higher than those throughout most of the USA. If the signal delivered from Rio in New York is just above the noise level, the same signal strength received in Rio from New York will be 13 db. below the noise level. The Rio signal would therefore be heard in New York but the New York signal would not be heard in Rio, regardless of the fact that both signals are of equal intensity. So while the laws of reciprocity are valid for signal intensities, they do not necessarily hold for signal to noise ratios. The differences in noise intensities that

(Continued on page 60)

Order Now For
Early
Delivery

CQ MAGAZINE

CQ 11

67 West 44th St., New York 36, N. Y.

Enclosed find \$_____ to cover this gift order for the

RADIO AMATEURS' MOBILE HANDBOOK

(\$2. each) and those gift orders below—

HANDBOOK to be sent to:

CQ 11

Name _____ Call _____

Address _____

City _____ Zone _____ State _____

CQ 11

Name _____ Call _____

Address _____

City _____ Zone _____ State _____

CQ 11

Name _____ Call _____

Address _____

City _____ Zone _____ State _____

CQ 11

Name _____ Call _____

Address _____

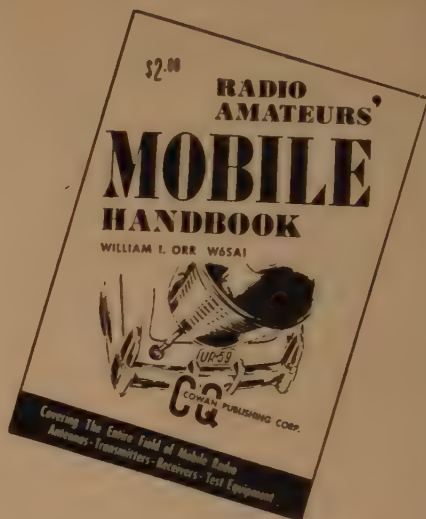
City _____ Zone _____ State _____

CQ 11

Name _____ Call _____

Address _____

City _____ Zone _____ State _____

**THE PERFECT GIFT**

From one Ham to Another, There cannot be a truer, more valued expression of Yuletide brotherhood than a gift of a **RADIO AMATEURS' MOBILE HANDBOOK**. Seven construction-rich chapters—192 pages crammed with up-to-date information designed to make your rig a joy to operate. The best Mobileers build their rigs from **HANDBOOK** designs—why don't you follow suit—be a leader in your mobile group!

National



Communications Receivers



NC-88

**World-Master in coverage...
World Beater in value**

The advanced NC-88 circuit uses 6 high gain miniature tubes and amplifier sockets 540kc to 40mc with variable bandspread for amateur bands. Built-in speaker, two IF stages, 2 audio stages with phono input and tone control, antenna trimmer, separate high frequency oscillator, sensitivity control, series valve noise limiter, delayed AVC, headphone jack, and other features that add valuable performance characteristics for the price or made.

NC-88 complete with tubes \$129⁹⁵



SW-54

**Mighty Midget with a
7-continent "pull"**

For the compact home shack — a truly modern receiver only 11" long, 7" wide, 7" high, yet designed and built to hold a selective, sensitive chassis, a good speaker and a front panel as handy and handsome as any. Slide rule general coverage dial with police, foreign, amateur and ship bands clearly marked. Unique, adjustable bandspread. Covers 540kc to 30mc in 4 separate bands. Includes receive-standby switch, AM-CW switch, phone jack.

SW-54 complete with tubes \$59⁹⁵

**Anywhere in The World
ORDER BY MAIL
DIRECT FROM HARVEY**

**Write for full details
and accessory lists to:**

NOTE: In view of the rapidly changing market conditions, all prices shown are subject to change without notice and are Net, F. O. B., New York City.

HARVEY

**ALWAYS HAS IT...IN STOCK
For IMMEDIATE DELIVERY**

HRO-Sixty

Latest and greatest of the great HRO's!

This famous receiver gives you dual conversion for all frequencies above 7mc plus 12 permeability tuned circuits in the three 456 kc IF stages. Other new features include current-regulated heaters in the high-frequency oscillator and 6BE6 mixer, four panel plug-in coils cover 1.7 to 30mc, bands switch automatically when coils are plugged in. Edge-lighted, direct frequency scale shows only the band in use. Negligible drift. Provision for crystal calibrator unit and NFM. High-fidelity push-pull audio with phono input jack. Controls: Bandswitch, Oscillator, Tuning, Tone, Antenna trimmer, Dimmer, AVC, Limiter, AF gain, Calibration, CWO, Phasing, Selectivity, On/Off, RF gain, AM-NFM-Phono. Accessory socket for Select-O-Ject.

HRO-60T Table Model, complete with tubes, less speaker \$533⁵⁰
Includes 4 coils, A, B, C, D, for 1.7 to 30mc.

HRO-60R Rack Model, supplied as above \$533.50
Other coils, covering broadcast, marine and other commercial and amateur bands, available

HRO-60RS Rack Model Speaker 76.00

HRO-60TS Table Model Speaker 16.00

NFM-83-50 Narrow Band FM Adapter 17.95

SOJ-3 Select-O-Ject 20.75

NC-183D

12 tuned IF circuits.

1mv sensitivity on 6 meters

Steep-sided skirt selectivity with 3 IF stages (16 tuned circuits on the 3 high bands; 12 on all other bands) plus a new crystal filter, new bi-metric, temperature-compensated tuning condenser for drift-free operation and other features make the NC-183D a revelation in all-around performance. Adaptable to NFM, Phono output jack. Covers 1.5-55mc, with bandspread dial on all amateur bands including 6 meters, and bandspread possible on all frequencies within range. Controls: Main tuning, Bandspread tuning, Band switch, RF gain — AC on/off, AF gain, Send/receive, AVC/MVC, tone CWO, CWO pitch, Limiter, Selectivity, Phasing, RF trimmer, Radio/Phono.

NC-183DT Table Model, complete with tubes, less speaker \$383⁵⁰

NC-183DR Rack Model, complete with tubes, less speaker 383.50

Speaker 16.00

NFM-83 Narrow Band FM Adapter 17.95

NC-125

With built-in Select-O-Ject

An up-to-the minute general coverage receiver incorporating late engineering improvements and including the Select-O-Ject audio filter. Select-O-Ject can boost any single selected audio frequency 38db or reject any single frequency 45db within a range of 100 cps to 12,000 cps. It practically eliminates annoying heterodynes, whistles and unwanted signals, gives selectivity surpassing that of most higher priced receivers. Also, edge-lighted direct reading scale with amateur, police, foreign and ship frequency bands clearly marked; voltage-regulated, stabilized oscillator, one for phono or NFM adapter, socket for battery operation and other valuable features.


NC-125 Complete with tubes, less speaker \$199⁹⁵

NC-125TS — Speaker 11.00

NFM-73 — Narrow Band FM Adapter 18.75

**WE'RE GENEROUS
ON TRADE-INS!**

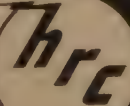What've you got to trade on this fine National equipment? Because of our big outlet in the New York market, we can make you a generous allowance. Send full description.



Harvey RADIO CO., INC.

103 W. 43rd St., New York 36, N.Y. • Judson 2-1500

NOVICE SHACK

Conducted by HERB BRIER, W9EGQ

385 Johnson St., Gary 3, Indiana

Diagrammed in *Fig. 1* is a transmitter designed by Everett Taylor, W8NAF, 1125 Highridge Ave., Dayton 10, Ohio, as a first transmitter for the Novice. Although easy to build, it has that "professional" appearance often missing in simple, home-constructed equipment. Designed to be used with a power supply furnishing 250 to 350 volts, it is capable of handling an input of ten to seventeen watts. The complete unit is pictured in *Fig. 2*.

All data required to duplicate the transmitter can be gleaned from the diagram and pictures. The thought of cutting the socket holes might frighten a constructor who does not possess a socket punch. Fortunately, the aluminum is so soft that it is not too difficult. One method is to drill a number of small holes around the perimeter of a circle the desired diameter, knocking out the center slug and filing the edges of the hole smooth. Another is to

cut them out with an ordinary coping saw, pausing frequently to allow the blade to cool.

An unusual feature of the transmitter is that the tuning condenser is mounted inside the coil form. One adjustment of the condenser holds for the entire Novice band. By providing separate coils for the two bands, switching from 3.7 Mc. to 7.2 Mc. consists of changing the coil and crystal. W8NAF could not give winding data for a 7-Mc. coil, but the data suggested in the parts list should be satisfactory.

Obtaining Power

To Operate The Transmitter

The unusual looking plug on the end of the power cable is actually an adaptor plug, used by W8NAF to borrow the power to operate the transmitter from his communications receiver. To do so, he installs a s.p.d.t. switch in the B+ circuit of the receiver power supply to switch the high voltage to *pin No. 6* of the output tube socket in the "standby" position. This pin is unused in octal-based audio pentodes and tetrodes. The adaptor plug brings the voltage to the transmitter.

To construct the adaptor, wire together an octal plug (may be an old tube base with all pins) to an octal socket, *pin for pin*, except *pin No. 6*. The transmitter power cable is then wired to it. Connections to *Pins 2* and *7*; B+ to *Pin 1*; B- to *Pin 6* on the plug only. The adaptor is plugged into the output tube socket and the tube is plugged into the adaptor. Be sure that *pin 1* of the output tube socket is grounded to the receiver chassis, and *pin 6* is used as a tie point, all connections to it must be removed to an extra tie point before the adaptor can be used for the transmitter B+ terminal.

In receivers with an auxiliary equipment socket it may be used, instead of the output tube socket, to bring power to the transmitter.

As is usually true of any scheme to get something for nothing, utilizing the receiver power supply to operate a transmitter has a number of disadvantages. Possibly the most serious of them in the eyes of the average owner of an expensive commercial receiver is the necessity of making wiring changes in the receiver. Unfortunately, the changes are more extensive than merely changing the "standby" switch. Not all B+ voltages are tapped off the power supply at the same point. Consequently, it is usually necessary to rearrange some of the B+ wiring to in-

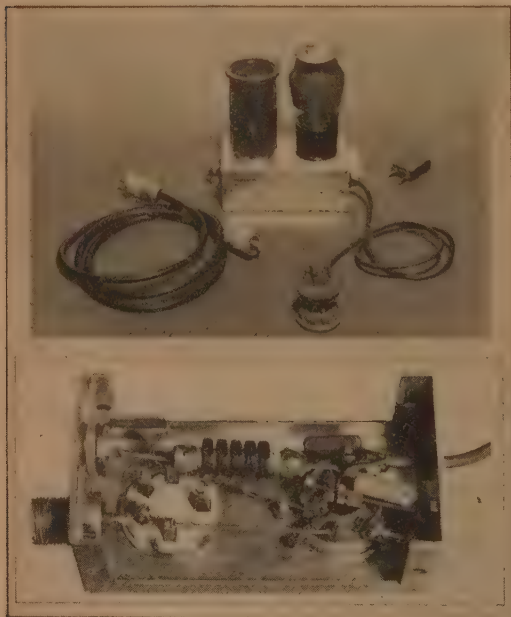


Fig. 2. Attractive Novice transmitter designed by W8NAF and reviewed in this month's column. It is capable of transmitting over long distances under favorable conditions.

(Continued on page 50)



LEO J. PETERSON
W8092

Pay only 10% Down! 18 months to pay on Major Equipment

New! It's easier than ever to buy from WRL where you get easy down payments, generous trade-ins, and personalized service from "The World's Most Personalized Radio Supply House," and "The World's Largest Distributor of Amateur Radio Transmitting Equipment." Send for our big list of over 600 reconditioned used items — all carrying new factory guarantee.

LEO GIVES BEST DEAL ON . . .

National RECEIVERS

NC-183 D RECEIVER

Dual conversion on the three highest ranges plus every feature you want in a truly modern receiver!

(Less Speaker) \$383.50



\$38³⁵ \$20.49 per month
cash down 12 months
\$20.90 per month
down 18 months

HRO-60 RECEIVER

with AUTOMATIC DUAL CONVERSION

Less speaker \$533.50

\$53³⁵ cash down
\$42.42 per month—12 months
\$29.08 per month—18 months

Now Available . . . NEW NC-88

only \$129.95
with Built-in Speaker

\$13⁰⁰
cash down
\$10.33 per mo.—12 mo.





A top-notch value for both the novice and experienced amateur! Compare these features: Calibrated bandspread for 80, 40, 20, 15, and 10 meter bands. Advanced A.C. superhet circuit uses 8 high gain miniature tubes plus rectifier. Covers 540 kcs. to 40 mc. in 4 bands. Tuned R.F. stage—two I.F. stages—two high fidelity audio stages with phono input and 2-position tone control. Built-in speaker. Antenna trimmer—separate high frequency oscillator. R.F. gain control. Series valve noise limiter. Delayed A.V.C. Headphone jack. And, send-receive switch.

JUST OFF THE PRESS!

NATIONAL RECEIVERS AND ACCESSORIES

MODEL

	CASH DOWN	CASH PRICE
NC-125 RECEIVER	\$20.00	\$199.95
SWS4 RECEIVER	6.00	59.95
SELECT-O-JET	2.88	28.75
NFM-R3-50 ADAPTER	1.80	17.95
SPEAKER (for HRO-60 or NC-183D)	1.60	16.00

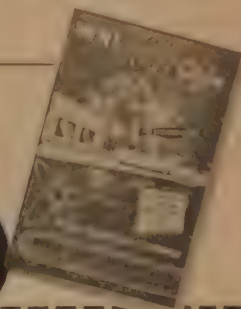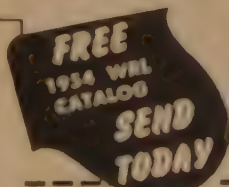

World Radio Laboratories
744 West Broadway
Council Bluffs, Iowa

C 11

Please send me:

- ☐ New Catalog
☐ Free Catalog
☐ Radio Map (25c)

- ☐ NC-88 Info
☐ NC-183 D Info
☐ HRO-60 Info
☐ NC-125 Info
☐ Used Equipment List

Name _____

Address _____

City _____

State _____


WRITE FOR DETAILED SPECIFICATION EQUIPMENT SHEETS

WRITE
WIRE

PHONE
3-0277

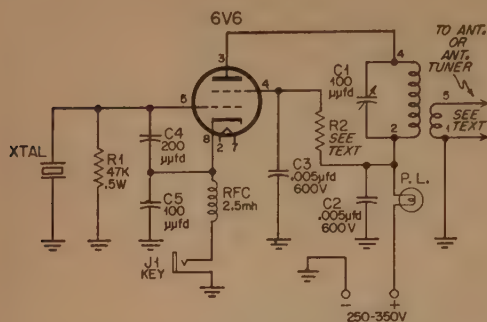World Radio
LABORATORIES COUNCIL BLUFFS, IOWA





- L1—3.7 Mc., 22½ t. #22 en. close wound.
 L2—3.7 Mc., 4 t. #22 en. close wound 3/16" below L1.
 L1—7.2 Mc., 12 t. #22 en. spaced wire diameter.
 L2—7.2 Mc., 3 t. #22 en. close wound ¼" below L1.
 (Coils wound on 1½" diameter, 5-prong forms, with rib for C1. Bud No. CF595 or equiv.)

- C1—100 μfd. APC type variable (mounted inside coil form)
 C2, C3—0.005 μfd. disc ceramic, 600v.
 R1—47,000 ohms ½w.
 R2—18,000 ohms 2w. for plate voltage of 350.
 10K, 1w for 300 volts.
 Omit and connect pin 4 of tube socket directly to pin 2 of coil socket for voltages less than 260 volts.
 RFC—2.5 mh. radio frequency choke.


- P.L.—No. 49, pilot-light plate-current indicator.
 J1—single-circuit phone jack.
 Tube—6V6 metal or glass.
 Xtal—3.7-3.75 Mc., or 7.175-7.2 Mc.
 —Also required—
 1 octal tube socket
 1 5-prong coil socket
 1 crystal socket
 1 output connector
 1 4 x 2½ x 1½-inch aluminum box (Bud or ICA)

Fig. 1. Schematic, coil table and parts list of the W8NAF seventeen-watt Novice transmitter. Note that tuning condenser C1 is mounted inside the coil form.

that the new switch breaks all B+ circuits.

When this is done, there is a possibility that the key-up voltage will be high enough to endanger the power supply filter condensers. And who knows, the manufacturer might have had a good reason for the way he wired the power supply.

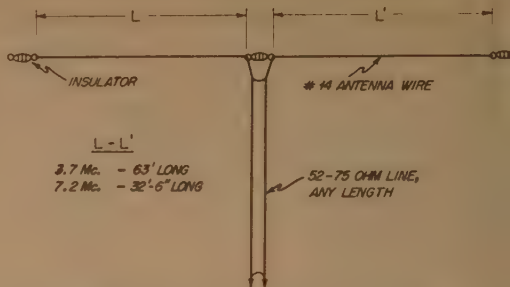Another point to consider is that using the receiver power supply to operate the transmitter precludes using the receiver as a monitor. Therefore a fre-



This half-wave doublet is the most suitable antenna for use with the W8NAF transmitter. For details, see text.

quency-meter/monitor would have to be built to comply with FCC regulations.

Considering everything, I doubt if many Novices would care to make the necessary modifications in a new receiver to save the cost of a small power supply, especially when the savings would be less than ten dollars (at amateur prices) for parts. Some of the older receivers, however, will operate head phone with the output tube removed from the receiver entirely. With such a receiver, the power normally consumed by the output tube may be used to operate a small transmitter. In fact, the output tube may be used as the transmitter oscillator tube. Transmitter input is limited to that normally drawn by the output tube, which usually totals about forty milliamperes. At the normal receiver plate voltage of approximately 250 volts, this allows an input of ten watts or so.

Antennas

Probably the best antenna for use with this transmitter is a ½-wave doublet, fed with 75-ohm "twisted lead," RG-58/U or RG-59/U coaxial cable. Such an antenna is merely connected to the output connector and the number of turns on L2 varied to draw the desired plate current.

Other antennas will probably require an antenna tuner. A satisfactory one would be a coil and capacitor duplicating C1, L1, and L2. The two L windings are connected through a low-impedance

(Continued on page 60)



KN6NAP, San Francisco, Calif., and operator, Len Gerald, who is seventeen years old. In three months operation, seven states and three countries have been worked. Receiver is an NC183D. Transmitter is home constructed—a 6V6 driving a 6146 to fifty watts input. Antenna: Coaxial-fed doublet.



Ex-Novice Bill Steinmetz, W4TFP, Sarasota, Fla. Bill uses a five-element beam on 28 Mc., and a long wire on the other bands. Although an avid Ham, Bill, a junior in high school, believes that school comes first. He carries a straight "A" average! P.S. Bill's dad is W4YI.



FOLLOW ARROW FOR BIGGEST STOCK AT LOWEST PRICES

• RADAR-TRANSMITTERS
• RECEIVERS - TUBES - PARTS

UHF 420 MC. TRANSCIVER

Complete transmitter-receiver unit with 3 stages of 30 MC IF amplifier. This unit is the famous APS-13 Radar Set. Less tubes and dynamotor. \$9.95



dynamotor tube, for remote control and citizen band use. With mounting bracket. \$9.95
Less R.F. section, tubes & dynamotor 5.95

HS-18 HEADSET, High Imp. New.....	\$2.45
HS-23 HEADSET, High Imp. New.....	4.95
HS-30 HEADSET, Featherweight type Low Imp. NEW.....	\$2.49 USED..... 1.49
HS-33 HEADSET, Low Imp. New.....	6.95
HS-38 HEADSET, USED, steel cond.....	1.49
M-164 High Imp. 8000 ohms. New.....	3.95
DESK STAND MIKE, New.....	5.95
LIP MIKE, New type New.....	98
TU-17 TUNING UNIT, (2.3 MC.) For BC-228 Xmitr. Used.....	\$ 2.95
1-70 "S" TUNING METER New.....	2.50
WOBULATOR, See p. 43 Dec '51 RADIO NEWS.....	5.95
BC-1023 75 MC. MARKER BEACON RECEIVER, Complete with tubes, mfg. Jack NEW.....	10.95
TU-25 TUNING UNIT, (3.5-5.3 MC.) For BC-228 Xmitr. Used.....	2.95
R-28 ARC-5 2-METER RECEIVER 100-156 MC. With tubes First cond.....	45.00
PE-101 DYNAMOTOR New.....	5.95

25W FL TUBE
Limited quantity! Order now!

DASH MATCHED PAIR \$9.95
..... \$17.00

COMMAND EQUIPMENT (SCR-274N)

	Used	New
BC-442 ANTENNA RELAY Less cond. \$ 1.95	\$ 2.95	
BC-481 TRANSMITTER CONTROL BOX	1.80	
BC-480 3 RECEIVER REMOTE CONTROL BOX	2.95	
MC-218 MECHANICAL DRIVE SHAFT Per length.....	2.95	
BC-496 2-POSITION RECEIVER CONTROL BOX.....	2.95	
BC-455 4-9 MC RECEIVER With tubes	9.95	14.95
BC-483 With tubes.....	10.95	
BC-484 RECEIVER With tubes.....	12.95	
BC-457 TRANSMITTER 4-5.3 MC. With tubes.....	9.95	
CCT-52232 NAVY COMMAND TRANSMITTER 2 1-3 MC. New, with tubes.....	14.95	

	Used	New
MC-211 90° ANGLE COUPLING UNIT		\$9.95
FT-234 MOUNTING RACK for single transmitter.....	\$2.05	3.50
FT-226 MOUNTING RACK for 2 Command Xmitr.....		3.95
FT-221 MOUNTING PLATE for FT-220		1.90
FT-220 MOUNTING RACK for 3 receivers.....		2.25
FT-225 MOUNTING PLATE for BC-456		2.25
BC-456 MODULATOR For SCR-274 ..		5.50
Complete set of 4 tubes for transmitter.....		1.25
BC-458 TRANSMITTER 5.3-7 MC. With tubes.....	9.95	
BC-459 TRANSMITTER 7-9 MC. With tubes.....	9.95	

ID6-APN-4

Complete with tubes and crystal.

Excellent Condition \$42.50

C.A.P. SPECIAL BC-625 VHF TRANSMITTER

Freq. range 100-186 MC With modulation section, 1.2m tubes & crystals, with conversion dops. Used, \$9.95 good condition.

BC-604 30 W. FM TRANSMITTER. For 20-27 MC. band ideal for 10-11 meters. Complete with tubes, temperature controlled crystal oven and technical manual with all instructions for BC-603 and BC-604. Less dynamotor and crystals. Excellent condition. \$12.95
BC-603 RECEIVER, NEW..... 65.00

Mobile C.D. Menl C.A.P.I.

UHF MOBILE DIRECTIONAL ANTENNA, New, .95c
SCR-283 TRANSMITTER-RECEIVER, Complete with dynamotor and tubes. 40, 80-meter, F.B. for \$24.50

DYNAMOTOR SPECIAL, 9 V. input. Output 450 v. 75 mls. With extended shaft and drive gear on one end. New..... \$7.95

ARC-4 MOBILE TRANSCIVER

140-144 MC. Complete with control box, tubes, 12/24 VDC dynamotor with schematic. This is a special \$32.50 reduction for this month only. Like new
RS-38 MIKE, Carbon type for ARC-4, NEW..... \$4.95
Used..... \$2.95 Mounting Bracket 50c

MP - 22 MOBILE ANTENNA

MOUNTING Per Pair..... \$4.95
BRACKETS Each..... 2.95

MN-28C CONTROL BOX, Excellent cond. \$ 9.95
MR-9 CONTROL BOX, Excellent cond. 14.95
RA-10DB COMMUNICATION D.F. RECEIVER, New..... 37.50

Miscellaneous Specials!

BROADCAST BAND & AERO

MN-28-C Remote Controlled navigational direction finder and communication receiver. Manual DF in any one of three frequency bands, 150 to 1500 KC. 24 V. Self contained dynamotor supply. Complete installation, including receiver, control box, keep transmission line and det. shafts \$49.50
BRAND NEW
MN-28-C alone, New..... 39.50

SCR-625 FAMOUS MINE DETECTOR

For prospectors, miners, oil companies, plumbers, etc. \$59.50

NEW WHILE THEY LAST!.....

TA-12 SOW TRANSMITTER, 40, 80 meters, Ideal for mobile. With tubes. Excellent cond..... \$29.95
MP-28 POWER SUPPLY, Excellent cond..... 14.95
FL-8 RANGE FILTER..... 1.95
FL-5 RANGE FILTER, NEW..... .95

PE-103 DYNAMOTOR

Like new cond. \$24.95


EQUIPMENT WANTED

To meet government and industrial orders we urgently need all types of new and used Test Equipment, Radar, Receivers, and Transmitters. WE PAY HIGHEST PRICES. Tell us what you have.

\$5.00 MINIMUM ORDER ACCEPTED. All shpts. F.O.B. where. Cal. residents add sales tax with remittance. 20% dep. Specify shpg. instructions. Send for FREE Catalogue, No. 112 Note: Max. shipping weight by parcel post is 20 lbs.

UHF TRANSMITTER

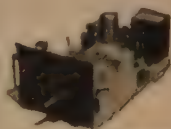450-710 MC. Tunable Transmitter, 10 W. output. Two 308-A type tubes as push-pull oscillators. Wide band video amplifier. Less tubes, with schematic. \$8.95
Excellent condition



R. F. MODULATOR

Complete Tunable 205 MC. Test Set. With 110 V. 60 cps. power supply, 3-stage audio amplifier. Terrific chassis for experimentation. With schematic, \$9.95 like new.....



INTERPHONE AMPLIFIER BC - 709 - B

A 2-position single stage audio amplifier. Uses 1 tube and operates from self-contained batteries. With instruction Manual \$9.95 and Schematic, NEW (less batteries)



TS-10 SOUND POWERED HAND SET
USED Excellent condition \$14.50
Per PAIR Only.....

Mailing Address: P.O. Box 3878-Q N. Hollywood, Calif.
Office-Warehouse: 7460 Varna Ave., N. Hollywood, Calif.
PHONE: Poplar 5-1810 CABLE ADDRESS: ArrowSales

ARROW SALES, INC.

New ...

Master Mobile


Does It Again!

FINEST HY "Q" ANTENNA COILS 20-40-75 METERS

AMATEUR - CIVIL DEFENSE - DEFENSE NETS -
FIRE - POLICE - UTILITIES - INDUSTRIAL -
- FORESTRY

Features Never Equalled:

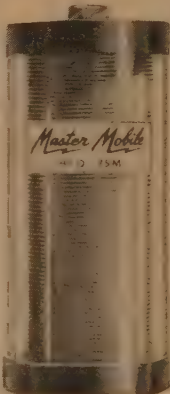1. HIGHEST "Q" POSSIBLE TO OBTAIN.
2. FACTORY PRE-TUNED. Minor adjustments necessary—ready to install.
3. RUGGED—with precision construction throughout.
4. AIR SPACED COIL WINDING—to guarantee finest transmission and reception.
5. LIGHT WEIGHT: 20 M—7½ oz. 40 M—11 oz. 75 M—12 oz.
6. EYE-APPEALING APPEARANCE. Beautiful, crystal-clear transparent plastic Tube Covers. High finish black Bakelite End Caps—easily removable.
7. COILS only 2½" diameter. Minimum wind resistance.
8. COILS PROTECTIVE COATED with Glypto—disposes of moisture interference.
9. INSTANT COIL INTERCHANGEABILITY—with NO LOOSE CONNECTIONS at any time. Just unscrew the Whip and CHANGE the Coil. INTERCHANGEABLE with all MASTER MOBILE Antennas and Mounts.



75 METER
COIL SHOWN

20 METERS	40 METERS	75 METERS
3½" x 2¾" Dia.	6½" x 2¾" Dia.	7½" x 2¾" Dia.
Weight only 7½ oz.	Weight only 11 oz.	Weight only 12 oz.

AMATEURS NET — \$6.95 EACH

SOLD BY LEADING JOBBERS

Master Mobile Mounts, Inc.

P.O. BOX 1817 · LOS ANGELES 36 CALIFORNIA

WAREHOUSE AND SHIPPING ADDRESS · 1306 BOND STREET

LOOK! Don't Miss These Guaranteed SPECIALS!

Vert. Whip Sectional ANTENNAS,
16 ft. \$2.45; 24 ft. \$3.95; 32 ft. \$5.25
METAL CABINET, brand new, 13½"x9¼"x6", with louvers,
less front panel: 75¢
METERS—2" 0-1 Ma: \$3.75; 0-500 Microamp: \$5.85,
all sizes available.
DYNAMOTORS, new PE-101C: \$4.50; CONVERTED 6V
input 300V-100MA, etc. \$9.50
SELENIUM RECTIFIER, Small bridge type, 115 V.A.C.
15 Ma. \$1.25
SENSITIVE RELAYS,
Sigma 4F: \$4.50; BK-35 Kurman \$4.25
CHROME SPEAKER BAFFLE and 5" PM SPEAKER (table
mdl jukebox) used \$1.95
HAYDON SYNCHRONOUS MOTOR—60 cy., 24V., (110
AC, with cond.) 5 RPH \$1.25
DYNAMOTORS: 6V., Inp.-300/150 MA \$9.50; 6V.-180V/
100 MA \$7.95; PE-101 \$4.2
10-20-40 M Sectional Molyb. Steel Whips for GRND PLANE
ANTENNAS

FREE C-366 Jackbox with \$10 order—Catalog C
GYRO ELECTRONICS, Dept. C, 325 Canal St., N.Y. 13,
Worth 6-1290

DX NEWS

(from page 32)

reach 216. CE0AA gave Ben an even 200 on pho
... PY2CK went to 244 with MP1ABW, CE0AA, ZC5
and VQ7UU. Don Jayme now tops the "phone on
section with a comfortable 222! ... W3KT hoisted hi
self to 242 with such as ZS9G, VS9AD, VQ9UU, CE0
and VS5ELA. Jesse came up to date with seven
phone to reach 164 ... W8NBK tacked on VS9UU
No. 241 while W3EVW also hits 241 with CE0
VQ7UU and VQ9UU. Rogers A3 CE0AA QSO gr
him No. 163 in this category ... W2AGW and W6S
both landed on 240 with Howy adding VS9UU and Fr
nabbing CE0AA and JZ0KF ... Luis gave W6CYI
No. 214 while G8IG climbed to 211 with KA0IJ, CE0A
VQ7UU and VQ9UU. Berts phone score went to
with KA0IJ ... W6PZ added SP1KAA for 170 wh
W6ID reported 143 with VS2AL and CE0AA ... W6E
came up to date with six additions to reach 136
W8KIA now tops the 39 zoners with 237 the latest be
CE0AA and VQ7UU for Glenn.

W2WZ goes to 229 with CE0AA, CR5SP and VQ7U
... Egon, 4X4RE, climbs to 225 with assists from L
AC8NP, VQ7UU, CR5SP and VQ9UU while Nor
WIHX, makes it 217 with CE0AA ... Mike, W9FF
adds ZC5VS, CE0AA, FK8AE and I5GO to reach

W4GG also goes to 211 with FG7XA, FB8I
CE0AA and MP4BU ... W3DKT is just behind w
210 after adding CE0AA while EV, KP4KD, rises
203 with Luis and VQ7UU ... Luis also hel
W9HUZ to 197 while VE3AAZ came up to date w
ten additions giving Bill 192 ... Roy, W6LW, ce
brated forty years of wedded bliss by hocking PK61
for No. 192 ... W9ABA added such as LZ1KPZ, CR64
HC8GI, CE0AA and ZC4IP to hit 174 while W6T
went to 144 with CP1BX, CE0AA, LU4ZI and VS2
... W3WU added five to reach 162 and W4EPA mo
to 146 with VQ1RO and FQ8AR ... OE1FF made
144 with CR6AI and SV0WP/Crete ... W2ZVS reach
158 with VP8AJ while Jim, W5FXN, went to 155 w
ZK2AA and CE0AA ... Ned, W1RAN, upped to
with SV0WG and Luis as Luis gave W6ZZ, No. 130

Lou, W1MCW, jumped to quite a lead in the 86 ze
A3 section when VR3C, CE0AA and KC6AA gave l
206! ... Winners in the Swiss, USKA, contest of 1
April outside of Europe were as follows: W1BFT, W2V
W1RY, OD5LC, WIHA, W2DKF, W1RAN and EA9J
... W8YIN added some nice ones in LZ1KPZ, CE0A
3A2AY, FK8AO and VQ1RO to reach 164. Mickey pla
to QRO his 150 water when he reaches 200 ... W2Q
went to 103 on 7 Mc. with ZK1AB, LU4ZO and CE0A
Howy also remains at 103 on 3.5 Mc. ... KP4
read his DUF's I, II and III and seeks an Asian F
IV. Ev also holds the "WPR-N" Certificate issued
contacts with ten WP4's, CW-to-CW, this takes plen
of patience! ... DL4AY, ex-W6HJP, slowly approach
the 100 mark with his 75A-2/32V-3 combo ... W6A
worked CE0AA on 4 bands CW and 3 bands pho
Don says Luis spent much time CQ'ing during the l
day so he figures that all the "serious minded" DX'
had surely worked him ... Congrats to Stew Pe
on his 160 meter W.A.C. which we believe is the fi
of its kind with EK1AO, ZC4XP, EI9J, KV4AA, HC1J
and ZL1AH. This was completed when WIBB QS6
ZL1WW, ZL1AH and ZL3RB at 1025 GMT August
... OE1FF received his BERTA Diploma ... N
certificates at W3EVW include WAP No. 59, WA
No. 450, WAJD No. 57, AAA No. 67 and WAA No.

W6BYB pulled in KS6AB and JZ0KF to reach 7
while Lou, W9ESQ, pulled in such as VK5JE, ZS6A
LU5ZO and FT5HP on 7 Mc. and ZB1CU, CR66
EA0AB, YI2AM and TF3AB on 14 Mc. ... KV4
keyed with YO3RF, CR7IZ, VQ7UU, VQ9UU, I5U
VS9UU and JZ0KF and 12 JA stns. Bill's mike
counted for such as ST2NW, ZB2I, KA9IJ, KR6A
ZD2S, MP4K, ET2LV and ET2ZZ ... W9FID made
217 confirmed with the arrival of CE0AA's card wh
W4ZAE nabbed HZ1AB on 060 ... W6QL added FK8A
030, and FP8AP, 012 ... G6YQ celebrated Aug. 23
working AC4NC, 118, at 1730 GMT and AC3SQ, 093,
1700 GMT ... The 160-meter band keeps in the ne
with the report of QSO's between VP4LZ and W2GG
W4KFC/W9NH on September 4 ... VE2WW hook
ZL2BG and ZL1CI on 3.5 Mc.

Fifteen Meters

After a two month summer's lull this band is rea
coming back with a bang and we look forward to "t
greatest activity ever" during these fall and win
months ... SV0WE was No. 61 for KP4KD. Oth
worked were EA9AP, ZP9AY, FA8CR, OD5BH a
YN1AA ... G6ZO made it 84 with ZD4BN (all Q


talk about a beating!

multiplex radio telephony systems must take it...

that's why REL specifies

CHICAGO


World's Toughest Transformers

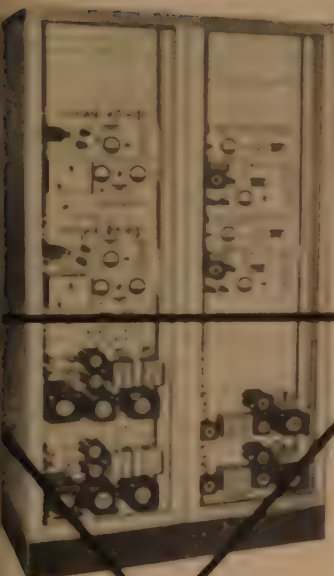

Illustrated at right: REL
900 MC Transmitter, Series
707-757. Illustrated immediately
above: REL Model 759 70 MC
Dual Transmitters and Receivers
These systems make wide
use of CHICAGO C-Type
"Sealed-in-Steel" transformer units.

Free CHICAGO Complete Line Catalog

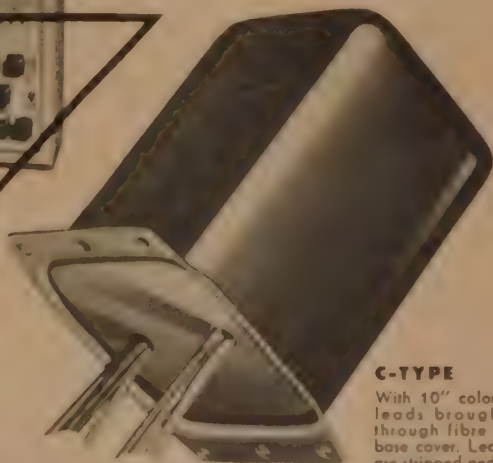You'll want the full details on all
CHICAGO "Sealed-in-Steel" New
Equipment Transformers and com-
plete replacement transformer
lines. Write for your free Cata-
log today, or get it from your
electronic parts distributor.



C-TYPE

With 10" color-coded
leads brought out
through fibre board
base cover. Lead ends
are stripped and tinned
for easy soldering.
Flange-mounted unit

CHICAGO STANDARD TRANSFORMER CORP.


3301 W. ADDISON STREET, CHICAGO 18, ILL.



Export Sales Div.:
Scheel International, Inc.
4237 N. Lincoln Ave.
Chicago, Ill., U.S.A.

CABLE ADDRESS:
HARSHEEL

PIONEER CHASSIS PUNCHES

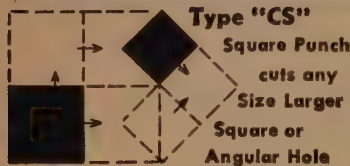

★
For mounting IF's, Terminal Strips, Sockets, Plugs, Meters, Controls, Xformers, Switches, Panel Lites, Etc.

■ SQUARES	● ROUNDS	Simple Hand Wrench Screw Action	
3/8 \$2.95	1/2 } \$1.95	1 1/4	\$2.30
1 1/8 \$3.25	3/4 } \$1.95	1 3/4	
3/4 \$3.50	7/8 } \$1.95	1 7/8	
7/8 \$3.85			
1 \$3.95			
● KEYED			
1 1/4 \$3.50	1 1/4 } \$2.15	1 3/8	\$2.60
	1 1/2 } \$2.30	1 1/2	\$2.95
	1 3/4 } \$2.30	2 1/4	\$5.65

"AT YOUR FAVORITE DISTRIBUTOR"


PIONEER TOOL CO.

LOS ANGELES 16, CALIFORNIA



TIRED OF BEING THE TVI VILLAIN?

IF YOU'RE tired of causing TVI in your neighborhood, take a leaf from the book of engineers designing Air Force electronic equipment and find out about METEX ELECTRONIC WEATHERSTRIPPING. Made of resilient, compressible knitted wire mesh, METEX TVI-20-S seals rig openings to RF leakage just as regular weatherstripping seals doors and windows. If you're worn out from wrestling with innumerable latches, screws, bolts and other clumsy closure methods—and still not getting satisfactory results, INVESTIGATE METEX TVI-20-S TODAY! If your supplier doesn't have it, write us direct.

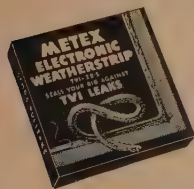

METAL TEXTILE CORPORATION

KNITTERS OF WIRE MESH FOR MORE THAN A QUARTER CENTURY

Roselle, New Jersey



(from page 52)

... KV4BB has connected several times on A3 with ZD9AA, 21220, 1400/1600 GMT ... W6ZZ nailed No. 46 with CE0AA on CW. Miles also A3'd with such as CEIBE, HCIMB, ZP5DC, VK9GW and TI3LA ... DL7BA went to 82 with CN2AP ... TI2TG nabbed OKIHI for No. 76 and reports that the OK stations can work this band during contests ... DL3RM now assumes the 21 Mc. lead with a remarkable 92! ... YOSLC continues action on this band ... W2WZ goes to 61 with HCIMB, ZD9AA, PJ2AA and IS1FIC ... KV4AA added HC1JW, OD5BH, CE0AA and ZP9AY for 63 ... G3GUM's No. 80 was SV1SP!

Here and There

ON4DB is now OQ5GU ... Some DM2's, Russian zone Germans, have been licensed. Notable among them is Heinz, DM2ABL, who runs 200 watts. See QTH's ... George, W6BIL, changed QTH to the country and hopes to have a full grown antenna farm for the contest ... W4GG's kw. is now happily free from TVI. GG nabbed VQ4NZK who is W6NZK ... W3KT nabbed VS9UU as insurance while waiting for VS9AD's QSL ... OE1FF seeks QSL's from FM7WF, CR7AD, HP1LO, HZ1AB, ZD1PW and MD4BPC. Any help? Frank may be reached via HB9IZ ... VK3KF regrets to advise that EL2P was lost in an aircrash on way home to Ottawa from Liberia. This voids chances of QSL's ... From W3RGQ we hear that a group of W stations will be on for any 160-meter DX each Thursday and Sunday from 0500 to 0700 GMT. Oct. 1st and 4th will be the first week periods. Any info on 160-meter DX may be forwarded to W3RGQ where it will be re-issued in a bi-monthly bulletin ... GM3EYP, ex-VP8AP, should soon be on with a TVI-proof 150 watt rig and a four-element rotary.

VE3AAZ seeks the whereabouts of W6CR/KC6, Palau, QSO'd in July '49 ... YN1WC, ex-W6EWC, suggests the gang watch 3999.25 kc. for what is probably the only SSB station in Central America. Wayne runs 400 watts to a pair of 813's in a linear that really gets out even through summer QRN ... W1RAN advises that DM2ABL will act as QSL Mgr. for the DM2's. See QTH's ... PA0FD is now 2nd op at PJ2AK. Dick will soon have his own PJ2 call. Six new PJ2's have passed their exams and will soon be allotted calls. Included were a OM/XYL team, the H.C. Waits (Thanks to PJ2AJ for info) ... Fred, ex-W5AGB/FM, KF3AA, says several of his QSL's seem to have gone astray covering North Pole QSO's prior to Jan. 6, 1953. He will be glad to replace upon request. See QTH's ... CT1CL advises that any CR3 station that has been worked has not been legal. It is hoped that CR8AB will be active in the near future.

DL7BA received his DUF IV ... DL7AP was advised by JA5AB that prewar J5CC was killed in Burma during the war ... C3BF will soon return stateside and will answer QSL's sent to W1WAY ... W2BIV sent in QSL's for DXCC ... Bill, W9GKK, now holds K6CEF. He works for Collins in Calif. ... Burt, ex-KG4AF, christened his new call, W4BQY, with a KV4AA QSO. Burt should be on with the kw. by now and working on his third DXCC! ... W4NWW is back on again after slight alterations to his gall-bladder ... W3VES is now W1ZDP. Phil is Rod Newkirks b-in-law ... From W6AM we hear that W7SAB skeds FK8AO each Sunday at 2300 GMT ... W3GRF now sports a wide-spaced 14 and 21 Mc. beam in same boom ... HB4FF was worked on 008. He says he is HB9PO operating from a Swiss Military station in Bulach, Switzerland ... KG6AUA will be active on 21 Mc. ... Several recent EA9DC QSL's have not been credited by ARRL. They are investigating to find out if EA4BH has EA9DC's log. This news came from W8HW ... W0ELA advises he will very probably go back to the Orient next spring or summer. He will attempt to put some rare southeastern Asian country on the air. He also may return to Brunei for the benefit of those who missed out last time. Plans are indefinite at this time but we will keep you informed ... YN1AA sent out over 800 QSL's in August. Thereby bringing himself up to date ... We are glad to see W6DBT going strong again after a bit of ticker trouble ... KJ6AC was QSO'd at Port Arthur, Tex. as W4DGW/5 ... W8FWO is now K2CBQ in Liverpool, N.Y. ... OQ5VN moved to Stanleyville. See QTH's.

Leo, ex-W6CYX, is now W0QAZ in Denver ... W8TJM got a FCC ticket for calling "9UU" ... See how lucky the rest of us are! The reason was, of course, incomplete identification ... G2MI, via U.R.E., reports that EA9DC has been thrown out of the Society for conduct prejudicial to the good name of Spanish Ham radio

W9TYB, Paul, now ops from 1A4TG. Bill W3RY, is going strong and may be better remembered as ex-KH6VP and K6CU. He will be there for ten months.

Latest QSL Addresses

DM2 Bureau Via DM2AB1, Heino, Lespingerstrat 11, Dusseldorf, R.F.G. Germans.
French R.F.F. Nouvelle QSL, Boite Postal 26, Yverdon, SFO, France.
QSL Bureau Alfredo Cavallio, Box 93, Ambato, Ecuador, S.A.
HC6TG Lucien, Box 505, Mogadiscio, Italian Somaliland, Africa.
IS1V Clark Peterson, Box 223, Coccol, Canal Zone.
KZ5CP Ray, Pago Pago, American Samoa, Pacific.
K84AB Norman Webber, c/o IAL, Juba, Anglo-Egyptian Sudan, Africa.
RT2NW Peter, Box 71, Kisumu, Kenya, Africa.
W4QEH W and VE QSO's via KH6OR.
VR3 Via KH6OR.
VR4AF R.A.F. Detachment, Car-Nicobar, Via P.O. R.A.F. Change, Singapore.
VU3AB QSO's before Jan. 6th '53. Fred White-side, Box 143, Oakdale, La.
W5AGB/FM W0MLY, ex-HZ1MY etc.— Dick McKercher, Box 185, Perry, Iowa.
KF3AA Thanks to W1RAN, W-KIA, KV4BD, W5FFW, VE3KF, KP4ND and the West Gulf Bulletin.
 Issued for January column, Nov. 15, '73's

Dick

EASTER ISLAND

(from page 27)

ZL's, 26 were PY's, 22 were VE's, 7 were VK's and the rest other countries. First contact on 21 Mc. was with W1VNE. First on 7 Mc. was H2ACV and the first on 3.5 Mc. was ZL1HY. The first W on 3.5 Mc. was W6BXL. Ten meters was not used, as that band was closed at all times.


Some of my friends were far from satisfied with single band contacts and many, such as W6AM, W8PQQ, W2QHH, W6SAI, T12TG and W9HUZ were able to raise me on most of the bands used. It would not have surprised me to have received requests to QSY to 2 and 160 meters and I am still wondering why some of these boys did not request QSO's on teletype and SSB!

Contacts sped along at a rate of from 40 to 50 per hour although on August 11th, 61 contacts were logged in an hour. QSO's on 3.5 Mc. and on phone considerably lowered my all-over QSO per hour average, which stood at 21 after 73 hours of operation over the eight-day period.

During a QSO with W6KJR he innocently told me that I was his first CE contact. He probably did not know that he had nabbed Easter Island and not Chile!

Conditions to Europe were fair with G stations predominating. They came through for a two-hour period during most days. I had counted on making contacts with F, I and OZ but none were heard. Africa was represented by ZS6DW and FA9VN while the only contacts in Asia were with 4X4RE and ZC4IP. In all, 53


(Continued on next page)

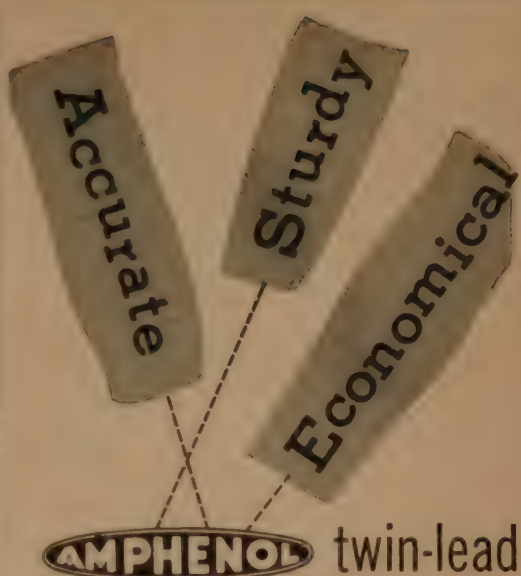

AMPHENOL twin-lead folded dipole ANTENNA

The AMPHENOL amateur communications antenna kit has proved to be very popular with amateurs everywhere. They have found the antenna to be economical in initial cost, efficient in operation and sturdy. Utmost accuracy is assured because the amateur cuts the antenna to the specific frequency he desires and does all assembly work himself.

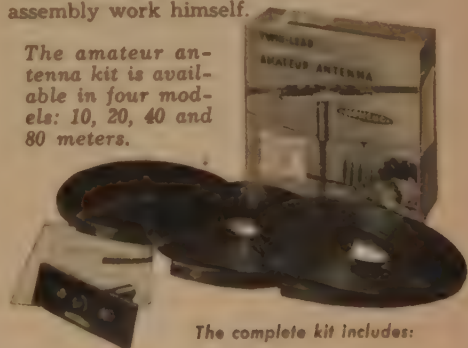The amateur antenna kit is available in four models: 10, 20, 40 and 80 meters.



The complete kit includes:

- 2 lengths of #16 copper-clad steel conductor twin-lead, cut to band length.
 - 1 75-foot length of standard 300 ohm twin-lead for use as lead-in.
 - 1 high strength laminated T-block.
- Assembly and installation instructions.

AMATEUR NET

10 meters	\$5.35	40 meters	\$ 7.80
20 meters	6.00	80 meters	11.25

see your

AMPHENOL

radio parts distributor

AMERICAN PHENOLIC CORPORATION

BUD LOW PASS FILTER

LF-601

REDUCES OR ELIMINATES TVI FROM AMATEUR TRANSMITTERS

Interference to television receiver reception caused by transmissions from an amateur station can be caused by harmonics from the transmitter. They can be eliminated or greatly reduced by the use of a Bud LF-601 low pass filter. Minimum attenuation of 85 decibels on all frequencies above 54 megacycles and a minimum of 93 decibels above 70 megacycles. Can be used with either 52 ohm or 72 ohm coax. Cut-off frequency is 42 megacycles. Maximum rejection is adjustable from 55 to 90 megacycles. The Bud LF-601 low pass filters have many other features. See them at your distributors today or write for literature.

Amateur Net - \$13.95

BUD RADIO, INC.

2118 E. 55th St. - Dept. Q - Cleveland 3, Ohio



Allied's new "Ham Shack Extraordinary"

We're not ones to boast, but we can't resist passing on what several thousand visiting Hams have said in the past few weeks about our new home and about the Shack in particular. "Terrific," "A Whole Ham Show in itself," "What a setup!" These are typical comments. We think it's something to see—so if you're out our way or coming through, we know you'll get a bang out of a look-see. And if you're doing business with us by mail, you'll get personal "Shack Service"—just as if you'd come in yourself . . . By the way, have you got your copy of our new 268-page 1954 Buying Guide? It's the most complete yet—everything in station gear and electronic supplies. Write for it: Allied Radio Corp., 100 N. Western Ave., Dept. 16-L-3, Chicago 80, Illinois.



(from preceding page)

countries were worked with the first station in each being as follows: CE3AB, CP5EK, CT1C, CX1CA, DL6IC, EA2CA, EI2T, FA9VT, FO8AI, G4CP, GI5UR, GM3DHD, GW3Z, HB9X, HC2LF, HC8GI, HP1TS, HR1A, I1BLF/T, IS1AHK, KH6MG, KL7PI, KP4A, KV4AA, KZ5CP, LU7TA, OA4C, OE1C, OK1MB, ON4AU, PA0UN, PY3DZ, TI2T, VE7VC, VK7KD, VP1AA, VP5AR, VP9B, VR2AS, W6GDJ, XE1IQ, YN1AA, YS1Q, YU1AG, YV1AA, ZC4IP, ZK1AB, ZK2A, ZL2FA, ZP5CF, ZP6DW, 4X4RE and 9S4A.

At noon, August 15, we received our departure notice and after a QSO with my own station, CE3AG, the big switch was pulled. 116 contacts had been made on CW and 375 on phone.

It may be said here that although the bad weather caused us much inconvenience it was responsible for my staying on Easter Island for eight days instead of the four or five days originally planned. Rough seas made unloading of the "ANGAMOS" a slow and difficult task.

Difficulty with the electric plant probably came about a hundred contacts but after I took time out to thoroughly clean the carburetor it went well. An unfortunate moment came for



Location of CE0AA on Easter Island showing antenna supports.

lowing a QSO with W8RLT when a nervous reflex on my part sent the D-104 mike crashing to the floor, shattering the crystal. Another crystal mike was obtained from the PA system on the island to carry on the phone work. The Collins 32V-2 and 75A-1 worked beautifully all times in spite of the rough voyage and handling.

Late in the afternoon of August 15, I bid adieu to the kind people of Easter Island after a hazardous trip to the "ANGAMOS" was able to haul my battered body and equipment, including the all-important log, up the swaying rope ladder without mishap.

At this point my ambitions to put CE0AA MM on the air were zero-minus. After a two-day rest, however, wild horses could not have help me back and CE0AA/MM was set up in the

dispensary with the enthusiastic assistance of all on board. At 9:20 a.m. on August 18, CP5FK was contacted at the first of some 200 QSO's from CIOAA MM.

During the next seven days the operation of CIOAA MM enabled all the passengers and most of the ship's officers to hold phone QSO's with their wives, children and mothers on the mainland and I assure you I was the most popular man aboard. Many stations were also contacted who had worked me from the island and their kind remarks regarding the expedition were most appreciated.

At last we arrived at Valparaiso on August 25 after a thirty-two day absence, and I set foot on shore with a happy heart and with the overwhelming satisfaction of knowing I had successfully carried out my ambition to put Easter Island on the Ham map. This has been a privilege I am proud to have had and marks the high spot of my amateur career. It also coincided with my 30th year in Ham radio.

To Commander Lira, to the Captain, crew and passengers of the "ANGAMOS" and to the Easter Islanders, go my heartfelt thanks for the kindness and cooperation which made my trip a success. I know this feeling is shared by fellow Hams throughout the world.

My thanks also go to those Hams who sent contributions. These will be used to establish a permanent station on Easter Island with the probable call letters of CIOAC. Most of you should have received your CIOAA QSL's by this date. We had 2,000 printed and are able to take care of everyone who contacted us including requests from SWL's. So—If that card is missing, let us know.

A 522 ON 220 Mc.

(from page 57)

for the purpose of connecting to the 832A plate pins. It will be found that the use of these small diameter wires will necessitate cutting down on the effective size of the tank coils, thereby lowering efficiency appreciably.

Summary

This completes the modification and no trouble should be experienced in tuning up the rig. The tuning dials should fall about half scale and as previously mentioned, the meter readings should be about the same. Power output on 220 Mc. as observed on a 25-watt lamp bulb was just about the same as on a 144-Mc. unit and if the modulation equipment is being used, the rig should modulate approximately the same as on the lower band.

All articles should end up by listing the

(Continued on next page)

to the

E.E. or PHYSICS GRADUATE

with an interest

or experience in

RADAR or ELECTRONICS

Here is
what
one of
these
positions
offers you

Hughes Research and Development Laboratories, one of the nation's large electronic organizations, is now creating a number of new openings in an important phase of its operation.

OUR COMPANY

located in Southern California, is presently engaged in the development of advanced radar devices, electronic computers and guided missiles.

THESE NEW POSITIONS

are for men who will serve as technical advisors to the companies and government agencies purchasing Hughes equipment.

YOU WILL BE TRAINED

(at full pay) in our Laboratories for several months until you are thoroughly familiar with the equipment that you will later help the Services to understand and properly employ.

AFTER TRAINING

you may (1) remain with the Laboratories in Southern California in an instruction or administrative capacity, (2) become the Hughes representative at a company where our equipment is being installed, or (3) be the Hughes representative at a military base in this country—or overseas (single men only). Adequate traveling allowances are given, and married men keep their families with them at all times.

YOUR FUTURE

in the expanding electronics field will be enhanced by the all-around experience gained. As the employment of commercial electronic systems increases, you will find this training in the most advanced techniques extremely valuable.

How
to
apply

If you are under 35 years of age and have an E.E. or Physics degree and an interest or experience in radar or electronics,

write to

HUGHES


RESEARCH AND DEVELOPMENT
LABORATORIES

Scientific and Engineering Staff
Culver City,
Los Angeles County, California

Assurance is required that the relocation of the applicant will not cause the disruption of an urgent military project.

NEW MOTOROLA

Home Unit Monitor Receiver

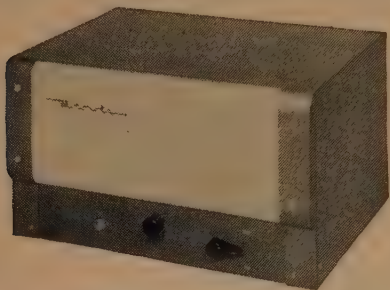

Now available—the new Motorola Monitor or Alert Receiver, for operation in the 25-50 mc. and 152-174 mc. ranges. Optional selective signaling, emergency 6 VDC power supply, and red-yellow-blue-white light alert cabinet attachments. Ideal for amateur, as well as public safety, civilian defense, industrial and commercial radio systems.

For further information write to:

Motorola®

Communications & Electronics, Inc.

Amateur Sales Dept. - CQ - 11

1327 W. Washington Blvd., Chicago 7, Illinois

Attention: Harry Harrison, W9LLX, Tel. Taylor 9-2200—Ext. 161

LIMITED QUANTITY

NOW AVAILABLE



NEW PANADAPTOR PCA-2

This invaluable visual signal observer is rapidly becoming impossible to get. Order yours TODAY while we have a limited supply to fill immediate requests.

NEO-TECH PRODUCTS, INC.

14 SOUTH SECOND AVE., MOUNT VERNON, N.Y.

For complete information WRITE now for a descriptive folder.

(from page 57)

superb DX worked with the equipment described. Well, why should a VHF man not have this privilege? The first QSO using this BC-625 gismo resulted in breaking the then world's record with W5ONS on 220 Mc.

SERVO MECHANISMS

(from page 16)

swung more than 180 degrees, the antenna will rotate in the opposite direction; therefore a habit of swinging the *controller* more than a half turn could soon result in the feeders being torn off, in spite of the stop.

To prevent the antenna from rotating in the opposite direction, first turn the *controller* slightly less than a half a turn. Allow the antenna to rotate far enough, so that an additional rotation of less than 180 degrees will put the antenna in the desired position; then bring the *controller* to the final position.

A normally closed "limit" switch in each motor lead will give positive protection against tangling the feeders. There are a pair of them in the AYLC 1591 motor that must be removed. They may be remounted externally for this purpose.

Although my antenna can only be rotated about a revolution and a half without damage to the feeders, I never relished the thought of having to swing a beam 340 degrees to achieve a net change in position of twenty degrees. Therefore, I use no method to limit rotation. So far, I have never wrapped up the feeders. One reason may be that it is easy to inspect them, if I suspect that they are twisting.

DX ANTENNA

(from page 23)

Mc., because it is somewhat shorter than a quarter-wave, its efficiency is reduced, but it does put out a very good signal both locally and at distances of several hundred miles. At night on 3.9 Mc., we have worked stations over 1,000 miles away with this antenna, in the Western U. S., and the West Indies, from W4RXO.

Now for a word about TVI. This antenna definitely helps that situation. In the first place, it is fed by coaxial line, which is buried underground from the transmitter out to the tuning unit. Use of coaxial line enables us to insert a low-pass filter in the line as it leaves the transmitter. If any harmonics do get by the filter they are discriminated against by the antenna

(Continued on page 60)

Johnson **BI-NET**

FULLY AUTOMATIC

Mobile Dual Band Antenna Resonator

- one antenna
- two bands
- no switching

Dual mobile antenna loading network for 10 and 20 meter amateur bands. Mounted in the center of a standard mobile whip antenna, it enables the operator to change bands while in motion. Operation is completely automatic, no relays nor mechanical control required. After initial adjustment, the BI-NET requires no further attention. Now, for the first time, true bandswitching mobile operation is attainable.

The BI-NET is a tuning network consisting of two adjustable, low-loss inductors and a ceramic insulated fixed capacitor. Inductors are silver plated for maximum conductivity. The assembly is enclosed in a streamlined, weatherproof plastic housing and is equipped with $\frac{3}{4}$ " x 24 female threads at each end for antenna mounting. Overall size, 4-7 16" high, 5-5, 16" long, 2 $\frac{3}{4}$ " maximum width, weight 14 oz.



AMATEUR NET

\$10.95

Catalog Number 250-22

PATENT
PENDING


E. F. JOHNSON COMPANY

220 SECOND AVENUE SOUTHWEST

WASECA, MINNESOTA



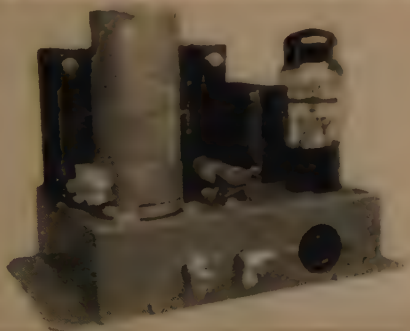Now Available . . . MOBILE POWER SUPPLY KITS



6-volt **\$29.50**
input

12-volt **\$31.50**
input

Wired and tested — \$7.50 extra

Nothing else to buy—these KITS include all hardware, pre-punched chassis and base, rectifier tube, heavy duty vibrator, etc. for immediate shipment.

PALCO ENGINEERING, INC.

150 West 75th Street

Indianapolis, Indiana

- Power Supply for mobile or marine transmitters
- Designed by mobile equipment engineers
- High efficiency with lower battery drain
- Output 500 volts filtered d.c. at 225 ma.
- Does not require high current switching
- Instant start and stop. No waiting for voltage buildup or coasting down as in rotary equipment.
- No battery drain while on receive or standby
- Special heavy duty communication type vibrator for dependable long life.
- Properly designed filter assures very low ripple
- Fully detailed assembly and wiring instructions with each KIT
- Small, compact, rugged construction

BUY OF A LIFE TIME!

TRIED AND PROVEN THE WORLD OVER



LETTINE MODEL 240 TRANSMITTER WITH MOBILE CONNECTIONS AND A.C. POWER SUPPLY

This outstanding transmitter has been acclaimed a great performer throughout the world. It is excellent for fixed station, portable or mobile operation. Even if you have a transmitter of your own you can't afford to miss this wonderful buy, direct from our factory, ready to operate.

The 240 is a 40 to 50 watt Phone-CW rig for 160 to 10 meters, complete with: (8 x 14 x 8) cabinet, self contained A.C. power supply, MOBILE connections, meter, tubes, crystal and coils for 40 meters. Tubes: 6V6 osc., 807 final, 6SJ7 crystal mike amp., 6N7 phase inverter, 2 6L6's mod., 5U4G rect. Weight 30 lbs. TVI instructions included. 90 day guarantee Price \$79.95.

\$25. deposit with order—balance C.O.D.
80, 20, 10 meter coils \$2.91 per set. 160 meter coils \$3.60
Also for CAP, Broadcast, MARS, Marine, State Guard; Novice.

LETTINE VFO & ANT. TUNER NOW IN STOCK

LETTINE RADIO MFG., CO.

62 BERKELEY STREET

VALLEY STREAM, N. Y.

*Keep Your
Shack Neat
with a*

BOUND VOLUME

You'll appreciate the handy convenience of this compact volume of the 1951 or 1952 issues of CQ . . . handsomely book-bound in tan colored cloth . . . distinctive gold foil lettering embossed in a black panel strip . . . available NOW!

\$7.95

in U. S., Canada and
Pan-American
Union. Others,
\$1.00 more.

CQ MAGAZINE

67 West 44th Street New York 36, N.Y.

(from page 58)

itself, because as we go above 0.58 wavelengths in length, the radiation from a vertical antenna shifts from low to high-angle, where it can't do any harm to your neighbor's TV picture. The 21-Mc., drooping ground plane also discriminates against harmonics because of the mismatch which occurs at harmonic frequencies between antenna and feed-line.

And there you have it—a four-band antenna which takes very little space, which is neat in appearance, and which is easily erected. Comments and questions from readers will be welcomed.

PROPAGATION

(from page 45)

ionosphere to tilt so that they deviate considerably from being parallel to the earth, thus causing a transmission to be scattered in many directions rather than being normally reflected along its great circle path. Additionally, because of the tilt of the horizontal reflecting surfaces, the signal arriving from one direction will strike the reflection surface at a different angle than will a signal arriving from the reciprocal direction. This produces different reflecting characteristics and scattered signals of this nature do not usually obey the laws of reciprocity, and may result in "one way skip." "One way skip" due to scattering can usually be detected by the weakness and characteristic flutter or warbly fade associated with scattered signals. Scattered signals also usually arrive from directions that seem to bear no visible relationship to the direction of the transmitting station.

Scattering can take place from the regular layers of the ionosphere, Sporadic E layer, from Auroras and also from ground reflection points.

"One way skip" is therefore usually attributed to the geographical variation in atmospheric noise levels or scattering from irregular surfaces.

Thanks to all of you who have taken the time to send me comments regarding "DX and the Sun" which appeared in the July and August issues of CQ. It is gratifying to know that the article was found to be helpful in explaining some aspects of the mechanism that makes it possible for us to transmit radio signals over great distances.

THE NOVICE SHACK

(from page 50)

line similar to the one in the picture, although it may be much shorter than that one.

To tune a sixty-five foot antenna on 3.7 Mc., connect the stator of the condenser to one end of the coil, its rotor to ground, and the antenna to the other end of the coil.

If you wish to tune this antenna to 7.2 Mc., or a 130-foot antenna to either band, connect the condenser across the coil, grounding the rotor end, and connect the antenna to the stator end.

Tuning with either arrangement consists in adjusting the antenna condenser for maximum plate current, then returning *CI* for the "dip" in plate current, varying the number of turns in *L2* to vary loading. Use the minimum number of turns that will permit drawing the desired current.

(Continued on next page)

Letters And General News:

FCC Nabs KP4 Novice While Pirating Other Calls

The Spring and early summer issues of "Ground Wave," the monthly bulletin of the Puerto Rico Amateur Radio Club contain several references to some "lid" appropriating various KP4 call letters. But the pot really boiled over in July when the FCC moved in and apprehended the culprit. KP4ZZ, KP4ES, KP4MU, KP4OB, KP4JM, KP4CP, KP4QS, etc., was Novice Licensee WP4TQ!

Charges facing WP4TQ include: Novice licensee using a VFO, operating on a frequency not assigned to Novices, Use of fictitious call letters, and failure to maintain a log of operation. The four alleged violations occurred on ten known days. Section 502 of the Communications Act of 1934 provides a fine of up to \$500.00 a day per violation upon conviction, plus suspension of license. Enough said!

If any comment on the above is required, WP4TQ made it. He was assuring the station he was working thusly: "They'll never catch me. I'm too smart for them." At that moment "they" knocked on the door of his shack.

More pleasant news from Puerto Rico is the announcement by the P.R.A.R.C. that they are now issuing a special WPR-N (Worked Puerto Rico Novices) certificate to any station submitting proof of two-way radio contact with ten Puerto Rico Novices, using CW emissions only. Once the certificate has been won, stickers will be awarded for proof of contact with additional P.R. Novices in blocks of ten.

Mail confirmations with return postage to Puerto Rico Amateur Radio Club, Inc., P.O. Box 3533, San Juan, P. R.

They say confession is good for the soul, so here goes. A few weeks ago, I received a postal card from a Novice listing the call letters of the DX stations he had worked on 21 Mc. Sad to say, the card immediately disappeared. If the writer of the card sees this, I offer my congratulations on his fine work of contacting DX on 21 Mc. in the middle of summer when conditions were supposedly the poorest and my apologies for mislaying his card. For what it is worth, the only call letters on the list that I recall are those of TAZEPA (Turkey).

KN2EPZ writes, "Talk about premonitions! The night before I got my ticket, I dreamed that I got the call KN2EPZ. The next day my ticket arrived, and my call is KN2EPZ! I have eleven people who will verify the truth of this story. 73"—Wait, KN2EPZ.

Dan, K2BVQ, writes, "Dear Herb, I received my General ticket last month, so KN2BVQ is gone forever. Tho my call is changed, I'm not. I am still active on Novice 40. My twenty watts and my 8-20R (plus audio filter) seem to work best there. As a Novice, I racked up fourteen states and got my code speed up to fifteen w.p.m. But best of all, I made over seventy new friends.

"This letter is written in an attempt to make more new friends. Enclosed is a TVI form letter (Too long to print: Herb). It was gotten out by the Wave Riders, a radio club I am proud to belong to. I would like to extend an invitation on behalf of the rest of the Wave Riders for any teen age Ham or would-be Ham to come to one of our meetings and meet the fellows.

"Clubs are a good way to learn what you must for your new ticket or to learn from the experience of others how to make your procedure top notch. Also, it is easier for a group of people to put up your new antenna than for you to go it alone.

"To date, our club dues are \$0.00 per year. When money is needed for form letters, etc., we hold a voluntary collection among our members. Any who wish to join need only to pick up their telephone and call (in Brooklyn, N.Y.) ULater 8-7143, and ask for Dan—that's me. 73"—Dan Grunberg, K2BVQ, 1518 50th St., Brooklyn 19, N.Y.

Eddy, W5ZBC, gets right to the point. "Dear Herb, I got the 'N' out of my call. Anyone who has traffic for Arkansas and nearby states can call W5ZBC on 7209 Kc. (In the phone band! Herb) between 3:45 and 5:30 p.m., maybe later, 73"—Eddy, W5ZBC.

From Ontario, Neal, VE3BRF writes, "Dear Herb, although I am not a Novice, I am a comparative newcomer to Ham radio. And I like your column in CQ. Been on the air since last September. The very first station I worked was a Novice station—WN2ILQ. Since, I have worked many Novices, being the first VE for many of them.

"I am trying for WAS (worked all states) on '80"

(Continued on next page)

BIGGEST BUY ON MARKET for 2-METER CONVERTER KIT

For those who want to operate on 2-METERS, here's THE BIG BUY YOU'VE WAITED FOR: K & L 2-METER CONVERTER KITS—with or without Power Supply. These enable you to receive 2 meters on a conventional Short Wave Receiver. Especially designed Push-Pull 6J6 R. F. Amplifier into 6J6 Oscillator-Mixer. Balanced line input, coaxial output. All slug tuned adjustments, high quality components. Output frequency is 21 to 25 MC. Highly stable oscillator. . . . Tests show they operate as effectively as many more-expensive crystal units.

These quality K & L 2-METER CONVERTER KITS have ALL necessary components supplied. The Converter is PRE-WIRED excepting the tuned Circuits. . . . Small size: Only 5" long—3 1/4" wide—3 1/2" deep. . . . Anyone with even the slightest experience can complete in a comparatively short time. . . . COMPLETE SIMPLIFIED INSTRUCTIONS SUPPLIED WITH EACH KIT. . . . With proper assembly, WE GUARANTEE satisfactory results.

Can be used for a Mobile 2-Meter Converter into a Standard Mobile Converter by using Model 1 and a separate battery for oscillator tube filaments.

6J6 Tubes (each unit requires 2). **\$1.25** net each.



K & L MODEL 1

K & L MODEL 1 KIT: **\$9.95**
Unbelievably low Wt.: only 8 oz.



K & L MODEL 2—WITH POWER SUPPLY
K & L AC MODEL 2 KIT: **\$14.45**
UNUSUAL PRICE —

Same as MODEL 1 but also includes Complete Power Supply with Instructions. Wt.: Only 24 oz.


K & L RADIO PARTS CO.

PRospect 0553

1406 VENICE BLVD., LOS ANGELES 6, CALIF.
POSTAGE PREPAID ANY PLACE IN U.S. Send check or money order TODAY. No C.O.D.'s. California orders add 3% sales tax.

AT ANY PRICE...

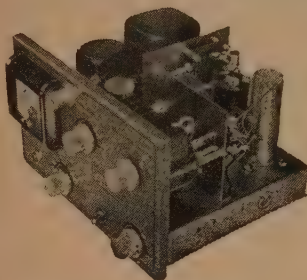you couldn't ask for more in a MOBILE TRANSMITTER!



40 WATT BABCOCK MOBILE D-X MITTER

6 BAND—BAND SWITCHING

- 2 Bands (3.5—7.3 mc) (14—30 mc)
- 2 Crystal Frequencies per band
- Instantaneous Antenna Change-over with LS-1 or LS-2 Units into 8 ft whip

Features:

- Finest Components available
- 6BK5 oscillator
- 6146 final amplifier
- Complete Metering, including Watts output into 52 ohm antenna load
- Small Size—5" hi., 8" wi., 7" d.
- Readily adaptable to mobile or home use.

ABSOLUTELY GUARANTEED

**ONLY \$99.50
HAM NET**

Priced to Gain Volume Sales among Discriminating Ham Operators

**PRICE INCLUDES
TUBES**

Write for Free Literature and name of your nearest dealer.

BABCOCK • RADIO ENGINEERING, INC.
7942 Woodley Ave., Van Nuys, Calif.

Radio Operators!

**THE GUARDIAN
SERIES 200
RELAY...**

Interchangeable
**COIL and CONTACT
SWITCH ASSEMBLIES**
Save Time—Cut Costs!

★ Coil assembly includes coil and field piece. Contact assembly consists of switch blades, armature, return spring and mounting bracket. Standard and Midget contact assemblies in either S.P.D.T. or D.P.D.T. are interchangeable and can be used with any of 13 coils described below.

CONTACT SWITCH ASSEMBLIES

CAT. NO.	TYPE	COMBINATION
200-1	Standard 8 amps	Single Pole Double Throw
200-2	Standard 8 amps	Double Pole Double Throw
200-3	Standard Contact Switch Parts Kit with complete assembly and wiring details	
200-4	Standard 12.5 amps	Double Pole Double Throw
200-5	Standard 8 amps	Double Pole Double Throw
200-M1	Midget 8 amps	Single Pole Double Throw
200-M2	Midget 8 amps	Double Pole Double Throw
200-M3	Midget Contact Switch Parts Kit with complete assembly and wiring details	

13 COILS ASSEMBLIES

CAT. NO.	A.C. COILS—VOLTS	CAT. NO.	D.C. COILS—VOLTS
200-6A	5 A.C.	200-6D	6 D.C.
200-12A	12 A.C.	200-12D	12 D.C.
200-24A	24 A.C.	200-24D	24 D.C.
200-115A	115 A.C.	200-32D	32 D.C.
		200-110D	110 D.C.
		200-5000D	for current type

*All A. C. coils available in 25 and 50 cycles

GUARDIAN ELECTRIC
1604-M W. WALNUT ST. CHICAGO 12, ILLINOIS

A Complete Line of Relays Serving Radio Amateurs

(from preceding page)

and would like to work some of the Novices in the southern states. If any are interested, I would like to arrange a sked. To encourage them, my best Novice DX on "80" was with Betty, WN6QPI (my first YL!), and she was using only twenty-five watts input and a long wire antenna. Fine business indeed.

"My WAS score is thirty-three worked, twenty-five confirmed. Some of my unconfirmed states are in the south. Not Novices, though. I find that they usually QSL 100%. I do too, and that's why I like to work Novices, even at five wpm 73"—Neal, VE3BRF, Box 427, Oshawa, Ontario, Canada.

Don, KN2EGM, has a very common "gripe." "Dear Herb, Well, after a long wait, I have my ticket. I have been on the air for exactly one week and have made about fifteen contacts. Already, I have a gripe. Some of the fellows I ask to QSL reply, 'I will QSL only if you QSL first.' In my opinion, that is being childish and foolish.

"I would like to get in touch with any other Novices in my home town so that we could organize a club. I presume they all read the Novice Shack, therefore, I hope they will give me a call on the air or the telephone. 73"—Don Parker, KN2EGM, 37 Roquette Ave., Elmont, L.I., New York. Telephone: FL 23749.

Richard, KN2DEM, writes, "Dear Herb, I've worked eight or nine states in about two months. I have a Meissner transmitter, running thirty-five watts, an HQ-129X receiver, and folded dipole antennas for 3.7 Mc. and 7.2 Mc. When I operate 3.7 Mc., I use the 7.2 Mc. antenna on the receiver, and vice versa.

"I was thirteen years old today, and I am helping a friend (12) get his Novice ticket. My dad is W2ASI. He has been a Ham for twenty-eight years. 73"—Richard, KN2EDM.

From Roy, WN3WAF, "Dear Herb, I got on the air with the good help of Andy, W3NL. In about two months, I've had about 100 contacts, with fifty-two confirmed. My transmitter uses a 6L6 running twenty watts, and the receiver is an S-40A.

"I live in an apartment and have had some antenna trouble. I would like to hear from anyone with any suggestions. 73"—Roy Goldsmith, 549 Newcomb St., SE, Washington 20, D.C. Phone JO 2-6804.

Help!

Lads requesting help in obtaining an amateur license this month are:

Bill E. Stroud (16), 168 Hamilton St., Plymouth, Mich. (Wants pen pals interested in amateur radio).

Burt Cohen, 183 West Scott, Fond du Lac, Wis. Paul Helmick, Jr. (14), 3323 Dartmouth Circle, Montgomery, Ala.

Edward Jars (14), 21a Richmond St., Philadelphia, Pa. Phone RE 9-1613.

Donald Kellicutt (16), Horton, Mich. Bobby Powell, Drawer #5, Wilson, N. C.

Leigh Littleton, 730 Fairview Ave., Bowling Green, Ohio.

Don R. Ruse, 10091 Brecksville Rd., Brecksville, Ohio. (Also interested in forming SWL correspondence club.)

David Boyd (14), 874 Mill Road, Buffalo 24, N.Y. Tel HO 2013.

Bob Uuholland, 1656 Liggett Ct., St. Louis 19, Mo.

Albert Del Rosario, P.O. Box 152, Kahuka, Oahu, Hawaii.

James G. Wray, 252 Lee St., Hampton, Va. (Has photographic darkroom. Will be glad to develop and print helping Ham's pictures.)

Johnny Ulmer, 7925 Spruce St., New Orleans, La.

Getting back to our letters, Jack, W0KSF, says, "Dear Herb, As a Novice, I worked forty-two states with fifteen watts input. Now I am running ten watts to a Meissner 'Signal Shifter,' mostly on 7 Mc. With it, I have worked Bermuda and Mexico, and several Canadians. 73"—Jack, W0KSF.

Myron Smith, SWL/WN2, comments, "Dear Herb, I notice that some SWL's object to sending postage with their cards. I write letters and enclose postage when I report hearing a station. My friend just sends cards. My percentage of replies is over fifty per cent. His is very low. 73"—Myron, 222 Ames St., Rochester 11, N.Y.

Ex-Novice Jim, W3UXO, writes, "Dear Herb, I do not have a rig of my own now, because I am building a new one that will run seventy-five watts to a 6146. But I operate W3PQT, the club station at the Patuxent Naval Air Station. So far, I have worked thirty-four states and seven foreign countries.

"Regarding the letters you receive from fellows who think they will not like CW when they get their licenses: At first glance, it may seem harder than phone, but the thrill that comes from being able to send and receive high-speed code and the fact that one can get out well with relatively simple equipment means much more to me than operating phone. I operate CW almost exclusively and doubt if I will be on phone for a long time if ever. I have a 25-wpm. sticker and can copy almost thirty.

"I am fifteen years old, and I would like to hear from some YLs about fifteen or sixteen. 73"—J. E. Goldring, W3UXO, c/o Dental Clinic, N.A.S., Patuxent River, Md. Bill, W4TFP, reports what was probably the first Novice operation from a boat. A condensed version of his letter follows: "On October 13, 1951, two friends and I went on an overnight fishing trip in a twenty-one foot cabin cruiser. The cruiser was designed for two; therefore, with three people, plus complete fishing and diving equipment, there was not room for a rig, but that did not stop me.

"There was no 115v. a.c. on board; so I operated the RME 45 and my Novice transmitter from a vibrator power supply and a storage battery. Getting a late start, I just threw the equipment into the cabin until an hour before the schedule I had arranged with W4LMT to notify our parents of our safety. I screwed a twelve-foot collapsible whip on the deck and connected it to the transmitter through a length of bell wire and tuned up. Promptly at 1700, I called W4LMT, who came back with a surprising RST599X report. After handling my traffic and arranging another schedule for the next day, I closed down to conserve the storage battery. It was hard to do, because I heard another Florida station and one in Georgia calling, but I had no choice. The schedule the next day went off with a hitch also, and our parents were waiting when we docked. 73"—Bill, W4TFP. (See picture on these pages for an idea of Bill's present station—Herb.)

Ralph, W9SNMG, writes, "Dear Herb, In eight weeks, I have worked twelve states and Canada. The transmitter runs thirty-five watts, and the receiver is an NC-125. I use a 1/2-wave antenna on 3.7 Mc. and a 3/4-wave one on 7.2 Mc. 73"—Ralph, W9SNMG.

That takes care of our space this month. Keep those letters and pictures coming. 73, Herb, W9EQQ

YL'S FREQUENCY

(from page 43)

guitar. She also plays the mandolin. John and June have always taken part, singing solos or whatever was needed, even when they were very small.

Just to complete the family affair, they offer an award to anyone who works all four of them on the air. It's a certificate called WAB—Worked All Battins. FB, folks, and good luck to all of you!

14th YLRL Anniversary Contest

The annual YLRL Anniversary Party will be held this year in December. The phone portion of the contest is set for Dec. 5th, and the CW portion for Dec. 12th. Details are given in the box. Join the fun and get acquainted with other YLs. Any and all YLs are invited to participate, but only members of YLRL are eligible for awards.


Conventions

The New Hampshire State Convention on Sept. 13th at Concord drew a record turnout of about thirty-five YLs. The photo, for which our thanks to W1FTJ, shows those who attended the YL meeting. Others at the convention included W1MDV and W1WVT, and there may have been more. The YL meeting was directed by Peg, W1BCU, assisted by Esther, W1RYJ. Each YL told a little about herself, including call, bands worked, etc. This was followed by a YL QSL card contest, won by W1OAK for her

(Continued on page 65)

Here's the new **SHURE**
SLIM-X

All-Purpose Crystal
MICROPHONE

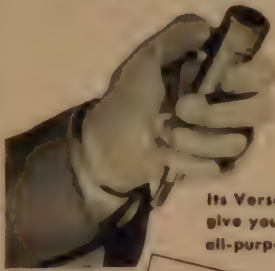

MODEL 777
List Price \$21.00
MODEL 777s (with switch)
List Price \$23.00
(Price includes cradle
for mounting on stand)

Its Versatility and "Hand-a-Bility"
give you an ideal low-cost
all-purpose microphone



LIGHT! The new "777" Slim-X Microphones are rugged little microphones weighing only 6 ounces! They are designed for good-quality voice and music reproduction. Their versatility and "hand-a-bility" make them ideal for use by lecturers, announcers, instructors, and Hams; for audience participation shows; carnivals; panel and quiz shows; and use with home-recorders. When mounted on either cradle or swivel, the "777" can be removed in a flash (no tools necessary)—simply by lifting it out of the holder. This makes it an ideal "walk-around" hand-held microphone.

TECHNICAL INFORMATION: Smooth frequency response—60 to 10,000 c.p.s.; special-sealed crystal element—for long operating life; high impedance; 7' single-conductor cable, disconnect type. Dimensions: (Microphone only) Length, 4 1/2"; Diameter 1". *Finish:* Rich satin chrome overall.


NOTE: Lavalier cord for suspension of Microphone around neck is included.

ACCESSORIES FOR "777"

MODEL S38 STAND is a heavy die-cast base. Includes metal screw machine stud for connecting microphone adaptor to stand base. **List Price: \$3.30**

MODEL A25 SWIVEL ADAPTOR features a long-life, high-quality swivel connector. Is lined with a long-life nylon sleeve—for noise-free and scratch-free insertion and removal of microphone.

List Price: \$5.50

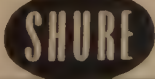

On S38 Desk Stand
With A25 Swivel

CQ

The Radio Amateurs' Journal

The Year Round Christmas Gift—

BECAUSE—CQ is the one magazine in the Ham field that pays top dollar for top-notch feature material. You don't take a chance on catching a "prize" from a CQ article because everyone of them is paid for.

BECAUSE—CQ has a staff of experts in each one of the important Ham activities. Since they are not clustered in one area they gain a diversified view of what the reader wants to see in CQ. Maybe our departments are copied, but they will never be equalled for coverage.

BECAUSE—CQ plans on expanding in the fields to be of greatest interest to the maximum number of readers. Having demonstrated our leadership in mobile work we will go on to thoroughly cover other important aspects of the hobby.

BECAUSE—CQ has consistently published the most outstanding articles on new subjects within the past year. In antennas it's the "T2FD"; in mobile noise limiting it's the "TNS"; in receivers it's "Mechanical Filters"; in VHF it's the "Piggy-Back"—name any field and see if CQ hasn't covered it!

Subscribe now by using this handy envelope



P.S. Not shown in the regular subscription rate chart is our "Buddy Rate" which provides a means of sending a subscription to a friend overseas as a Xmas present. A one-year subscription plus your own one year subscription (or extension) may be obtained at only \$5.00. This is a saving of \$2.00 over the individual rates. Why not take advantage of this offer to tell someone overseas you are thinking of them.

CQ Magazine

67 WEST 44th Street
New York 36, N. Y.

(from page 63)

YLRL 14th ANNIVERSARY PARTY RULES

- Dates:** Phone Start Sat., Dec. 6, at 1200
RST Fri. Sun., Dec. 6, at 1200
CW Start Sat., Dec. 12, at 1200
RST Sat. Sun., Dec. 13, at 1200
- Operation:** All bands. Cross-band operation, phone to phone and CW to CW, is permitted.
- Frequencies:** All bands. Cross-band operation, phone to phone and CW to CW, is permitted.
- Eligibility:** Contest open to any licensed YL or XYL operators throughout the world. Not limited to YLRL members. Contacts with OM's do not count.
- Procedure:** Call "CQ YLRL."
- Exchange:** QSO number; RS or RST report; name of State, U. S. Possession, VE District or Country.
- Scoring:**
a—4 points for each contact.
b—Same YL may be worked on other bands for additional credit.
c—Add number of points and then multiply by number of different States, U. S. Possessions, VE Districts and Countries worked. Maryland and District of Columbia count as one state.
d—All phone contestants running 150 or less watts input at all times may then multiply the final score by 1.5.
e—All CW contestants running 150 or less watts input at all times may then multiply the final score by 1.25.
- Awards:** Highest phone score—Cup
Highest CW score—Cup
These cups are awarded on a yearly basis. Any operator winning the same cup three times gains permanent possession of it.)
2nd and 3rd place awards to be determined.
- Logs:** Copies of phone and CW contestants logs must be postmarked not later than Dec. 31st, 1953; to be sent directly to Ruth B. Siegelman, W2OWL, Vice-President, YLRL 1414 Wythe Place, Bronx 52, New York.
When submitting copies of logs, please list phone contacts and CW contacts separately.

oak-leaf QSL card. Her prize was an Englishware dinner plate with a picture of the N.H. State House archway. Following the informal YL get-together, a YLRL meeting was held under the guidance of Ann, W1OAK, first district chairman. Ann gave a door prize which was a title with the State of Vermont on it. She gave a short history of YLRL and nominations were made for first district D/C for next term.

The Delta Division held its convention in New Orleans on Sept. 5-6. Though we have no list of YLs attending, there were some 200 XYLs and YLs who enjoyed the afternoon tea, informal coffee and "Out of Style" show. This depicted styles worn from 1910 through the 30's and apparently was as much enjoyed by the OM's who invaded the entertainment as by the gals. Lots of the ladies went home happy with prizes won, for close to fifty were given away, the top ones a TV set, oriental rug and three sets of dinnerware.

Here and There

W9FZO and W9FSS are now definitely located in Florida. The QTH: 1038 Macy, West Palm Beach.
(Continued on next page)

CRYSTALS!

370	396	419	443	466	491	513
372	397	420	444	468	492	514
374	398	422	445	469	493	515
376	400	423	446	470	494	516
378	401	424	447	472	495	518
379	402	425	448	473	496	519
379	403	426	450	474	497	520
380	404	427	451	475	498	522
381	405	429	452	476	500	523
383	406	430	453	477	501	525
384	407	431	454	479	502	526
385	408	433	455	480	503	527
386	409	434	456	481	504	528
387	411	435	457	483	505	530
388	412	436	458	484	506	531
390	413	437	459	485	507	533
391	414	438	461	486	508	534
392	415	440	462	487	509	536
393	416	441	463	488	511	537
394	418	442	464	490	512	538
395				495	513	540

ASSORTED SPECIALS:

- Any 5 Above Assid. Crystals (except the 500 Kc) 39c ea.
Any 10 Above Assid. Crystals (except the 500 Kc) 29c ea.
Any 20 Above Assid. Crystals (except the 500 Kc) 25c ea.

COMPLETE SET—80 CRYSTALS

- In above graduations from 370-516 Kc., 54th Harmonic, INCLUDING 500 Kc. & 455 Kc. crystals. **\$9.95**
Only Per Set

COMPLETE SET—120 CRYSTALS

- In above graduations from 370-540 Kc., 72nd Harmonic, PLUS 500 Kc. & 455 Kc. crystals. **\$14.95**
Only Per set

- 200 KC. CRYSTAL Ea. \$2.25
500 KC. CRYSTAL Ea. 1.25
1,000 KC. CRYSTAL Ea. 3.25

- All crystals sent as is and sent postpaid.
All items subject to prior sale. Send for FREE Catalog.

- ARW-2 REMOTE CONTROL UNIT**
Front can be converted to 2 meter. Comes equipped with large complement of tubes, & crystal. Has ten 10,000-ohm relays which can be made into individual radio control units. All new, Full Price. **\$27.50**

J. J. GLASS ELECTRONICS CO.
1624 S. MAIN ST. LOS ANGELES 15, CALIF.

ANOTHER RAISE!

Men and women often report two pay raises—sometimes three—while studying with I. C. S. That's just the beginning! You'll be amazed how fast you progress, how quickly you can master any one of 391 fascinating subjects. Personalized instruction by mail. Low cost. Courses tailored to your needs—whether unskilled or executive. Easy-to-follow texts. Diplomas to graduates.

TWO FREE BOOKS

"How to Succeed." Also free big catalog on course that interest you

INTERNATIONAL CORRESPONDENCE SCHOOLS
Box 2784, Scranton 9, Pa.

Without cost, send me free book "HOW TO SUCCEED" and free catalog on course checked.

- | | |
|--|--|
| <input type="checkbox"/> Accounting | <input type="checkbox"/> Highway Engineering |
| <input type="checkbox"/> Aeronautical Engineering Jr | <input type="checkbox"/> Hydro Electric Power Plant |
| <input type="checkbox"/> Aircraft Design | <input type="checkbox"/> Industrial Engineering |
| <input type="checkbox"/> Architecture | <input type="checkbox"/> Industrial Instruments |
| <input type="checkbox"/> Architectural Drawing | <input type="checkbox"/> Industrial Supervision |
| <input type="checkbox"/> Automobile Mechanic | <input type="checkbox"/> Machine Shop Practice |
| <input type="checkbox"/> Auto Elec. Technician | <input type="checkbox"/> Mathematics |
| <input type="checkbox"/> Bookkeeping | <input type="checkbox"/> Mechanical Engineering |
| <input type="checkbox"/> Building Contractor | <input type="checkbox"/> Mechanical Drafting |
| <input type="checkbox"/> Business Administration | <input type="checkbox"/> Practical Accounting |
| <input type="checkbox"/> Certified Public Accounting | <input type="checkbox"/> Practical Electricity |
| <input type="checkbox"/> Chemical Engineering | <input type="checkbox"/> Reading Shop Blueprints |
| <input type="checkbox"/> Civil Engineering | <input type="checkbox"/> Reading Structural Blueprints |
| <input type="checkbox"/> Cotton Manufacturing | <input type="checkbox"/> Radio Servicing |
| <input type="checkbox"/> Diesel Engines | <input type="checkbox"/> Railroad |
| <input type="checkbox"/> Diesel Locomotive | <input type="checkbox"/> Railway Postal Service |
| <input type="checkbox"/> Drafting | <input type="checkbox"/> Salesmanship |
| <input type="checkbox"/> Electrical Engineering | <input type="checkbox"/> Stenographic Secretarial |
| <input type="checkbox"/> Electrical Maintenance | <input type="checkbox"/> Structural Engineering |
| <input type="checkbox"/> Electronics | <input type="checkbox"/> Textiles |
| <input type="checkbox"/> Foremanship | <input type="checkbox"/> Toolmaking |
| <input type="checkbox"/> Television | <input type="checkbox"/> Tool Design |
| <input type="checkbox"/> General Radio | <input type="checkbox"/> Traffic Management |
| <input type="checkbox"/> High School | |

Other _____

Name _____ Age _____

Home Address _____

City _____ State _____

Occupation _____

Special tuition rates to members of Armed Forces. Canadian residents address International Correspondence Schools Canadian, Montreal.

RADIO Surplus Buys




MIDGET TYPE NT-6 WILLARD 6-V STORAGE BATTERY DRY CHARGED

3 amp hour rating. Transparent plastic case. Size $3\frac{3}{8}'' \times 1-13/16'' \times 2\frac{3}{8}''$. Weight approx. $1\frac{1}{4}$ lbs. Uses standard electrolyte. Regularly lists at \$12.00 **\$2.49 ea.** each. Now sensationally **4 for \$8.50** priced. New. Unused. **postpaid**


TUNER FROM NAVY

"BN" EQUIPMENT

Simply modified into 2-meter converter for car or communications receiver.

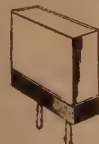

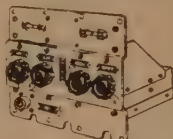Uses 1-6J6, 1-6SH7, 1-9006, 1-6J5 (Not Furnished). Slug is tuned from 157 to 187 Megacycles. Includes schematic diagram for "BN" equipment. Now—A New LOW Price Each



\$3.95

CRYSTALS

in FT 241-A Holders— $\frac{1}{2}''$ Pin SPC Marked 54th OR 72nd Harmonic MC Freq. Listed below by fundamental frequency with fractions omitted.
500 KC Crystals ea. **\$1.95** 1000 KC Crystals ea. **\$3.95**
200 KC Crystals ea. **\$3.95**
Write for our complete list of crystals and prices.

POWER TRANSFORMER

Primary 125 volts tapped at 105 and 115 volts 50 to 425 cycles. Secondaries: 5.1 v. at 3.0 amps. 325-0-325 v. at 0.175 amp., 5.4 v. at 8 amp., 6.4 v. at 10.3 amp., 2.5 v. at 3.0 amp., 4500 v. at .005 amp., 2.5 v. and 4500 volt windings insulated for 6000 volts. All other windings insulated for 1500 volts. Cost government more than \$42.00—a real bargain at—Ea. **\$3.95**
Shipping wt. 29 lbs.

ALL EQUIPMENT F.O.B. PASADENA UNLESS OTHERWISE SPECIFIED. PLEASE ENCLOSE FULL AMOUNT WITH ORDER

C & H SALES CO.

2176 E. Colorado St. - Pasadena 8, Calif.
Box 356-NQ East Pasadena Station - Pasadena 8, Calif.

WANTED

WE NEED YOUR SURPLUS
ELECTRONIC EQUIPMENT

WE PAY TOP \$\$\$ FOR:

- RADIO RECEIVERS
- TRANSMITTERS
- ARC-1
- ARC-3
- ART-13
- CONTROL BOXES
- INDICATORS
- CLAMPS
- PLUGS
- CORDS
- RELAYS
- TELEPHONE MATERIALS
- AN CONNECTORS
- WE BUY ANYTHING!

WRITE, WIRE TODAY! TELL US WHAT YOU HAVE

TALLEN CO., Inc., Dept. CQ

159 Carlton Ave. Brooklyn 5, N. Y.

Selectronic Supplies, Inc.

has moved to
1320 MADISON AVENUE
TOLEDO, OHIO

Free catalog and gift to those who report reading this announcement.

(from preceding page)



The all-Ham Battin family of Elgin, Ill. L. to r.: John, W9MEM; Edith, OTO; Ev, OWD; and John, OTM. The photo was taken on Aug. 14th, the 20th wedding anniversary of Edith and Ev.

Helen and Ralph send a special thank-you to all the Hams they visited this summer and who extended such grand hospitality.

New check-ins for the NYLON net are W7PQW, W7RXT and VE7UF.

September meeting of the Los Angeles YLRO drew twenty-five YLs. In addition to regular club members there were these visitors: W3VNN, W5RFK, W6AKE, SGL, QLM, PCO and KN6ACN.

W6EHA, Gen, is new NCS for the YLRL 20-meter net (14,240 kc) beginning Oct. 1st. Gen and he OM, by the way, are sporting a new 32V3, a 75A3 and a new steel desk to hold 'em. Seems this all comes by way of having lived in a trailer all the time they were in Las Cruces, N.M., and saved paying rent!

33—till next month—W5RZ.

PI-NETWORKS

(from page 25)

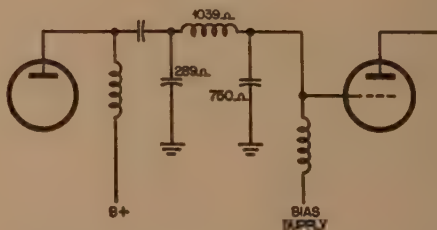


Fig. 6. Final values for solution of second problem.

Conclusion

The pi-network has a definite role in the design of new equipment. It is hoped that this simplified approach may help in understanding how the pi-network may be used. Credit is due to WØEDB for advice and suggestions on this solution.

Do you want cash for that old receiver?—see our revitalized classified section! Is your junkbox overflowing into the living room? Well, make a clean sweep with the aid of a CQ classified ad. You'll be more than satisfied with the results.

AMPLITUDE MODULATION REVIEW

(from page 37)

of a final amplifier tube having a third of the dissipation that would be required with constant carrier. The peak d-c power that must be delivered by the power supply, however, is still the same as that for constant-carrier operation with carrier power P_c . To the extent that the required power-supply regulation can be achieved by adding filter capacity, the power-supply requirements approach the average power consumption of about one-fourth the supply required for constant-carrier operation

TABLE 3. SCREEN MODULATION PLATE DISSIPATION
 $P_c = 13.5$ WATTS

CARRIER	TOTAL D-C POWER INPUT P_d (WATTS)	AVERAGE CARRIER POWER OUTPUT (WATTS)	PEAK-MODULATION CARRIER OUTPUT P_p (WATTS)
CONSTANT	22	7.3	7.3
CONTROLLED	17*	4.4*	22

* WITH PERFECT POWER SUPPLY REGULATION


• WITH MODULATION CARRIER POWER ZERO WITH NO MODULATION.

with carrier power P_c . Table 3 compares the peak-modulation carrier output power, the average carrier output, and the d-c power input required for operation of the final at 13.5 watts plate dissipation.

Conclusions

The questions posed at the beginning of this article can now be given definite answers on the basis of our calculations. As far as overall power efficiency is concerned, there is no particular reason for choosing one type of modulation over another; the difference between the most efficient method and the least efficient is less than one decibel. The choice must be made, therefore, on the basis either of convenience or of equipment simplicity. For a given final amplifier tube whose power input is limited by tolerable plate dissipation, and for constant-carrier operation, plate modulation allows a carrier power output about three times greater than screen modulation. Because of limitations on final amplifier plate voltage and current, controlled-carrier operation yields no practical increase in peak-modulation output for plate modulation. For screen modulation, the use of controlled carrier allows about three times the peak-modulation carrier output of constant-carrier operation with an average carrier output that is considerably less.

EIMAC ACCESSORIES for the Custom Rig...

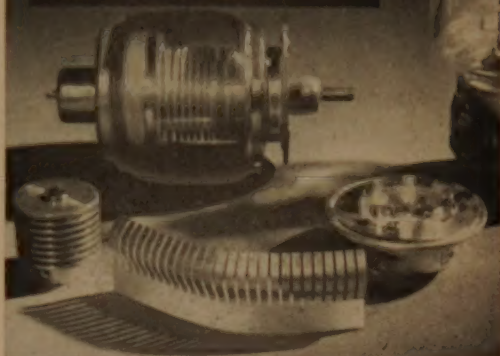

- ★ VACUUM CAPACITORS ★ HR CONNECTORS
- ★ AIR-SYSTEM SOCKETS ★ FINGER STOCK

Preformed contact finger stock is an ideal electrical weather stripping for TVI proofing cabinets as well as being excellent for use with VHF and UHF circuitry. Silver plated, three widths—17/32, 31/32, and 1 7/16 inches.

HR heat dissipating connectors, precision machined from dural rod, available in 10 sizes.

Air system sockets, designed for Eimac tube types 4-400A, 4-1000A, 4X150A and 4X150D, simplify cooling and assure adequate flow of air to various seals.

Variable vacuum capacitors come in three models, are lightweight, compact and have low inductance. Also available are eight types of fixed vacuum capacitors.

- ★ For information
write our Amateurs'
Service Bureau.

EITEL-McCULLOUGH, INC.
SAN BRUNO, CALIFORNIA



Export Agents: Frazer & Hansen, 301 Clay Street, San Francisco, California

EASY TO LEARN CODE

It is easy and pleasant to learn or increase speed the modern way—with an Instructograph Code Teacher. Excellent for the beginner or advanced student. A quick, practical and dependable method. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready, no QRX, beats having someone send to you.

ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for full particulars and convenient rental plan.



INSTRUCTOGRAPH COMPANY

Dept. C., 4701 SHERIDAN RD., CHICAGO 40, ILL.

GET YOUR COMMERCIAL TICKET EASIER WITH...

RADIO OPERATOR'S LICENSE
Q AND A MANUAL
(4th Edition)


by Milton Kaufman
Covers Elements 1 through
8. Complete discussion
of answers to every
technical question in the
F.C.C. Study Guide! Used
by over 50 leading
schools. Only \$6.60 at
jobbers, bookstores
or direct from—



JOHN F. RIDER Publisher, Inc.
480 Canal Street, New York 13, N. Y.



AMAZING NEW VIBROPLEX

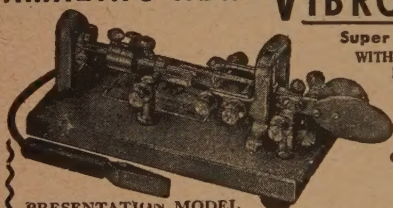

Super Deluxe
WITH ADJUSTABLE
MAIN SPRING
AND OTHER
GREAT
FEATURES
24-K
GOLD-PLATED
BASE TOP
\$29.95

PRESENTATION MODEL

Vibroplex presents the first really speed control key. An adjustable main spring permits operator to send slower or faster as desired. No more muddy signals... no sacrifice of signal quality! Suits any hand or any style of sending. Free of arm tension. Sends easily as pressing a button. Praised by operators and beginners alike. Try this new Vibroplex key! You'll be delighted. Other new popular Vibroplex keys from \$12.95 up. At your dealer or

THE VIBROPLEX CO., INC. 833 Broadway, N. Y. 3, N. Y.

MOBILES! C. D. MEN! CAP!!

IDEAL DYNAMOTOR — CONVERTS EASILY
TO SUPPLY UNIT DELIVERING

12 VOLT INPUT

610V @ 150 MA

325V @ 125 MA

BRAND NEW WITH CONVERSION DATA \$3.75

Send Check or M.O.

6V INPUT

300V @ 90 MA

160 @ 110 MA

Ship. Chgs. C.O.D.

COMMUNICATIONS EQUIPMENT CO.

131 LIBERTY ST

Q-11

NEW YORK 7, N. Y.

GOTHAM 20 M. 2-E1 BEAM INCLUDES:

1-12 Foot Boom 1" Alum. Tubing

2-12 Foot Centers, 1" Alum. Tubing

4-12 Foot Ends 3/8" Alum. Tubing

1-T match, with polystyrene tubing

1-Mounting casting

All hardware, fittings, castings

Assembles quickly, adjustable over entire band, stacks easily.

Only \$24.95—sent on approval by express collect to licensed

Hams. Send for data on 6-10-15 and 20 meter beams.

Gotham Hobby Corp., Dept. C-2, 107 E. 126 St., N.Y.

MAIL ORDER ANTENNA

(from page 37)

in the coaxial feed line. Set the shorting bar at an arbitrary position and feed a small amount of r-f energy at the desired frequency into the feed line. Adjust the variable condenser for minimum SWR. If the SWR is higher than desired, change the position of the shorting bar slightly and re-adjust the variable condenser. Repeat as often as necessary to reduce the SWR to a satisfactory value.

This procedure assumes that the radiator itself is fairly close to resonance, so that it will efficiently radiate the power fed into it. This is a valid assumption, especially as the large diameter of the radiator reduces its Q , making its length non-critical. The relatively-small length/diameter ratio is also the reason the recommended radiator length is somewhat less than that of a conventional $1/4$ -wave antenna constructed of wire or small-diameter tubing.

For a given set of conditions, the position of the shorting bar and the capacity of the series condenser can be calculated with fair accuracy by making certain assumptions. However, because results still require a cut-and-try procedure, therefore the mathematics are omitted. Antenna design is an art, not a science! However, thanks are due to W6DSZ of the Antenna Laboratory, University of California, for his original assistance in calculating constants for the feed system.

Life Expectancy Of Antenna

All metal is subject to corrosion, especially when in contact with the earth. Aluminum is no exception; therefore a check was made with a metallurgist on the life that can be expected from this antenna. The following is based upon his report:

If the antenna is installed in dry, sandy soil its life will be indefinite. In normally-moist soil which is essentially chemically neutral, a minimum life of five years can be expected. In weakly-heavily-alkaline or acid soil, corrosion is more intense and the useful life will decrease. If in doubt of the type of soil in your yard, an easy-to-use kit for testing its acidity or alkalinity may be obtained from any garden-supply store.

The critical point is at the ground level of the vertical member. Corrosive pitting of the tubing will decrease its strength, and heavy winds might snap off the antenna. This possibility can be greatly decreased by driving a five-foot wooden "round" inside the tubing; that the point of maximum stress will be raised about a foot above the ground, where it will be isolated from corrosive effects of the earth.

Do not saturate the base of the antenna in salt solution to decrease the ground resistance. It or sea water will corrode aluminum practically while you watch.



**FREE 156 PAGE
1954 B-A CATALOG**

Complete guide to Everything in Radio, TV and Electronics for Dealers, Servicemen, Schools, Amateurs, Broadcasters, Public Utilities, Engineers, Experimenters, Factories and Laboratories.

BURSTEIN-APPLEBEE CO., 1012 McGEE ST., KANSAS CITY, MO.

COMMENTARIES

(from page 29)

theoretical aspect that increased signal strengths may be expected if some care is taken in developing a suitable vertically directive array. While they particularly mention a broadside array of dipoles, it appeared that comparable results might be obtained using a single horizontal wire below the radiator acting as a reflector. This idea was put into practice as shown in Fig. 1.

This antenna was cut for the 40-meter band and has a reflector mounted one-tenth wavelength below the radiator. The reflector was tuned with a short stub at the center in order to avoid pruning the ends. Tuning was accomplished by adjusting the stub for a minimum reading on a field strength meter directly below the reflector. The field strength meter had a horizontal antenna of the miniature variety.

The SWR would reach a value of 1.3:1 for any frequency to which the reflector was adjusted. It rose to 2:1 about 75 kc. either side of this frequency.

High Angle Results

Excellent results were obtained with this antenna. Stations from 40 to about 350 miles away reported that my signals were louder with the high-angle radiator than they were with the vertical. Some stations reported a 20 db. increase in signal strength. The general of improvement was of the order of $1\frac{1}{2}$ S-units. At distances of 350 to 600 miles the two antennas seemed to be about equal. Beyond this the vertical took over (these tests were at night) and during the daytime the vertical was the better antenna at any distance.

A bonus with this type of antenna is the reduction of night-time static that arrives via fairly low angles. Using the high angle radiator I was often able to read DX signals that were buried in the static on the vertical.

Further Experiments Needed

Many questions remain to be answered regarding this type of radiator. I feel that a beam consisting of two elements spaced a quarter-wavelength and fed 90 degrees out-of-phase will produce a considerably broader radiation pattern than this parasitic array. There is some indication that this radiator/reflector shown in Fig. 1 is too sharp.

This idea will probably work best on 75-meters where high-angle radiation is somewhat more important. In any case, the high-angle beam is not offered as a DX catcher, but it does have possibilities for traffic work, contests and medium distant QSO's.

Major R. H. Mitchell, W6TZB

MULTI-BAND OPERATION

S
I
N
G
L
E



SIDEBAND

8 TIMES THE VOICE POWER
HARMONIC TVI VIRTUALLY ELIMINATED
MULTIPHASE EXCITER MODEL 10A (upper left) Approx. 10 watts peak output 160 to 20 meters, somewhat less on 10-15 meters. Will drive beam power tetrodes to more than 1 KW input from 20 to 160 meters. SWITCHABLE SSB, with or without carrier, double sideband AM, PM, break-in CW, VOICE OPERATED BREAK-IN and receiver disabling, it's ALL BUILT-IN to this truly versatile exciter. Built-in power supply also furnishes blocking bias for linear amplifier and voltage for optional VFO. With internal xtal and coils for one band. Wired and tested \$159.50. Complete kit \$112.50. Extra coil sets \$3.95 per band.

QT-1 ANTI-TRIP UNIT

Plugs into socket inside 10A EXCITER. Permits loudspeaker operation, yet prevents voice-control circuit from tripping on heterodynes, static, noise pulses or loud signals. All electronic, no relays, adjustable trip level. Completely wired, with tube. Price.....\$12.50

SIDEBAND SLICER

MODEL A RECEIVER ADAPTER (upper right) Improves any receiver. SWITCHABLE upper and lower sideband reception of SSB, AM, PM and CW. Cuts interference and heterodynes in half. Eliminates distortion caused by selective fading. Works into any receiver having 450-500 KC IF. Built-in power supply. Use a Model A Slicer—notice the "holes" in even our most crowded bands and hear signals you have never heard before. Wired and tested \$74.50. Complete kit \$49.50. PS-1 Plug-in prealigned 90 degree phase shift network and socket available separately for use with GE Signal Slicer and SSB Jr. \$7.95 postpaid. WRITE FOR LITERATURE

Central Electronics, Inc.

2125 W. Giddings Street

Chicago 25, Illinois


"RADIO AMATEURS"

PROTECT YOUR SHACK AND MOBILE FROM FIRE
FIRE-KILLER

THE FAMOUS CO₂ EXTINGUISHER

No Maintenance Expense, No Leakage, No Freezing, No Dangerous Acids, No Explosion Risk, No Poison Gas
FIRE-KILLER Contains no Injurious Chemicals.
Anyone can safely use it.

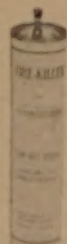This improved dry chemical compound is non-deteriorating and unaffected by climate. When brought into contact with fire it develops carbon dioxide gas that at once smothers the flame. Carbon dioxide is known to be the fastest and safest fire extinguishing agent yet discovered.



STOPS FIRE INSTANTLY
FIRE-KILLER has no complicated mechanism and will last a lifetime, requiring no attention or inspection.
PRICED ONLY \$3.00 POSTPAID
FREE test sample of compound on request
FIRE-KILLER MFG. CO. OF PENNA.
HAZLETON, PENNA.

ELECTRONIC TUBES


URGENTLY NEEDED

Cash paid for: Radio, TV, Special Purpose, all types, small and large quantities. State types, quantities, prices.

Write Now to Box AA.

c/o CQ, 67 West 44th St., New York 36, N.Y.

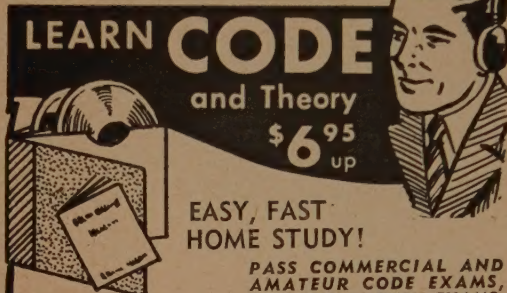for a CAREER in communications
... to pass FCC amateur exams



LEARN CODE
and Theory
\$6.95
up

**EASY, FAST
HOME STUDY!**

**PASS COMMERCIAL AND
AMATEUR CODE EXAMS,
AMATEUR THEORY EXAMS,
FOR YOUR FCC LICENSE!**

78 RPM

4 AMECO Courses Available:

No. 1—NOVICE CODE COURSE. You get and keep 10 recordings (alphabet through 8 W.P.M.). Includes typical FCC type code exams. Free instruction book on learning how to send and receive code the simplest, fastest way; plus charts to check your receiving accuracy; plus an album; all for the low price of only.....**\$7.95**

No. 2—SENIOR CODE COURSE. You get and keep everything given in the Novice Course except that you get 22 recordings (alphabet through 18 W.P.M.), plus typical FCC type code exams for General class and 2nd class commercial telegraph licenses. All this for only.....**\$12.95**

No. 3—COMPLETE RADIO THEORY COURSE. A complete, simplified home study theory course in radio covering the Novice, Technician, conditional and general classes—all under one cover—with nearly four hundred typical FCC type questions to prepare you for license exam: No technical background required. You also get, FREE, one year of consultation and a guide to setting up your own Ham station. All for the amazing low, low price of.....**\$6.95**

No. 4—NEW ADVANCED CODE COURSE. Prepares Novice operators for the amateur general class and second class commercial license tests. Contains 12 recordings (8 through 18 W.P.M.) PLUS the complete code book—PLUS typical F.C.C. code examinations for general and commercial tests. ALL for only.....**\$6.95**

FREE LITERATURE AVAILABLE

Sold at leading distributors everywhere
or write direct to
Dept. C-11

AMERICAN ELECTRONICS CO.
1203 Bryant Ave., New York 59, N.Y.

Memo

Before you buy or trade, be sure to get our prices.

We stock all the leaders, including Hallcrafters, National, RME, Hammarlund, Elmac, Babcock, Gonset and a host of others.

You just can't beat buying from an old time and active Ham.

Fast four-hour shipping service. Trades accepted, and time payments if you wish.

M. H. DOSSETT CO.

"You always get more—
From a Ham Parts Store"

855 Burlington Ave., Frankfort, Ind.

8 WIRE CONTROL CABLE

Two No. 16. Six No. 20 tinned, stranded, copper, rubber insulated coded leads. Waterproof rubber jacket. Woven copper armor shield overall. Diameter 7/16 inch. Length to 400 ft. Minimum order 100 ft. Prepaid delivery 10¢ ft. made to nearest express or post office. U.S.A. only. **PREPAID**

TRANS-WORLD RADIO-TELEVISION CORP.

6639 S. ABERDEEN ST.

CHICAGO 12, ILL.

Phone: Austin 7-4538

CLASSIFIED ADS

Advertising in this section must pertain to amateur radio activities. Rate 25¢ per word per insertion for commercial advertisements. 5¢ per word for non-commercial advertisements. Remittances in full must accompany copy. Phone orders not accepted. No agency or term or cash discounts allowed. No display or special typographical setups allowed. "CQ" does not guarantee any product or service advertised in the Classified Section. Closing date for ads is the 25th of the 2nd month preceding publication date. Write: Jeanne Gillespie, Classified Ads, CQ, 67 W. 44th Street, New York 36, N.Y.

For Sale:

SONAR MR-3 MOBILE receivers \$39.95; RME mobile converters \$39.95; Meissner EX Signal Shifter with four coil strips \$39.95; Millen 90700 Variarm V \$19.95; Millen 90800 Exciters with tubes and one set coils \$19.95; other similar bargains in used, reconditioned equipment. Write for latest list to WIBFT, Evans Ranch, Concord, New Hampshire.

Going off **TWO METERS**. Sell SCR 522 transmitter. A converter built commercially, in cabinet. Single power supply for both. Four-element beam. Best offer takes or all. Don Renkowitz, K2DUW, 3020 Yates Avenue, Bronx 69, New York.

FREE LIST. New and reconditioned receivers, transmitters, etc. A hundred big bargains every month. High trade-in allowance. Fast four-hour shipping service. Special Novice department. Write today. Dossett, W9B 855 Burlington, Frankfort, Indiana.

FOR SALE: Two multiband mobile or base transmitter. Miscellaneous items. W4OHM, 739 Berryville Avenue, Winchester, Virginia.

FOR SALE: Astatic JT-30 Microphone \$7.50; Shure Dynamic \$35; Speidel men's gold watchband \$7.50; Faco vinylite wading pants for fishing, new, \$6; Hallcrafters "Sky Buddy" communications receiver \$20; portable radio LB-530, new Willard 2-volt battery cabinet \$25; Meck 6-tube walnut-cabinet radio; Tele-tone 8-tube AM-FM table radio \$25; small GE portable \$10; Collins FM-11 FM tuner \$45; Alliance A antenna rotator, never outdoors, \$15; Webster 3-speed record changer, GE RPX-050 triple-play cartridge, Garrard 2-speed changer, GE cartridge \$20; Columbia microgroove player \$10; Brush PL-20 transcription pickup, equalizer \$15; Audak transcription pickup, magn \$15; Eicor 1000 tape recorder, 7 1/2" speed, 7" reels, track, \$85; Twin-Trax tape recorder, same specification plus automatic reverse and two-way drive, built-in radio and phonograph \$150; Consumers Research high-fidelity amplifier, fine as speech amplifier (built-in microphone preamplifier) with 6SC7, 6J5, 2-6SN7, 2-6B4G, 5Y4 Peerless transformers, \$50; same amplifier, kit for \$35; Smith-Corona Silent Deluxe portable typewriter \$45; York tenor saxophone, case, \$65; Spertip portable ultraviolet-infrared lamp \$10; neon sign transformer \$7.50; vertical drillpress stand for 1/4" electric \$7.50. All items guaranteed excellent, priced FOB. Write: Hein, 418 Gregory, Rockford, Illinois.

REAL BARGAINS: New and reconditioned Col. Hallcrafters, National, Hammarlund, Johnson, Elmac, Gonset, Babcock, Morrow, RME, Millen, Lyso, etc. Reconditioned S38C \$85, S40A \$69, S40B \$79, S27 \$76 \$129, SX42 \$179, SX62 \$179, NC125 \$129, NC149, NC183 \$199, NC183D \$229, VHF152A \$49, Meissner 9-1090 bandswitching VFO \$49, HRO129X, SX71, 775A2, 32V2, 32V3, HRO50T1, HRO60, HRO Sr., and many others. Shipped on approval. Terms financed by us. Write for free list. Henry Radio, Butler, Miss. **BC-221 FREQUENCY METER**, original crystal, original calibration book, nice condition, checked against W \$60. Also BC-221 frequency meter, original crystal, original calibration book, good condition, fine for VFO, BC453 Q5'er, 190 to 550 kc., like new \$10. BC459-A transmitter, 7 to 9.1 Mc., good condition \$10. Shipped prepaid up to 600 miles. Tooker, W2VQL, Lakehurst, Jersey.

FOR SALE: Complete 1 kw. transmitter, built to commercial standards in closed rack. Remote Collins 31 drives PP 813's. Coils for 80, 20 and 10. D104 self-contained speech amplifier and self-contained 805's modulator. Best cash offer as unit. W3DGM, So. Biltmore St., Indianapolis, Indiana.

NATIONAL 101X receiver \$60. 7" TV \$30; 10" Want SSB Exciter. W4API, 1420 South Randolph, Virginia.